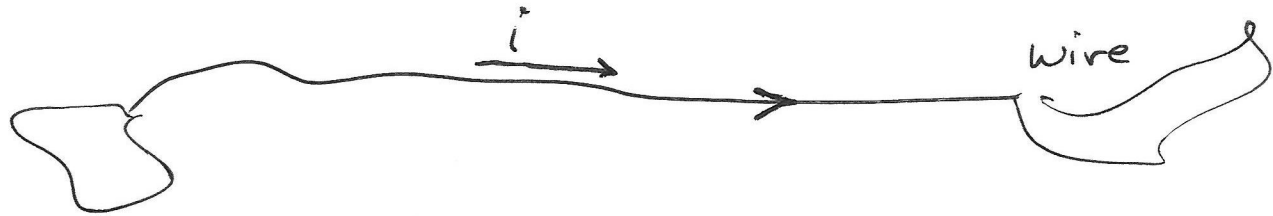


Current, $i \triangleq \frac{dq}{dt}$



lower case $i \Rightarrow$ time varying current
 upper case $I \Rightarrow$ constant

Resistor

units of resistance are ohms

A greek letter Ω
omega

ω is angular
rotation speed

R_1
 $10k\Omega$


R_2
 $2M\Omega$

R_3


Scientific Notation

T	10^{12}	tera
G	10^9	giga
M	10^6	mega
k	10^3	kilo
m	10^{-3}	milli
lower case Greek mu	10^{-6}	micro
n	10^{-9}	nano
p	10^{-12}	pico
f	10^{-15}	femto

Back to resistors.

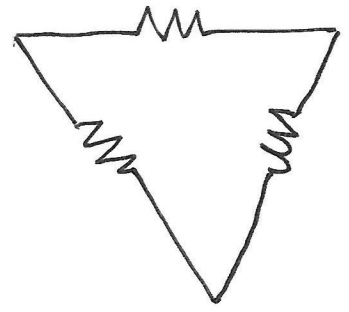

If we define a current

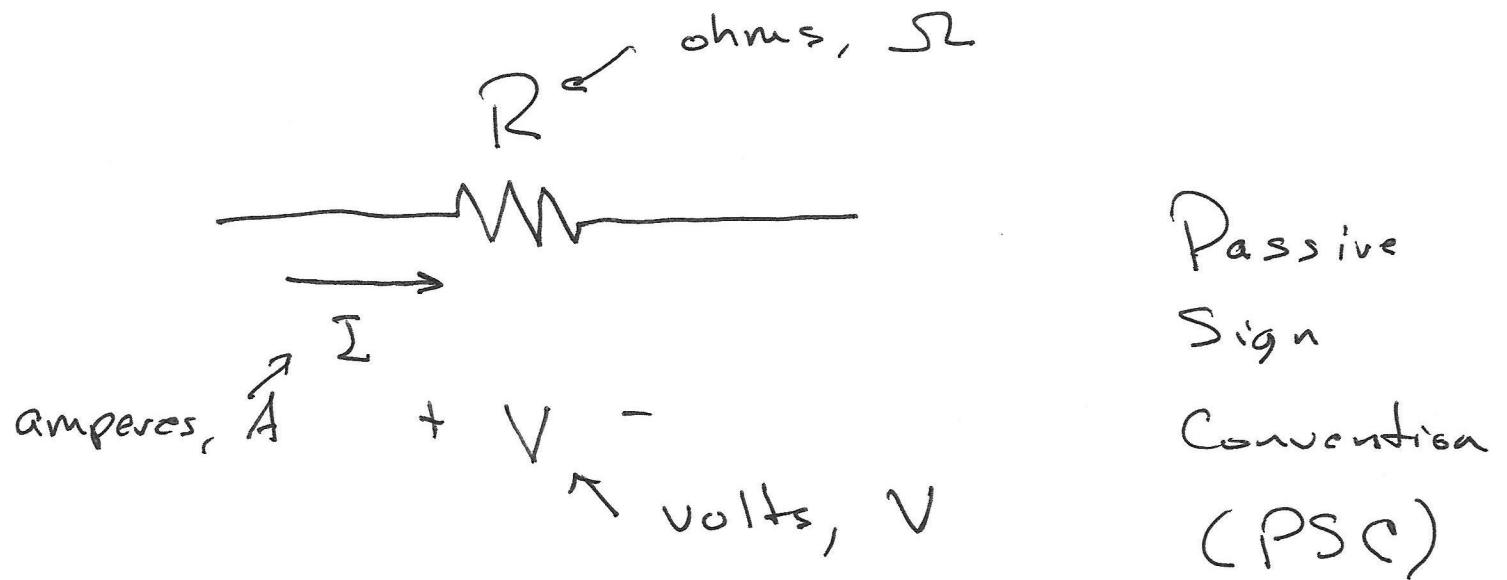

$$\boxed{V = RI \quad \text{Ohm's Law}}$$

For a resistor, V and I always satisfy the PSC


\Rightarrow resistors always absorb power.

Power:

$$P = VI$$

watts, W volts, V amperes, A

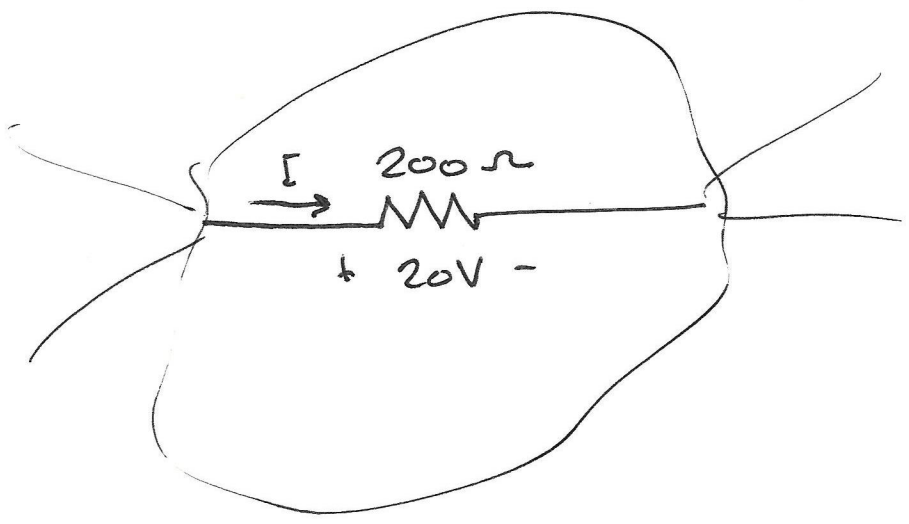For a resistor, if V and I
reference directions satisfy the PSC,
then $P \geq 0$.



$I = ?$

$$V = IR$$

\uparrow \uparrow
 20 200

$$I = \frac{V}{R} = \frac{20}{200} = \frac{1}{10} A$$

$= 100mA$

$$I = \frac{V}{R} = \left(\frac{1}{R}\right) V$$

conductance

G ~~ohms~~
 siemens, S



Capacitor

Farads, F

C_1
50nF

C_2


C_3
20pF

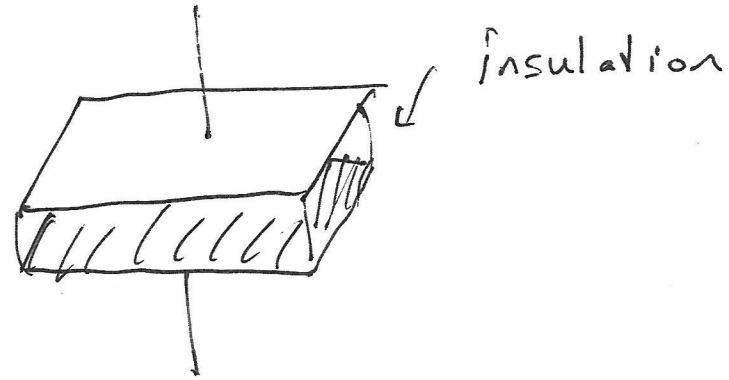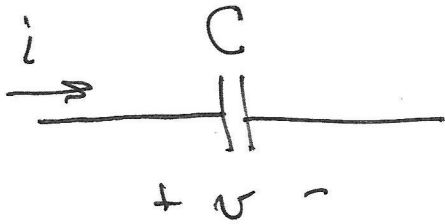

If we define a current i and a voltage v ,
that satisfy the PSC, then

$$i = C \frac{dv}{dt}$$

Inductor

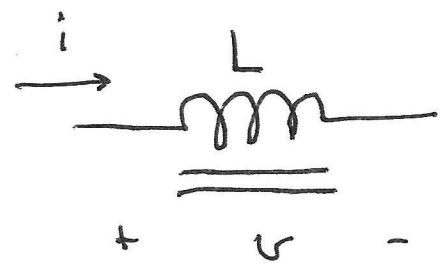


If v and i satisfy the PSC,
then

$$v = L \frac{di}{dt}$$

Annotations for the equation above:


- An arrow points from the word "volts" to the variable v .
- An arrow points from the word "henry, H" to the variable L .
- An arrow points from the word "amperes" to the variable i in the numerator of the derivative.
- An arrow points from the word "seconds" to the variable t in the denominator of the derivative.

Sources:

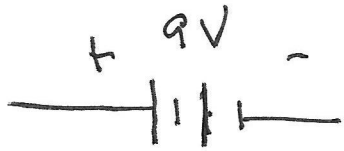


Battery symbol

voltage source

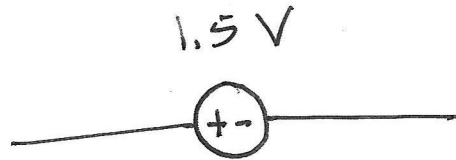

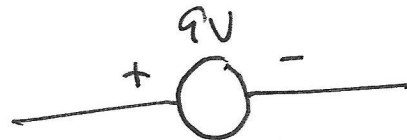
standard flashlight battery,
or clock battery



Most of the time, sources do not satisfy the PSP,
because they deliver power.


Kirchhoff's Laws:

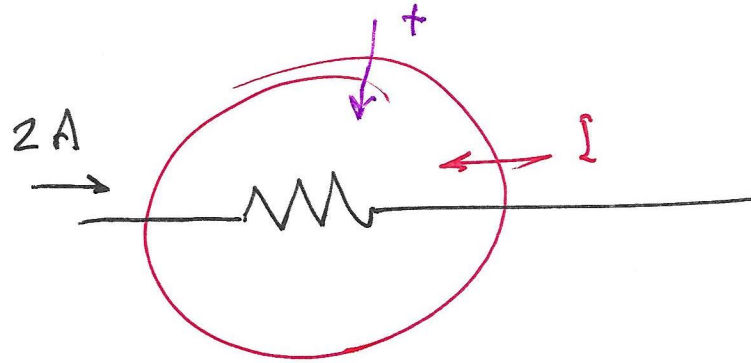1. The algebraic sum of all currents crossing any closed boundary is zero.



Kirchhoff's Current Law:
(KCL)


$$2A + I = 0$$
$$\Rightarrow I = -2A$$

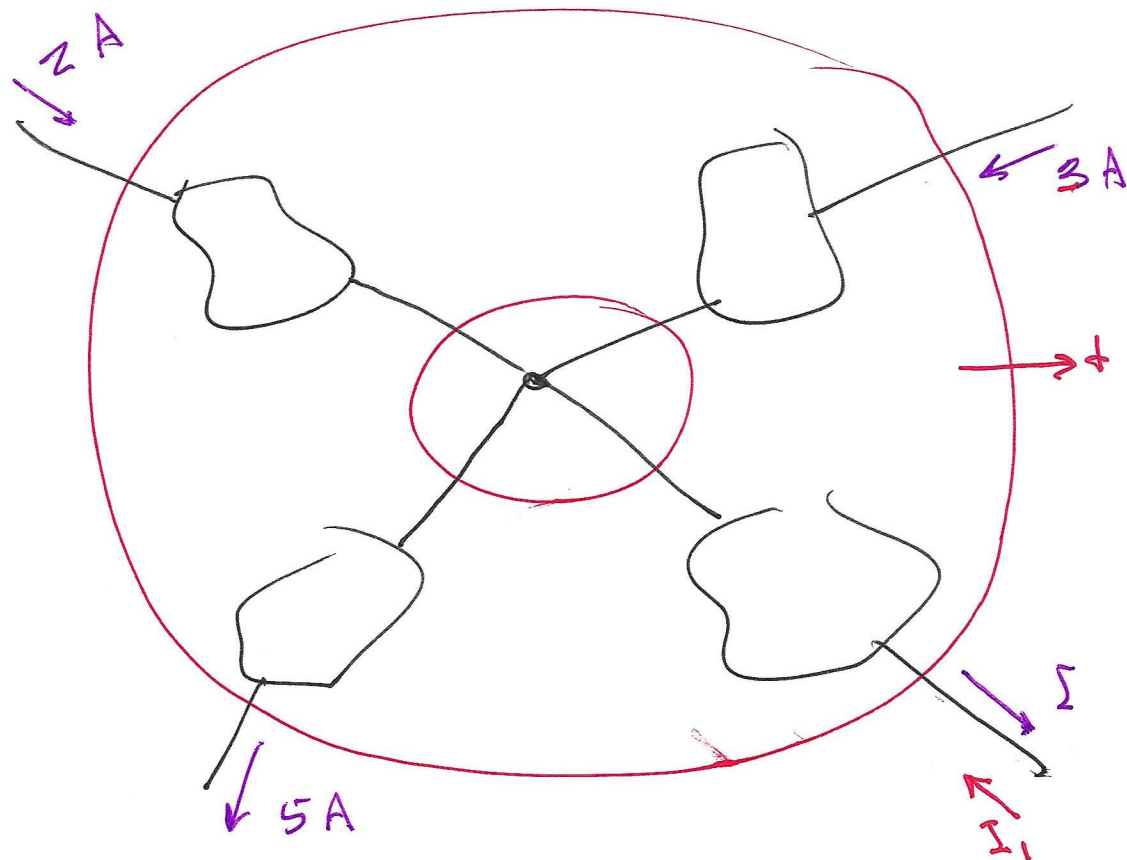

KCL: $-3 - 2 + 5 + I = 0$
 $\Rightarrow I = 0$

$$I_1 + 1 + 3 - 5 = 0$$

$$I_1 = 1A$$

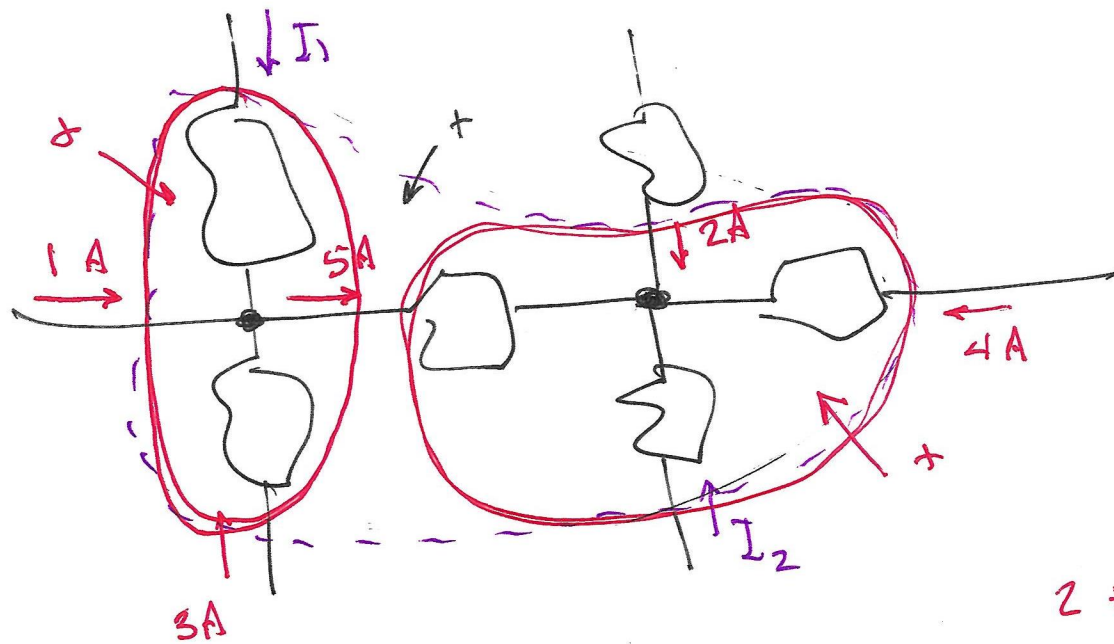

$$2 + 4 + I_2 + 5 = 0$$

$$I_2 = -11A$$


$$I_1 = ?$$

$$I_2 = ?$$

$$\begin{array}{ccccccc}
 I_1 + 1 + 3 + I_2 + 4 + 2 & = & 0 \\
 \uparrow & & \uparrow & & & & \\
 1 & & -11 & & & & \\
 & & & & & & = 0
 \end{array}$$

Kirchhoff's Voltage Law (KVL):

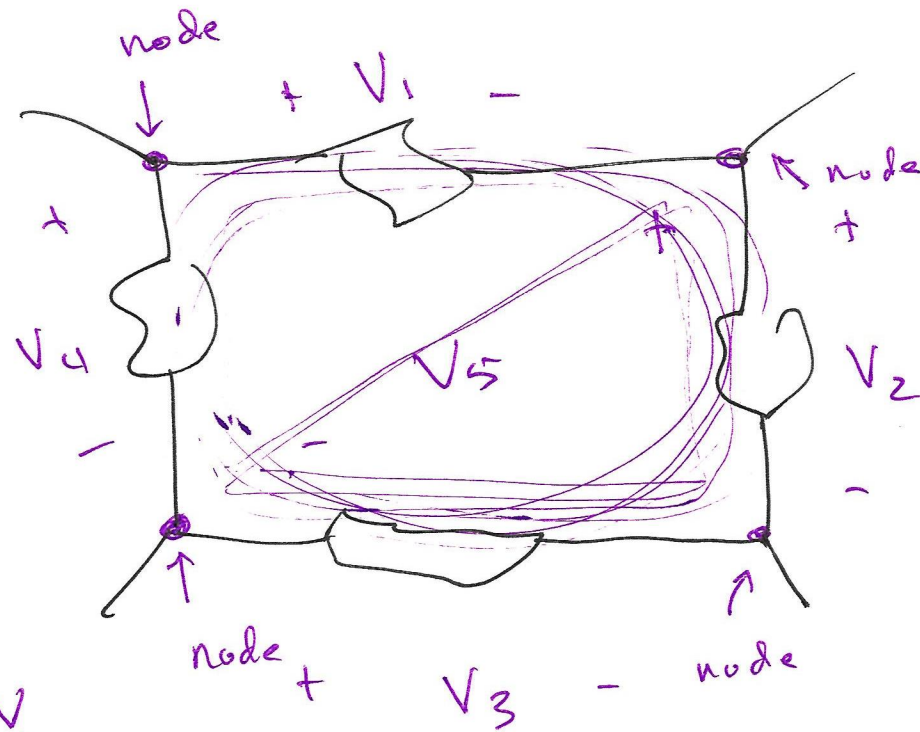The algebraic sum of all voltages encountered around any closed ^{path} is zero.



$\sum f$ $V_2 = 16V$,
then $V_3 = ?$

$\sum f$ $V_1 = 10V$
 $V_4 = 12V$
then $V_5 = ?$
 $+V_1 + V_5 - V_4 = 0$
 $10 + V_5 - 12 = 0$
 $V_5 = 2V$

$$-V_5 + V_2 - V_3 = 0$$

$$-2 + 16 - V_3 = 0 \Rightarrow V_3 = 14V$$

$$-V_4 + V_1 + V_2 - V_3 = 0$$

$$-12 + 10 + 16 - V_3 = 0 \Rightarrow V_3 = 14V$$