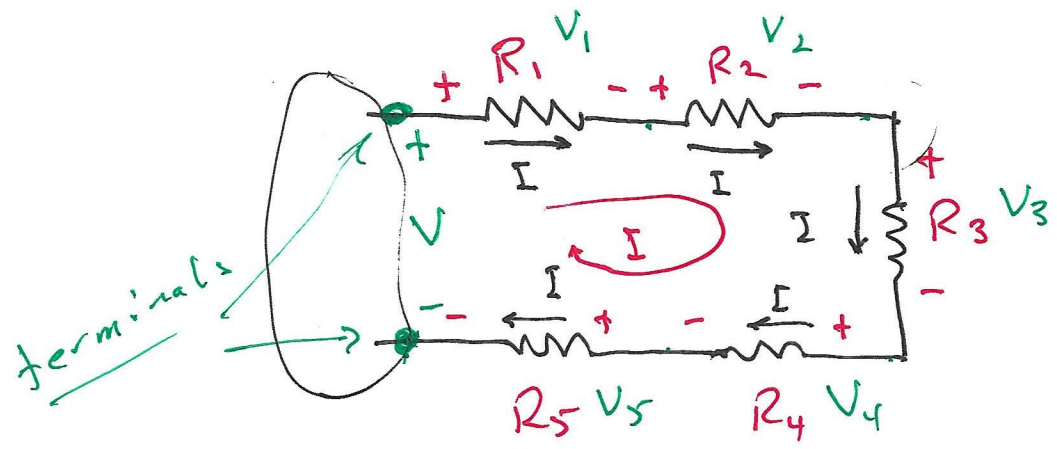


Equivalent

Series Resistors



All ~~resistors~~ ^{components} have the same current.

$$-V + V_1 + V_2 + V_3 + V_4 + V_5 = 0 \quad (\text{KVL})$$

$$V_2 = R_2 I$$



$$\begin{aligned}
 V &= R_1 I + R_2 I + R_3 I + R_4 I + R_5 I \\
 &= \underbrace{(R_1 + R_2 + R_3 + R_4 + R_5)}_{R_{eq}} I
 \end{aligned}$$

$$\frac{V_2}{V} = \frac{R_2 I}{R_{eq} I} = \frac{R_2}{R_{eq}}$$

$$V_2 = \frac{R_2}{R_{eq}} V$$

Voltage Divider


Example

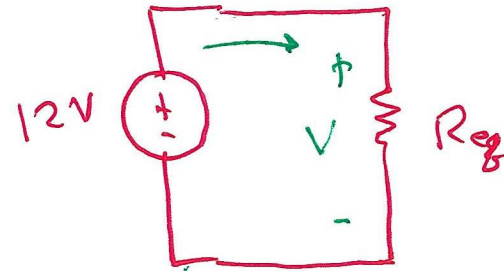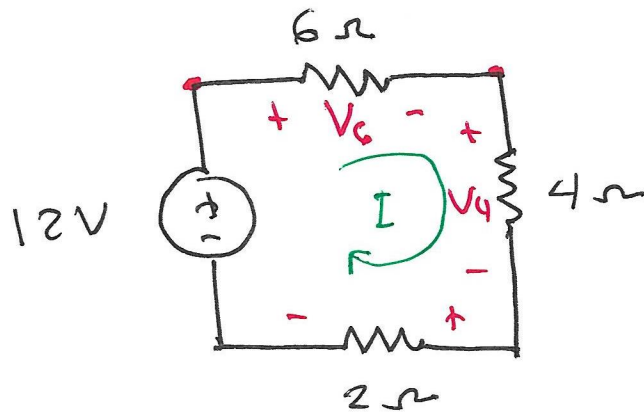

$$V_6 = \frac{6\Omega}{6\Omega + 4\Omega + 2\Omega} \cdot 12V = 6V$$

$$I = \frac{6V}{6\Omega} = 1A$$
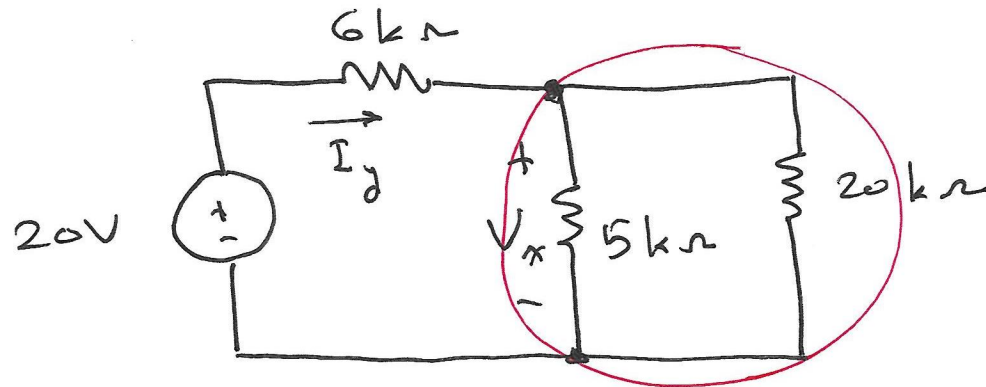
$$V_4 = \frac{4\Omega}{12\Omega} \cdot 12V = 4V$$



Determine:

- V_x
- I_y
- Power delivered to the $20k\Omega$ resistor.


$$\frac{1}{R_{eq}} = \frac{1}{5k\Omega} + \frac{1}{20k\Omega}$$

$$= \frac{4 + 1}{20k\Omega}$$

$$= \frac{1}{4k\Omega}$$


$$R_{eq} = 4k\Omega$$

(parallel resistor equivalent)

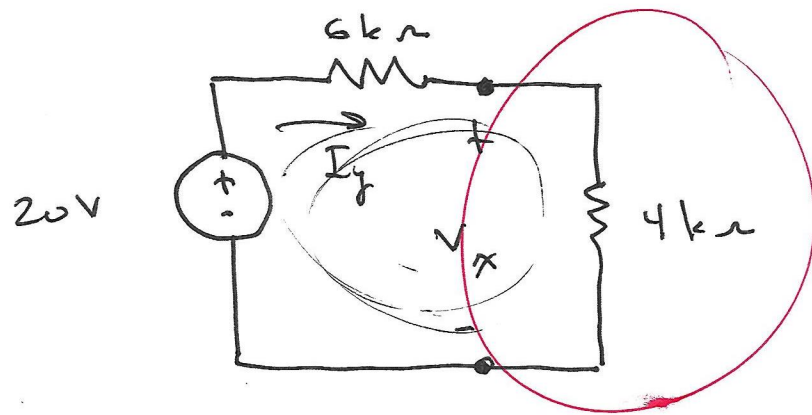

$$V_x = \frac{4k\Omega}{6k\Omega + 4k\Omega} \cdot 20V$$
$$= 8V$$
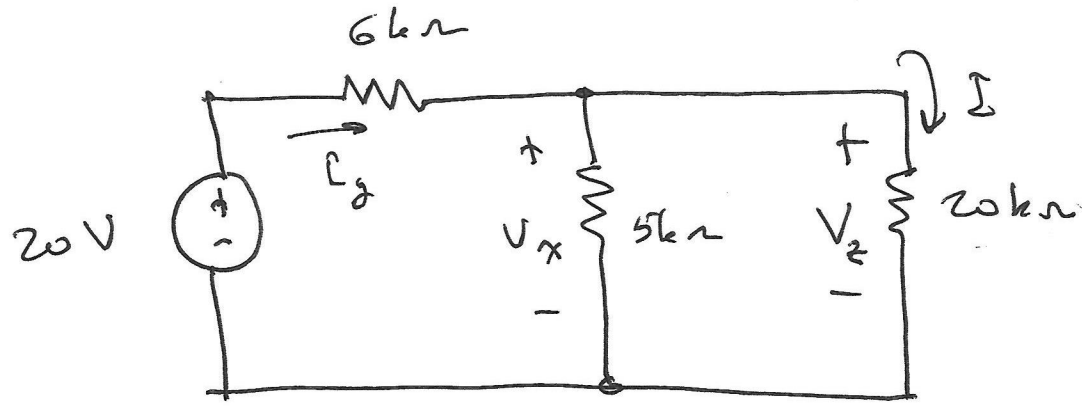
$$I_y = \frac{V_x}{4k\Omega} = \frac{8V}{4k\Omega} = 2mA$$




$$V_x = 8V, \quad I_g = 2 \text{ mA}$$

$$P_{20k\Omega} = V \cdot I = 8V \cdot \frac{V_z}{20k\Omega}$$

$$= 8V \cdot \frac{8V}{20k\Omega}$$

$$= \frac{64}{20} \text{ mW}$$

$$= 3.2 \text{ mW}$$

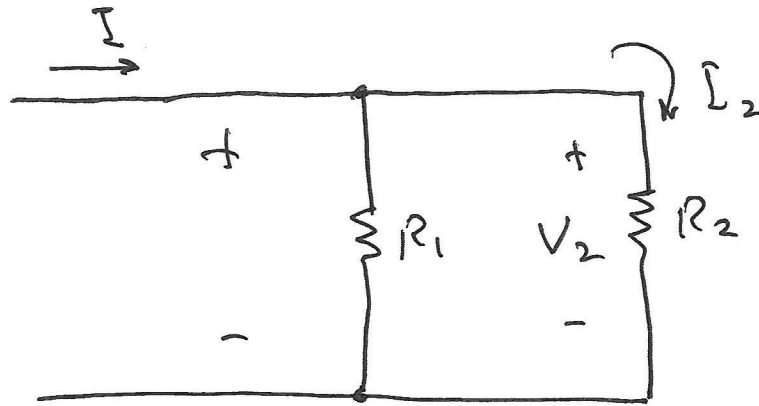

Given I ,
determine I_2 .

$$V_2 = R_2 I_2$$

also $V_2 = R_{eq} I$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$\therefore R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{1}{G_{eq}}$$

$$R_2 I_2 = R_{eq} I$$
$$= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} I$$

$$\Rightarrow \frac{I_2}{I} = \frac{1}{R_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right)} = \frac{1}{\frac{R_2}{R_1} + 1}$$
$$= \frac{R_1}{R_2 + R_1}$$

For 2 resistors, $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$

$$\Rightarrow G_{eq} = \frac{R_1 + R_2}{R_1 R_2}$$


This page was
corrected after
class.

$$\frac{I_2}{I} = \frac{R_1}{R_1 + R_2}$$

$$I_2 = \frac{R_1}{R_1 + R_2} I$$

Current
Divider

Mind
Reset

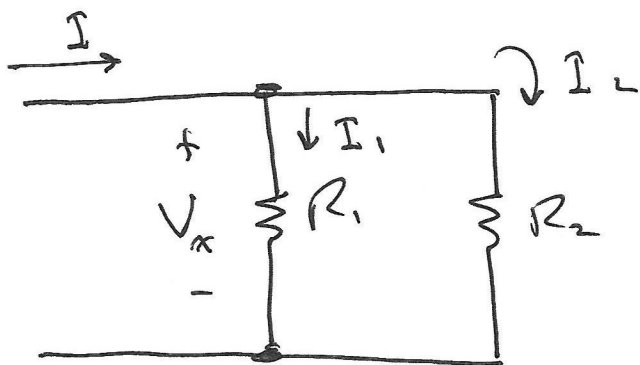

$$I_2 = \frac{V_x}{R_2}$$


$$I = \frac{V_x}{R_{eq}} = \frac{V_x}{\left(\frac{R_1 R_2}{R_1 + R_2}\right)} = \frac{R_1 + R_2}{R_1 R_2} V_x$$

$$\frac{I_2}{I} = \frac{\frac{1}{R_2} V_x}{\left(\frac{R_1 + R_2}{R_1 R_2}\right) V_x} = \frac{R_1 R_2 \frac{1}{R_2}}{R_1 + R_2}$$
$$= \frac{R_1}{R_1 + R_2}$$

$$I_2 = \frac{R_1}{R_1 + R_2} I$$

Current
Divider



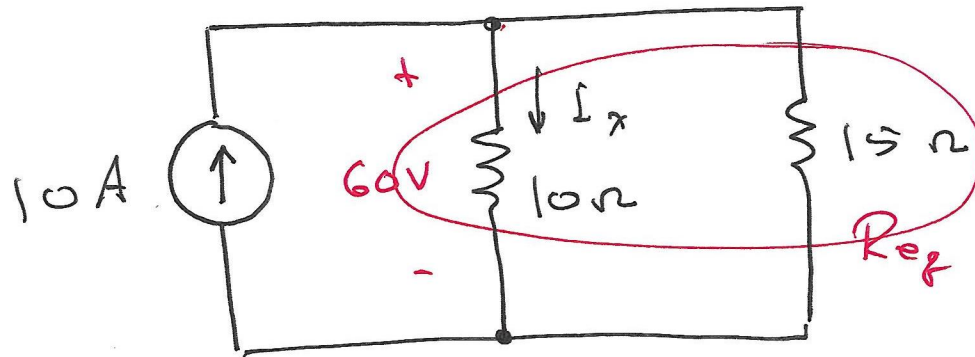


Determine the value of I_x .


$$\frac{I_x}{10A} = \frac{15\Omega}{10\Omega + 15\Omega}$$

$$I_x = \frac{3}{5} 10A = 6A$$
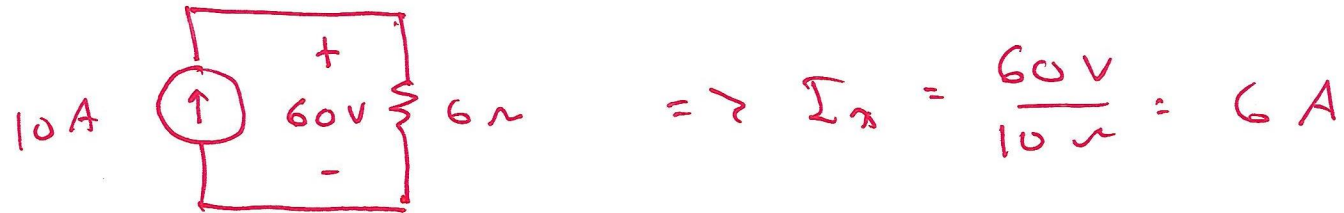
$$R_{eq} = \frac{10 \cdot 15}{10 + 15} = \frac{150}{25} = 6\Omega$$



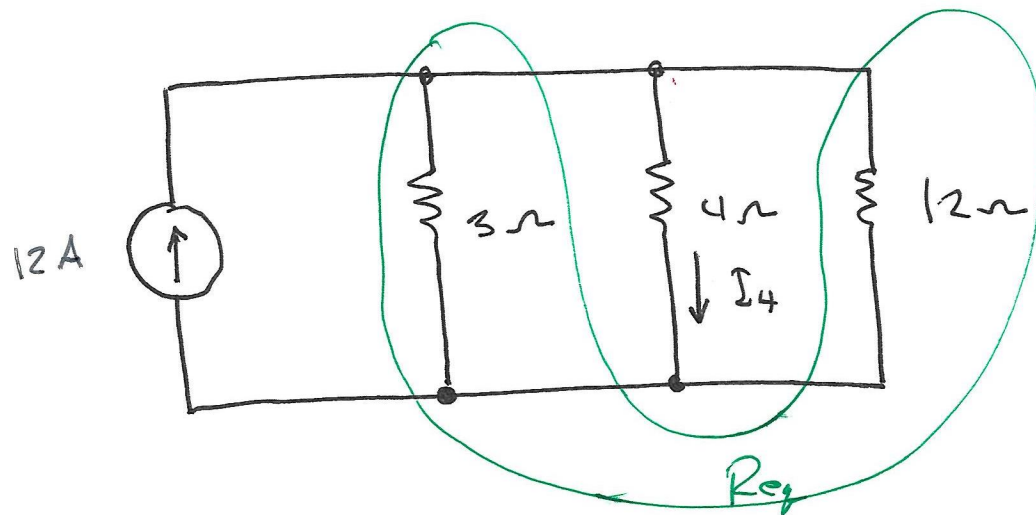
$$\Rightarrow I_x = \frac{60V}{10\Omega} = 6A$$



Determine the value of I_4 .
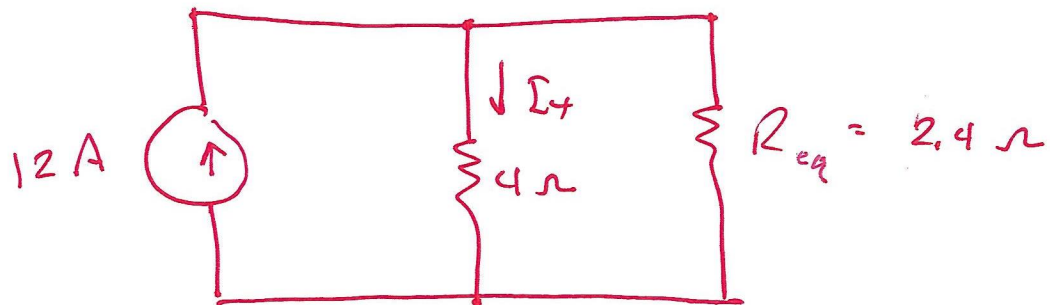
$$R_{eq} = \frac{3 \cdot 12}{3 + 12} = \frac{36}{15} = \frac{12}{5} = 2.4 \Omega$$



$$I_4 = \frac{2.4}{4 + 2.4} \cdot 12 A$$

$$= \frac{2.4}{6.4} \cdot 12$$

$$= \frac{3}{8} \cdot 12 = \frac{36}{8} = 4.5 A$$