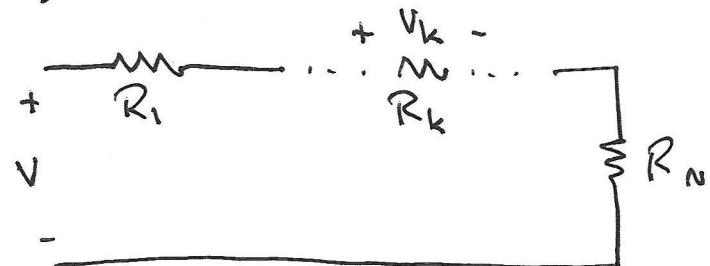



stuffle.website

Voltage Divider (series resistors)




$$\frac{V_k}{V} = \frac{R_k}{R_1 + \dots + R_k + \dots + R_N} = \frac{R_k}{R_{\text{eq}}}$$

Current Divider (parallel resistors)

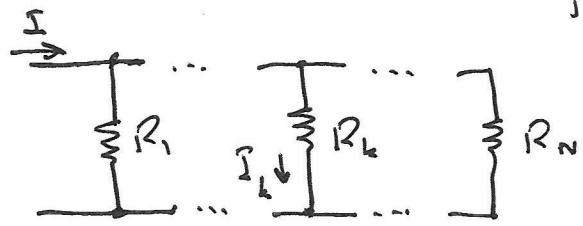


$$\frac{I_k}{I} = \frac{\frac{1}{R_k}}{\frac{1}{R_1} + \dots + \frac{1}{R_k} + \dots + \frac{1}{R_N}} = \frac{G_k}{G_{\text{eq}}}$$

Special case, 2 resistors

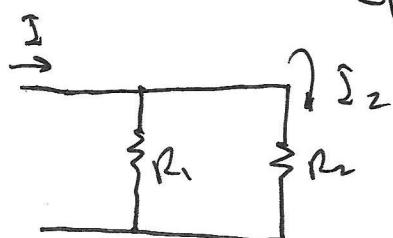

$$\frac{I_2}{I} = \frac{R_1}{R_1 + R_2}$$

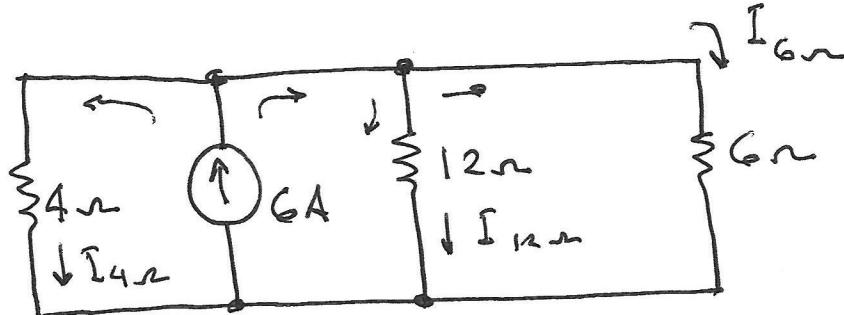Do not try to extend this to 3 or more resistors.



$$\frac{I_{6R}}{6A} = \frac{\frac{1}{c}}{\frac{1}{4} + \frac{1}{12} + \frac{1}{6}}$$

$$= \frac{\frac{2}{c}}{\frac{1}{c}} = \frac{2}{1}$$

$$I_{6R} = 2 \text{ A}$$


$$\frac{I_{12R}}{6A} = \frac{\frac{1}{12}}{\frac{1}{4} + \frac{1}{12} + \frac{1}{6}} = \frac{1}{6}$$

$$I_{12R} = 1 \text{ A}$$

$$\frac{I_{4R}}{6A} = \frac{\frac{1}{4}}{\frac{1}{4} + \frac{1}{12} + \frac{1}{6}} = \frac{3}{6} = \frac{1}{2} \Rightarrow I_{4R} = 3 \text{ A} \quad (\text{CD})$$

$$I_{4R} + I_{12R} + I_6 = 6A \quad \Rightarrow \quad I_{4R} = 3 \text{ A} \quad (\text{KCL})$$

(2)

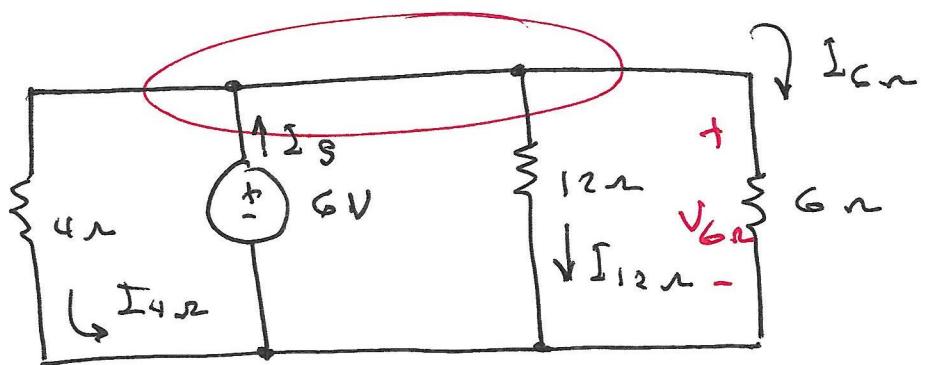

$$I_{6\text{ohm}} = \frac{6\text{V}}{6\text{ ohm}} = 1\text{ A}$$

$$I_{12\text{ohm}} = \frac{6\text{V}}{12\text{ ohm}} = \frac{1}{2}\text{ A}$$

$$I_{4\text{ohm}} = 1\frac{1}{2} \text{ A}$$

$$\Sigma_s = 3\text{ A} \quad (\text{KCL})$$


$$P_{6n} = V_{6n} \cdot I_{6n} = 6V \cdot 1A = 6W$$

$$P_{12n} = V_{6n} \cdot I_{12n} = 6V \cdot \frac{1}{2}A = 3W$$

$$P_{4n} = V_{6n} \cdot I_{4n} = 6V \cdot \frac{3}{2}A = 9W$$

$$P_s = P_{6n} + P_{12n} + P_{4n} = 6 + 3 + 9 = 18W$$
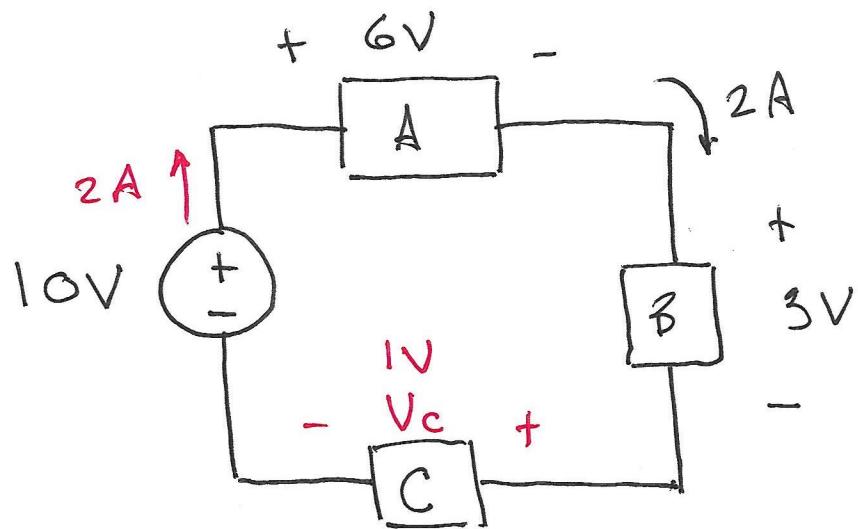
$$\text{or } 6V \cdot I_s = 6V \cdot 3A = 18W$$




1. Does C "absorb" or "deliver" power?
2. How much?
3. Does the source "absorb" or "deliver" power?
4. How much?

1. $-10 + 6 + 3 + V_c = 0 \Rightarrow V_c = 1 \text{ V}$

2. C absorbs power because V_c and the current satisfy the PSC.

$$P_c = 1V \cdot 2A = 2W$$

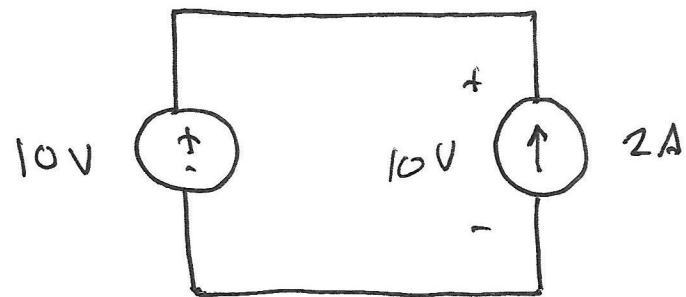3. delivers because it does not satisfy the PSC.
4. $P = 10V \cdot 2A = 20W$




Does the voltage source deliver power?

No because it satisfies the PSC.

$$\text{It absorbs } P = 10V \cdot 2A = 20W$$

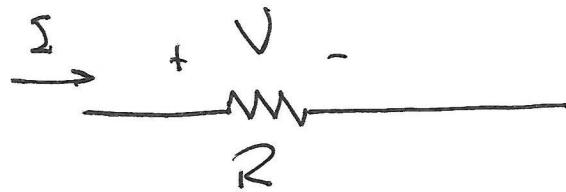The current source does not satisfy the PSC
 \therefore it delivers power = $10V \cdot 2A = 20W$



$$V = R \Sigma$$


or

$$\Sigma = \frac{1}{R} V$$

$$P = V \Sigma^2 = R I \cdot I = R I^2$$

$$= V \cdot \frac{1}{R} V = \frac{V^2}{R}$$
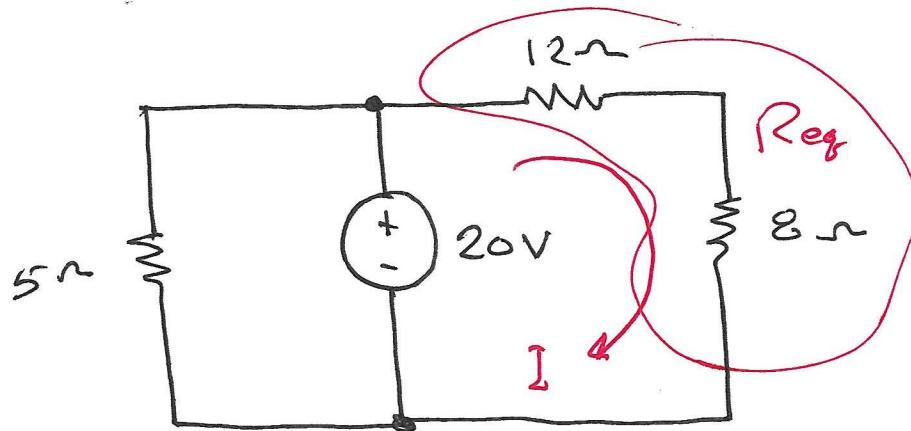
$$P = R I^2 \text{ or } \frac{1}{R} V^2 \text{ for a resistor}$$



How much power does each component deliver or absorb?

$$P_{\text{abs}, 5\Omega} = \frac{(20V)^2}{5\Omega} = 80 \text{ W}$$


$$R_Q = 12 + 8 = 20 \Omega$$

$$I = \frac{20V}{R_Q} = \frac{20V}{20\Omega} = 1 \text{ A}$$

$$P_{\text{abs}, 12\Omega} = I^2 \cdot 12\Omega = 1^2 \cdot 12 = 12 \text{ W}$$

$$P_{\text{abs}, 8\Omega} = I^2 \cdot 8\Omega = 1^2 \cdot 8 = 8 \text{ W}$$
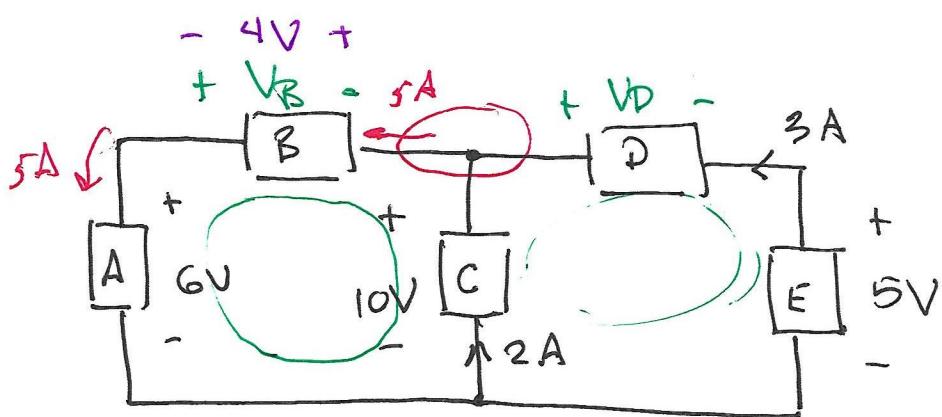
$$\begin{aligned} P_{\text{del}, 20V} &= P_{\text{abs}, 5\Omega} + P_{\text{abs}, 12\Omega} + P_{\text{abs}, 8\Omega} = 80 + 12 + 8 \\ &= 100 \text{ W} \end{aligned}$$



For each component, is power "delivered" or "absorbed"?

A absorbs power

$$-6 + V_B + 10 = 0 \Rightarrow V_B = -4V$$

B absorbs power

C delivers power

$$-10 + V_D + 5 = 0$$

D delivers power

$$\Rightarrow V_D = 5V$$

E delivers power
much?

How

$$P_A = 6V \cdot 5A = 30W \text{ absorbed}$$

$$P_B = 4V \cdot 5A = 20W \text{ absorbed}$$

50W absorbed

$$P_C = 10V \cdot 2A = 20W \text{ delivered}$$

$$P_D = 5V \cdot 3A = 15W \text{ delivered}$$

$$P_E = 5V \cdot 3A = 15W \text{ delivered}$$

Conservation of power
is satisfied.