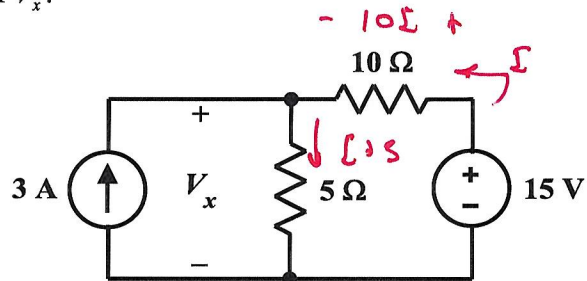


EE 2240  
Problem #03

Determine the value of  $V_x$ .



$$10 I + 5(I + 3) = 15$$
$$5I + 15$$

$$10 I + 5 I = 0$$

$$15 I = 0 \Rightarrow I = 0$$


$$I + 3 = 3$$

$$V_x = 5(3A) = 15V$$

Cut off last time.

EE 2240  
**Homework Problem #009**

For the circuit shown below:

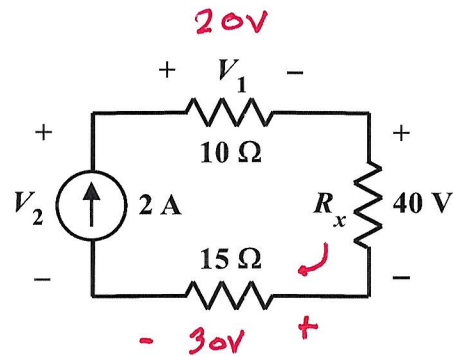

- a. Determine the value of  $V_1$ .

$$20 \text{ V} \quad \text{from Ohm's Law}$$

- b. Determine the value of  $R_x$ .

$$R_x = \frac{40 \text{ V}}{2 \text{ A}} = 20 \Omega$$

- c. Determine the value of  $V_2$ .

$$V_2 = 20 \text{ V} + 40 \text{ V} + 30 \text{ V} = 90 \text{ V}$$

- d. How much power does  $R_x$  absorb?


$$P_x = (40 \text{ V})(2 \text{ A}) = 80 \text{ W}$$

- e. How much power does the independent current source deliver?

$$P_s = (2 \text{ A}) V_2 = (2 \text{ A})(90 \text{ V}) = 180 \text{ W}$$

EE 2240  
**Homework Problem #010**

For the circuit shown below:

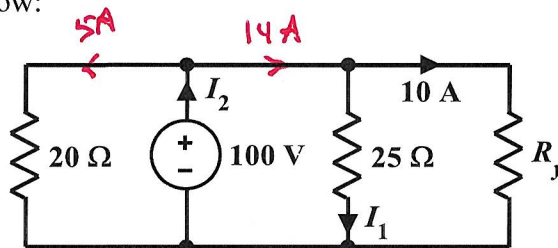

a. Determine the value of  $I_1$ .

$$I_1 = \frac{100\text{V}}{25\Omega} = 4\text{A}$$

b. Determine the value of  $R_y$ .

$$R_y = \frac{100\text{V}}{10\text{A}} = 10\Omega$$

c. Determine the value of  $I_2$ .

$$I_2 = 5\text{A} + 14\text{A} = 19\text{A}$$

d. How much power does  $R_y$  absorb?


$$P_y = (100\text{V})(10\text{A}) = 1000\text{W} = 1\text{kW}$$

$$= (10\text{A})^2 R_y = 1000\text{W} = 1\text{kW}$$

e. How much power does the independent voltage source deliver?

$$P_s = (100\text{V})(19\text{A}) = 1900\text{W} = 1.9\text{kW}$$

EE 2240  
Homework Problem #012

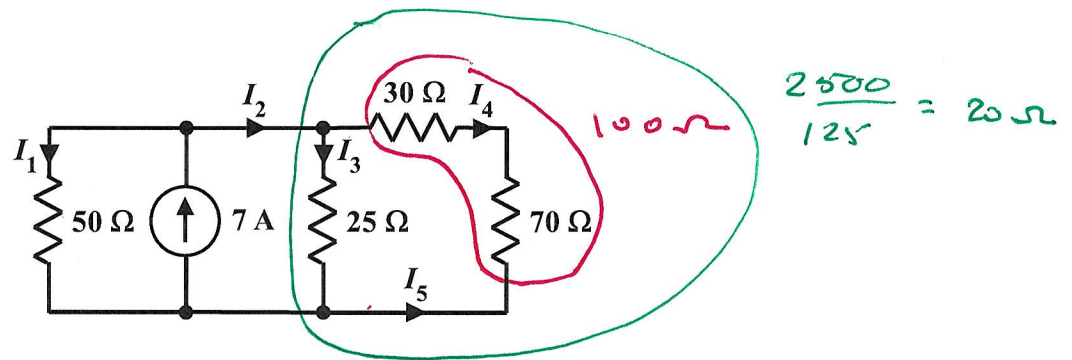

Use equivalent resistance and the current divider equation to determine each of the following:

a.  $I_1$

$$I_1 = \frac{\frac{1}{50}}{\frac{1}{50} + \frac{1}{25} + \frac{1}{100}} \cdot 7A = \frac{2}{7} \cdot 7 = 2A$$

b.  $I_2$

$$I_2 = \frac{50}{50 + 20} \cdot 7A = 5A$$

c.  $I_3$

$$\begin{aligned} I_3 &= I_2 - I_4 \\ &= 5A - 4A \\ &= 1A \end{aligned} \quad (\text{KCL})$$

d.  $I_4$


$$I_4 = I_2 - I_3 = 5 - 1 = 4A$$

e.  $I_5$

$$I_5 = -I_4 = -4A$$

$$I_3 = \frac{\frac{1}{25}}{\frac{1}{50} + \frac{1}{25} + \frac{1}{100}} \cdot 7 = 4A$$

EE 2240  
Problem #04

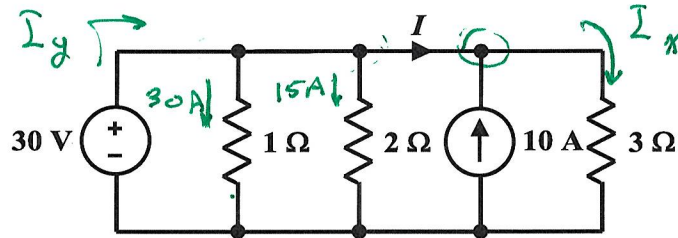

- a. Determine the power absorbed by the  $1\ \Omega$  resistor.

$$P_{1\Omega} = \frac{(30\text{V})^2}{1\Omega} = 900\text{ W}$$

- b. Determine the value of  $I$ .

$$I_x = \frac{30\text{V}}{3\Omega} = 10\text{ A}$$

$$I = 10\text{ A} - 10\text{ A} = 0$$

- c. Determine the power absorbed by the  $3\ \Omega$  resistor.

$$P_{3\Omega} = (10\text{A})^2 (3\Omega) = 300\text{ W}$$

- d. How much power is delivered by the 30 V independent voltage source?

$$I_y = 30\text{A} + 15\text{A} + I = 45\text{ A}$$


$$P_{V_S} = (30\text{V})(45\text{A}) = 1350\text{ W}$$

- e. How much power is delivered by the 10 A independent current source?

$$P_{10\text{A}} = (10\text{A})(30\text{V}) = 300\text{ W}$$


EE 2240  
Problem #05

Find  $V_o$ .

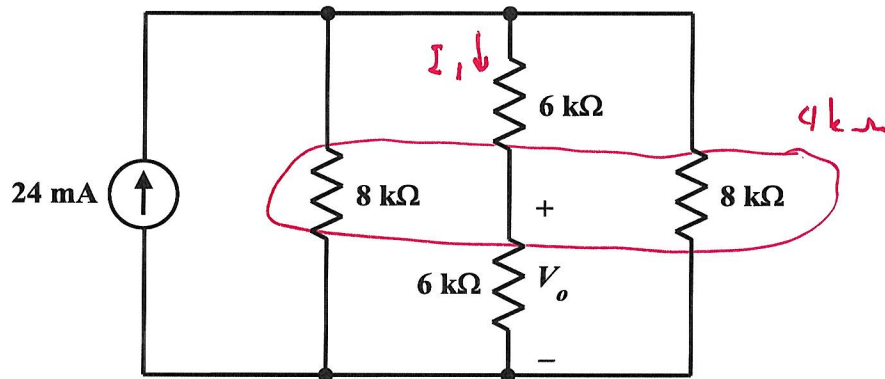

$$I_1 = \frac{4 \text{ k}\Omega}{4 \text{ k}\Omega + 12 \text{ k}\Omega} \cdot 24 \text{ mA} = 6 \text{ mA}$$

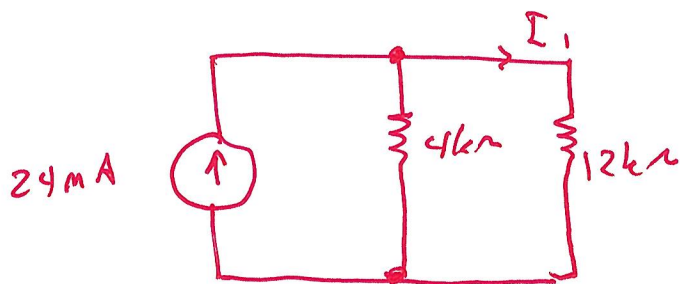
$$V_o = (6 \text{ k}\Omega) (6 \text{ mA}) = 36 \text{ V}$$



$$I_1 = \frac{4}{4 + 12} \cdot 24 \text{ mA} = 6 \text{ mA}$$

EE 2240  
Problem #06

Determine the value of  $V_x$ .

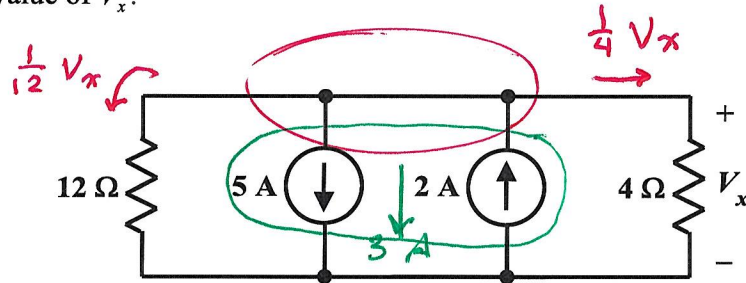


$$\frac{1}{12} V_x + 5 - 2 + \frac{1}{4} V_x = 0$$


$$\frac{1}{3} V_x = -3$$

$$V_x = -9V$$
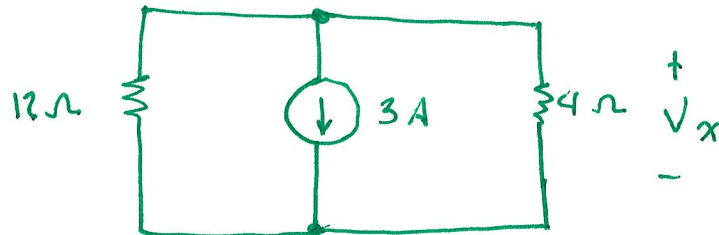
$$\frac{1}{12} V_x + 3 + \frac{1}{4} V_x = 0$$



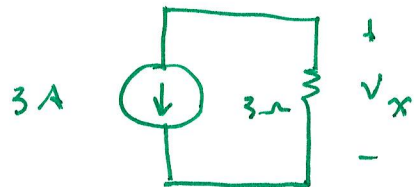
$$R_{eq} = \frac{4 \cdot 12}{4 + 12} = 3 \Omega$$



$$V_x = -(3 \Omega)(3A) = -9V$$

EE 2240  
**Problem #07**

Determine the value of  $V_x$ .

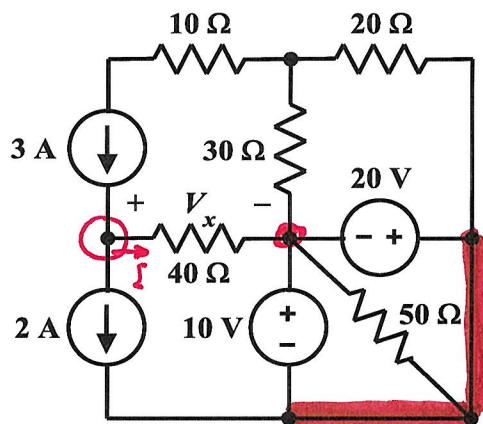

*Not  
 allowed!*




$$-3A + I + 2A = 0 \Rightarrow I = 1A$$

$$V_x = (40\Omega) I = 40V$$



EE 2240  
Problem #08


Find  $V_x$ .

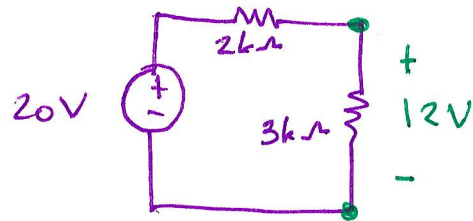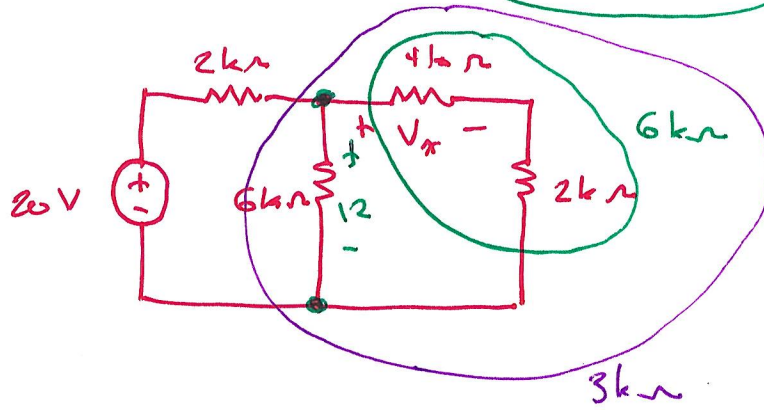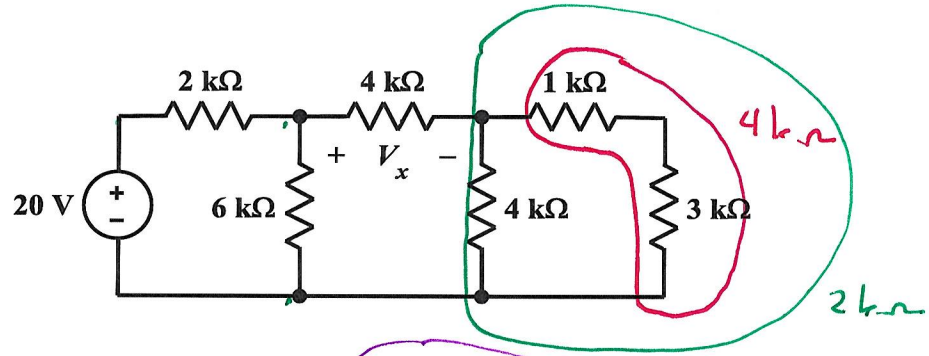

$$V_x = \frac{4k\Omega}{6k\Omega} 12V = 8V$$

EE 2240  
**Problem #09**

Determine the value of  $I_o$ .

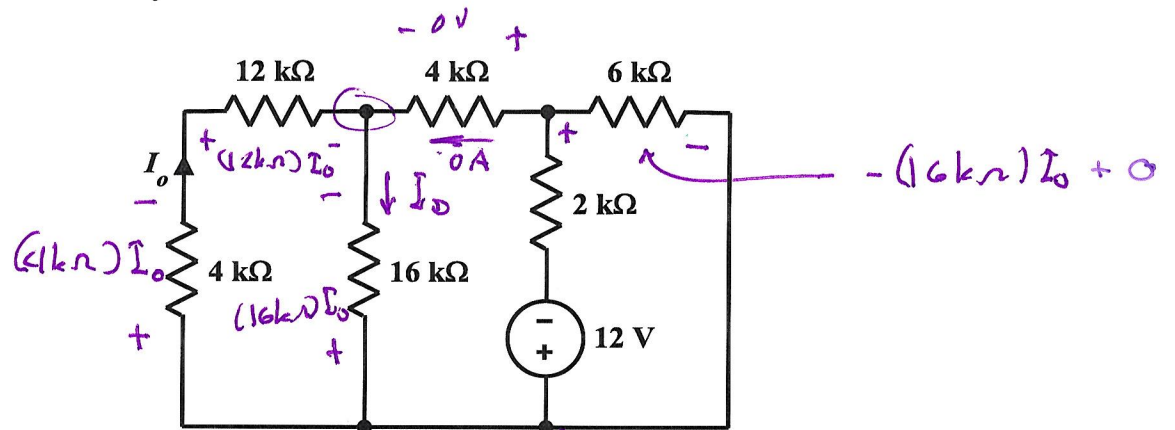

$$-(16k\Omega) I_o = \frac{6k\Omega}{8k\Omega} (-12)$$

$$= -9$$

$$I_o = \frac{9}{16k\Omega} \text{ A}$$

$$= \frac{9}{16} \text{ mA}$$