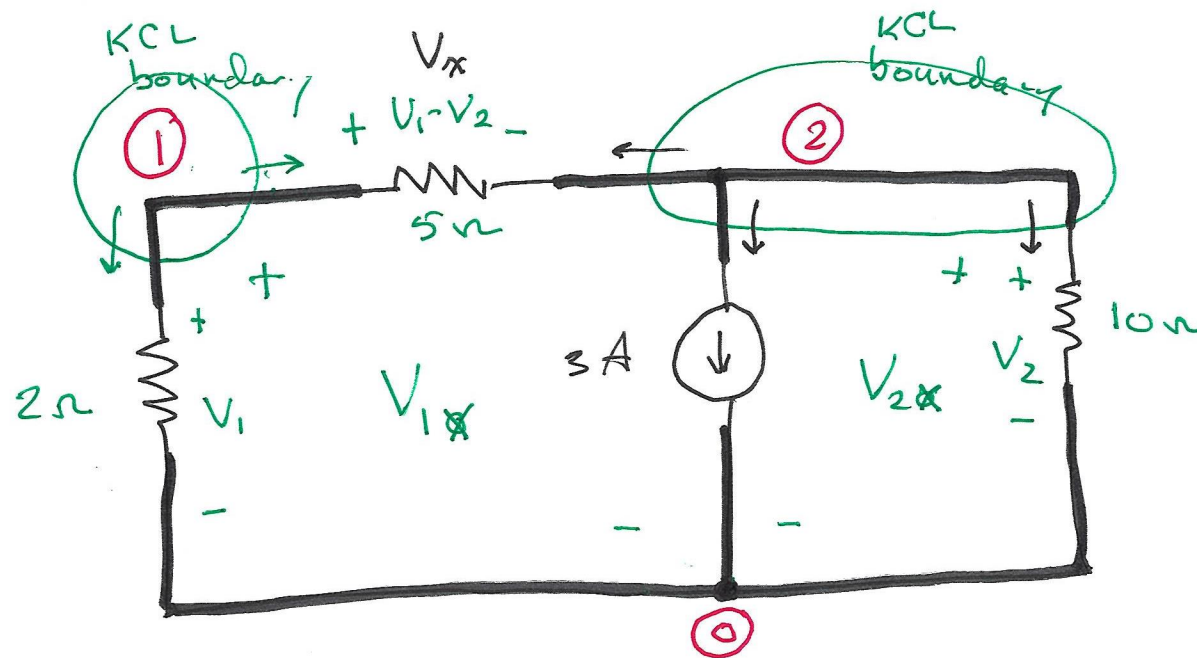


Nodal Analysis

Based on KCL.

Find all node voltages.



3 nodes

1. Choose a reference node and label it 0.

2

$$\text{At node 1: } + \frac{V_1 - V_2}{5} + \frac{V_1}{2} = 0$$


$$\text{At node 2: } \frac{V_2 - V_1}{5} + 3 + \frac{V_2}{10} = 0$$

In matrix form:

$$\begin{bmatrix} \frac{1}{5} + \frac{1}{2} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{1}{5} + \frac{1}{10} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0 \\ -3 \end{bmatrix}$$


Solving yields V_1 and V_2 .


$$\text{Then } V_x = V_1 - V_2$$

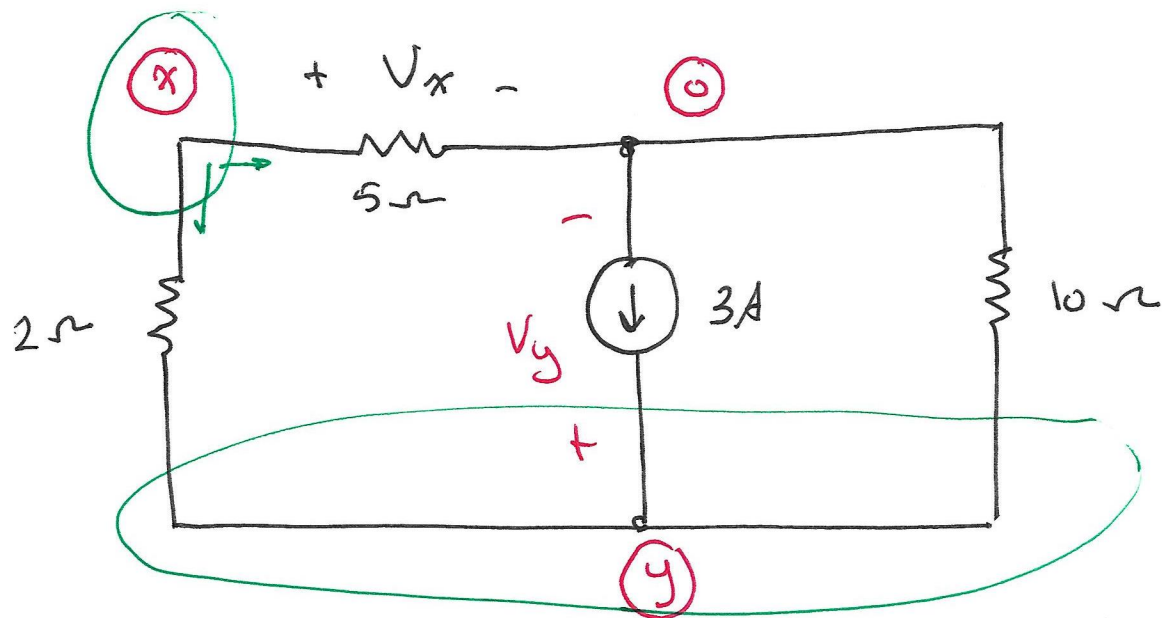

$$\frac{V_x}{5} + \frac{V_x - V_y}{2} = 0 \quad \text{at node } \textcircled{x}$$
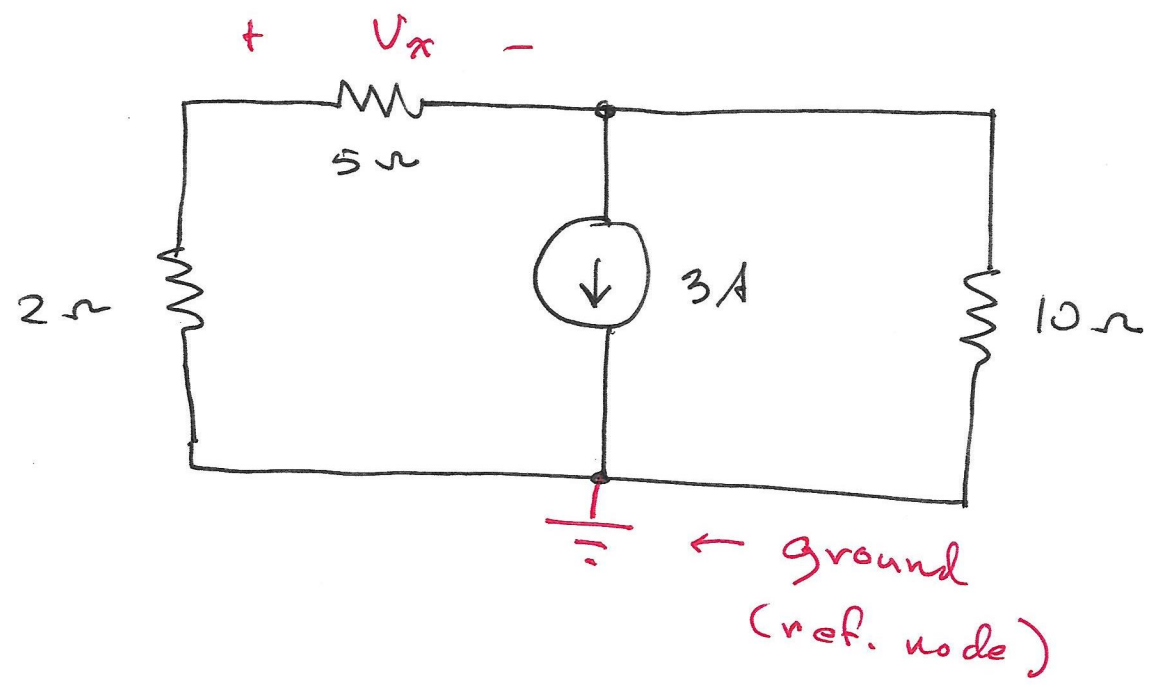
$$\frac{V_y - V_x}{2} - 3 + \frac{V_y}{10} = 0 \quad \text{at node } \textcircled{y}$$



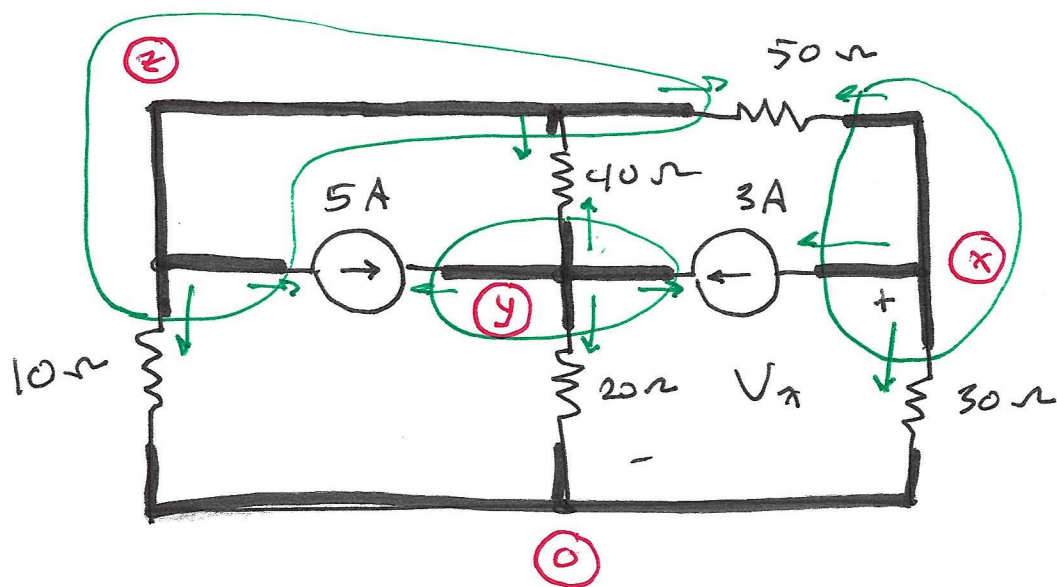

Write node eqns.
to solve for V_x .

3 nodes other than the ref. node
 \Rightarrow 3 node equations.

$$\frac{V_x}{30} + 3 + \frac{V_x - V_z}{50} = 0 \quad (\text{KCL at node } x)$$


$$\frac{V_y - V_z}{40} - 5 - 3 + \frac{V_y}{20} = 0 \quad (\text{KCL at node } y)$$

$$\frac{V_z}{10} + 5 + \frac{V_z - V_y}{40} + \frac{V_z - V_x}{50} = 0 \quad (\text{KCL at node } z)$$

In matrix form:

$$\begin{bmatrix} \frac{1}{30} + \frac{1}{50} & 0 & -\frac{1}{50} \\ 0 & \frac{1}{40} + \frac{1}{20} & -\frac{1}{40} \\ -\frac{1}{50} & -\frac{1}{40} & \frac{1}{10} + \frac{1}{40} + \frac{1}{50} \end{bmatrix} \begin{bmatrix} V_x \\ V_y \\ V_z \end{bmatrix} = \begin{bmatrix} -3 \\ 8 \\ -5 \end{bmatrix}$$

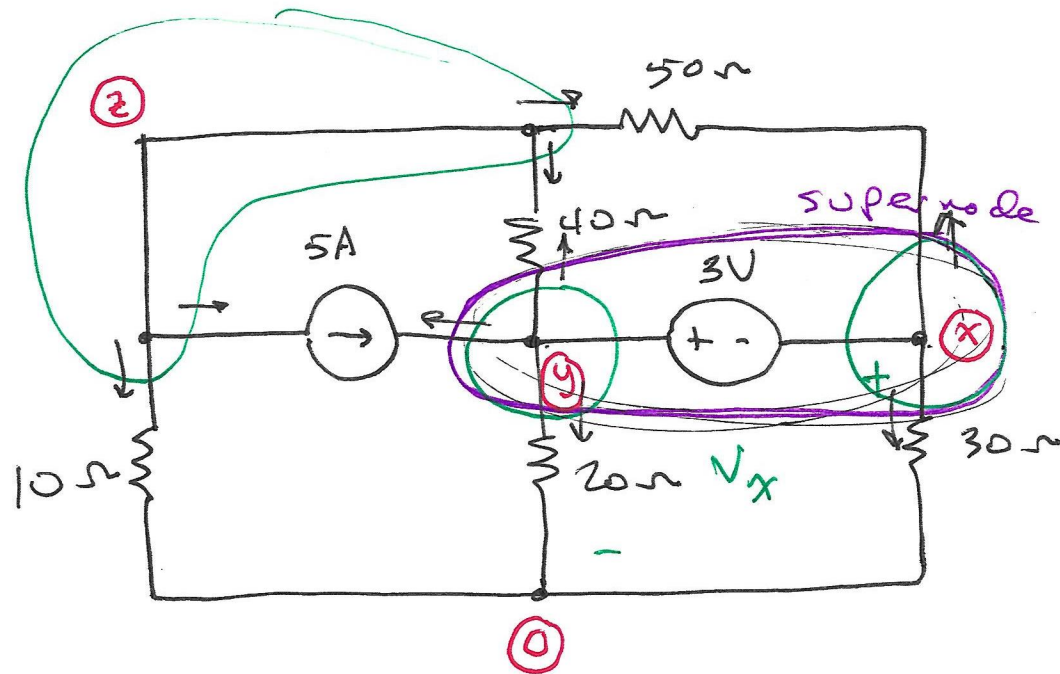What if the circuit contains a voltage source?




Solve for V_x
using the
nodal method.

$$V_y - V_x = 3 \quad (\text{constraint equation})$$

$$\frac{V_y - V_z}{40} - 5 + \frac{V_y}{20} + \frac{V_x}{30} + \frac{V_x - V_z}{50} = 0 \quad (\text{KCL for the supernode})$$
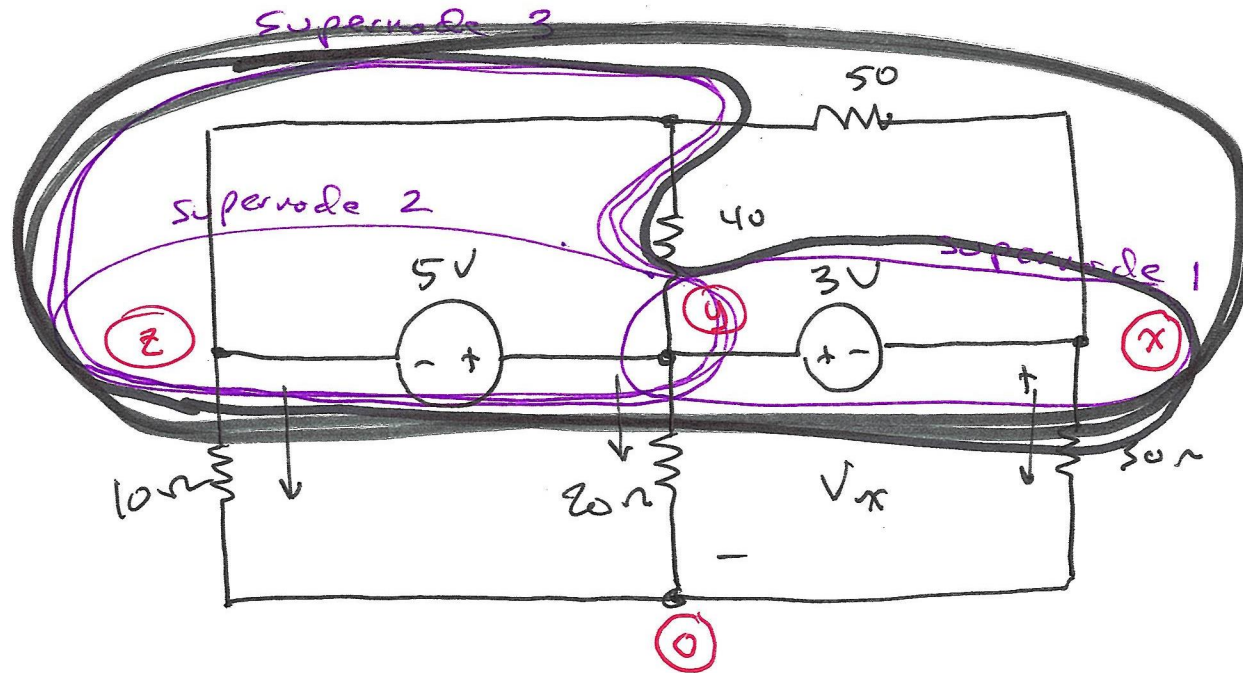
$$V_z - \frac{V_x}{50} + \frac{V_z - V_y}{40} + 5 + \frac{V_z}{10} = 0 \quad (\text{KCL for node } z)$$



$$V_y - V_x = 3 \quad (\text{Constraint eqn. for supernode 1})$$

$$V_y - V_z = 5 \quad (\text{Constraint eqn. for supernode 2})$$

$$\frac{V_x}{10} + \frac{V_y}{20} + \frac{V_x}{30} = 0 \quad (\text{KCL for merged supernode 3})$$

$$\begin{array}{l} \text{eqn 1} \\ \text{eqn 2} \\ \text{eqn 3} \end{array} \begin{bmatrix} v_x & v_y & v_z \\ -1 & 1 & 0 \\ 0 & 1 & -1 \\ \frac{1}{30} & \frac{1}{20} & \frac{1}{10} \end{bmatrix} \begin{bmatrix} v_x \\ v_y \\ v_z \end{bmatrix} = \begin{bmatrix} 3 \\ 5 \\ 0 \end{bmatrix}$$

Exam # 1 available Sept. 23

due by 9:15 AM Sept. 28

Open book, open notes, computer, calculator,

No class meeting on Sept. 28