
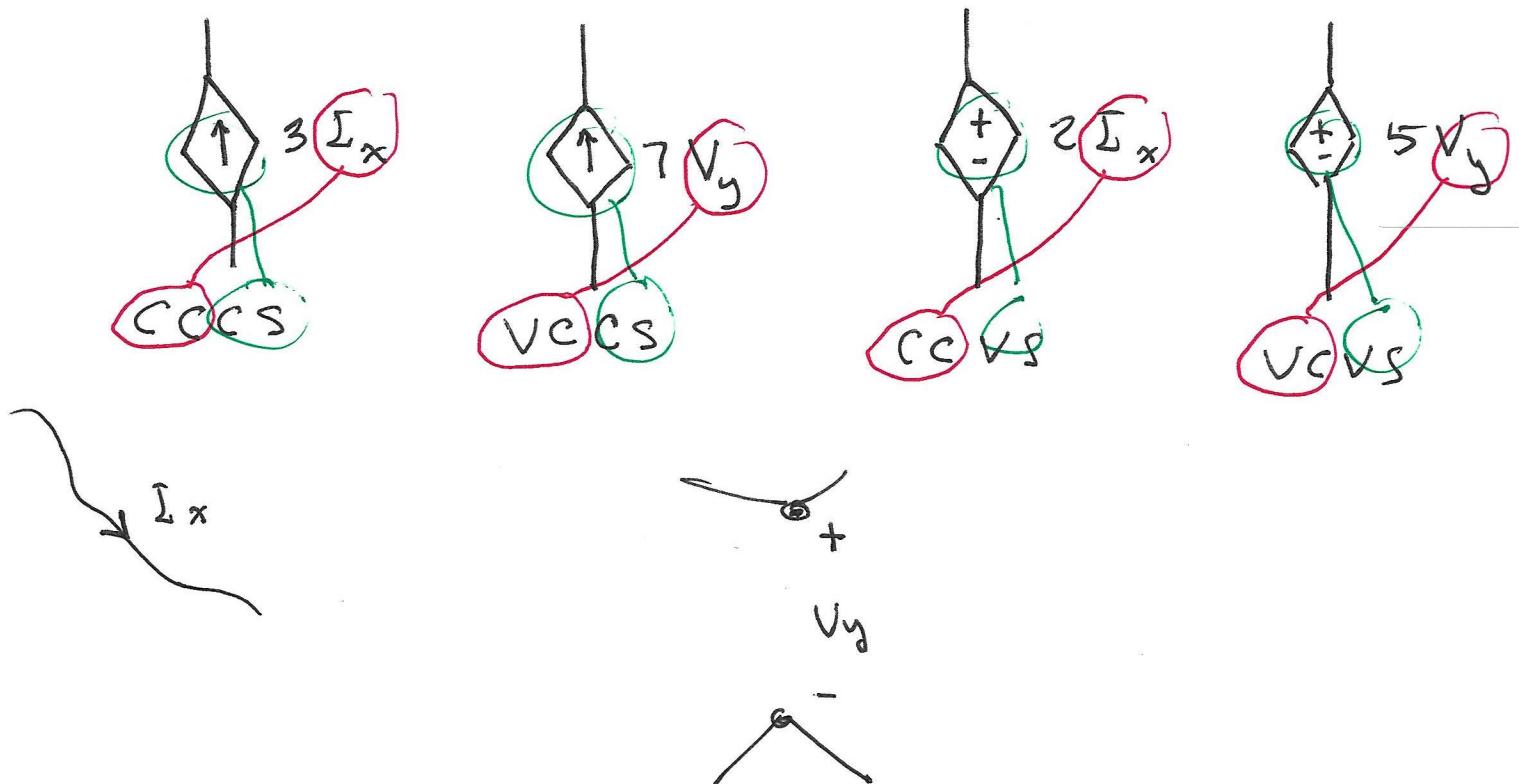


Dependent Source (Controlled)

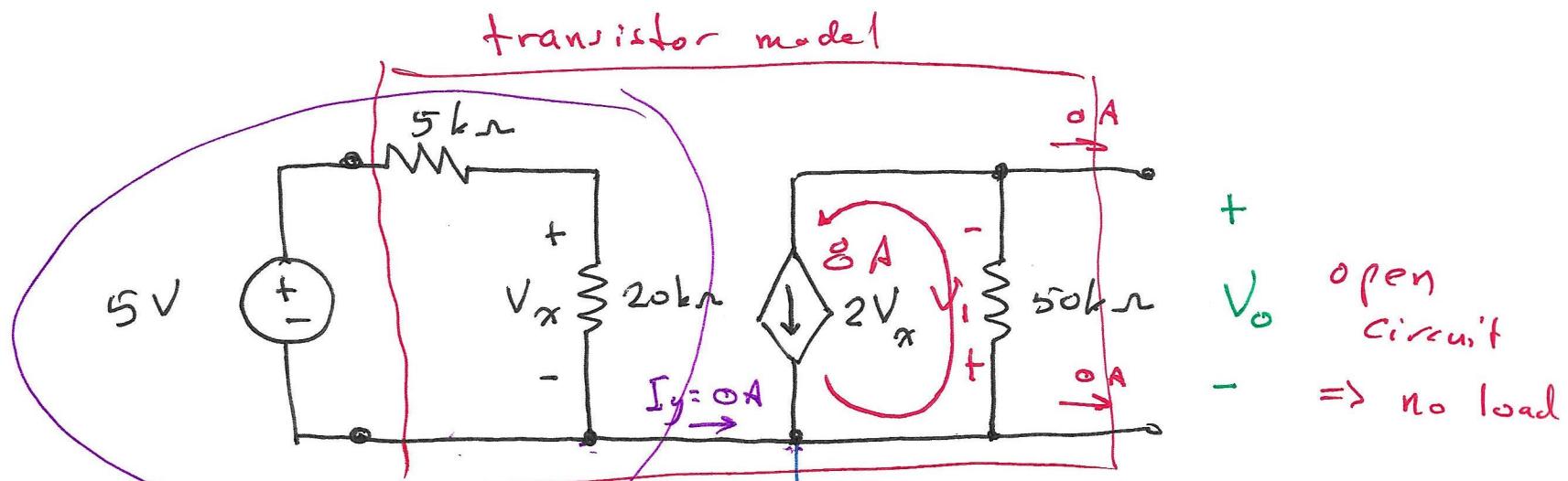Value of the output is determined by
a variable somewhere else in the circuit.





only one wire crosses
this KCL boundary

$$\Rightarrow I_g = 0$$


From the L.H.S.:

$$V_x = \frac{20k\Omega}{5k\Omega + 20k\Omega} \cdot 5V = 4V$$

From the R.H.S.:

$$V_i = (8A)(50k\Omega) = 400kV \text{ or } 4 \times 10^5 V$$

$$V_o = -V_i = -400kV$$

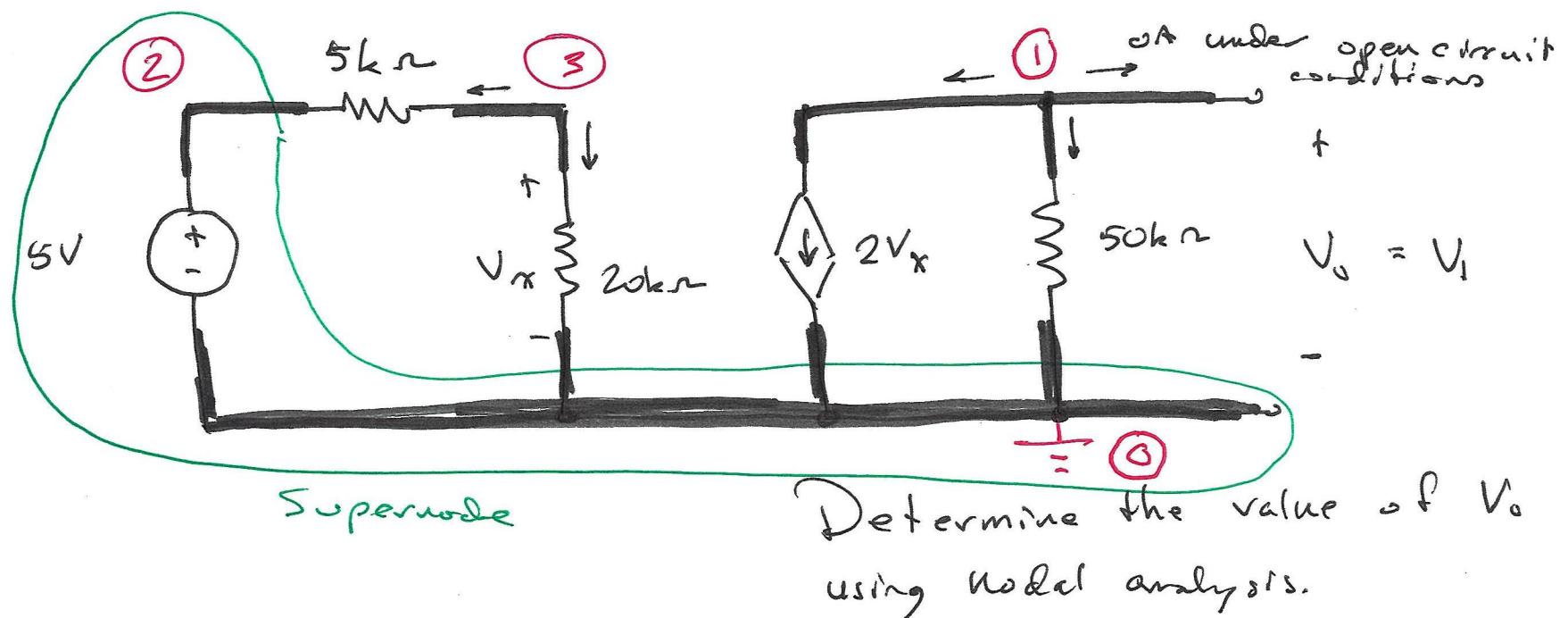

$V_2 = 5V$ (constraint eqn. for the supernode)

$$\frac{V_3 - V_2}{5k\Omega} + \frac{V_3}{20k\Omega} = 0 \quad (\text{KCL for node 3})$$


$$2V_x + \frac{V_1}{50k\Omega} + 0 = 0 \quad (\text{KCL for node 1})$$

$$V_x = V_3 \quad (\text{Definition of } V_x \text{ in terms of node voltages})$$

$$V_o = V_1 \quad (\text{Definition of } V_o \text{ in terms of node voltages})$$

In Matrix form:

$$\begin{array}{l}
 \text{eqn 1} \\
 \text{eqn 2} \\
 \text{eqn 3} \\
 \text{eqn 4} \\
 \text{eqn 5}
 \end{array}
 \left[\begin{array}{cccccc}
 v_1 & v_2 & v_3 & v_0 & v_x & 0 \\
 0 & 1 & 0 & 0 & 0 & 0 \\
 0 & -\frac{1}{5000} & \frac{1}{5000} + \frac{1}{20000} & 0 & 0 & 0 \\
 \frac{1}{50000} & 0 & 0 & 0 & 2 & v_1 \\
 0 & 0 & -1 & 0 & 1 & v_2 \\
 -1 & 0 & 0 & 1 & 0 & v_3 \\
 \end{array} \right] = \left[\begin{array}{c}
 v_1 \\
 v_2 \\
 v_3 \\
 v_0 \\
 v_x \\
 5 \\
 0 \\
 6 \\
 0 \\
 0
 \end{array} \right]$$

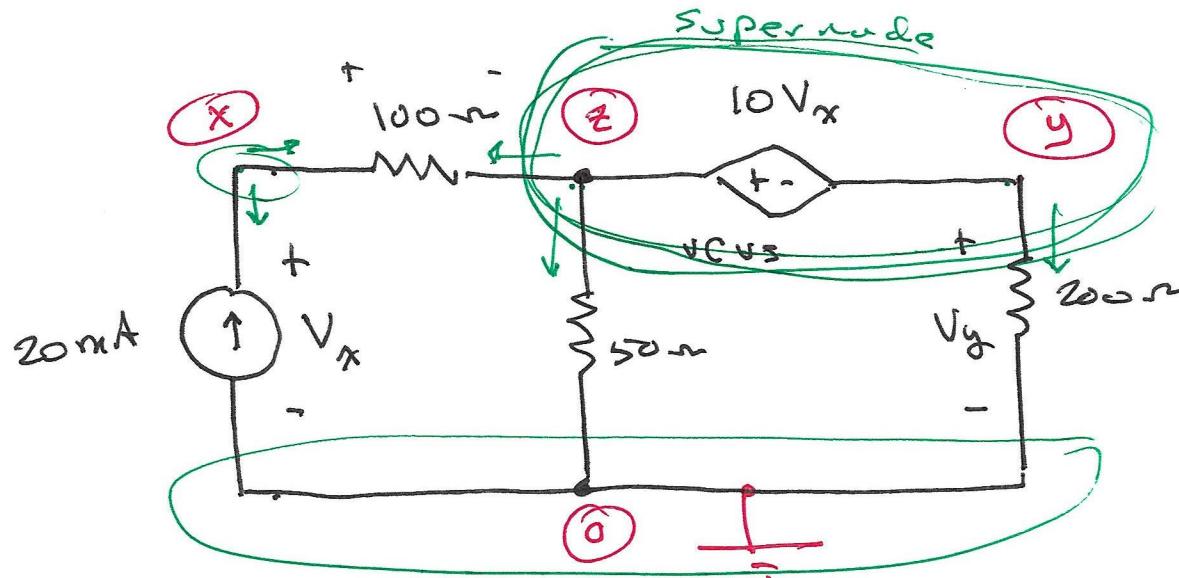

Set up node eqns.
required to solve
for V_y .

$$V_z - V_y = 10 V_x \quad (\text{constraint eqn. for the VCVS})$$


supernode

$$\frac{V_x - V_z}{100} - 20\text{mA} = 0 \quad (\text{KCL for node } x)$$

$$\frac{V_z - V_x}{100} + \frac{V_z}{50} + \frac{V_y}{200} = 0 \quad (\text{KCL for the supernode})$$

In matrix form:
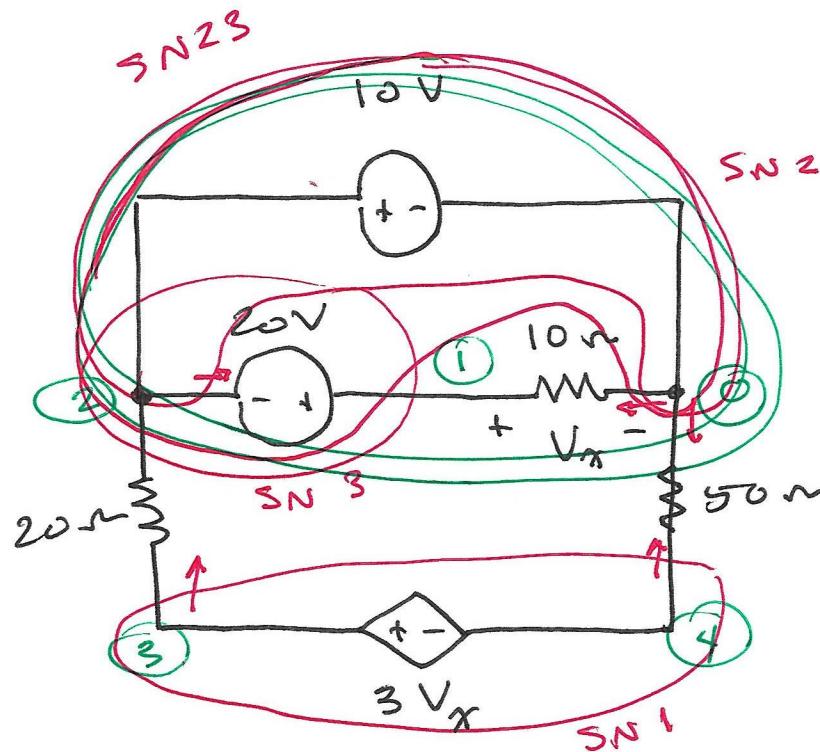
$$\begin{bmatrix} -10 & -1 & 1 \\ \frac{1}{100} & 0 & -\frac{1}{100} \\ -\frac{1}{100} & \frac{1}{200} & \frac{1}{100} + \frac{1}{50} \end{bmatrix} \begin{bmatrix} V_x \\ V_y \\ V_z \end{bmatrix} = \begin{bmatrix} 0 \\ 20 \times 10^{-3} \\ 0 \end{bmatrix}$$



For $SN1$: $\frac{V_3 - V_2}{20} + \frac{V_4}{50} = 0$ (KCL)

For $SN1$: $V_3 - V_4 = 3V_x$ (constraint)

For $SN2$: $V_2 = 10$ (constraint)

For $SN3$: $V_1 - V_2 = 20$ (constraint)

combine $SN2$ and $SN3$ because they have node 2 in common

Definition: $V_x = V_1$