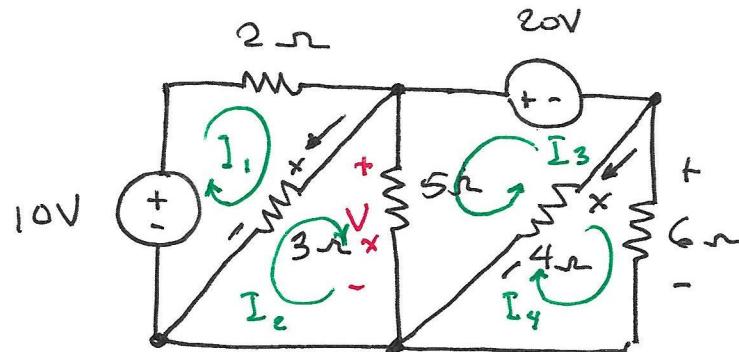


Mesh Analysis

KVL



a. Write mesh equations.

b. Solve the equations.

c. Determine V_x .

For mesh 1:

$$-10V + 2I_1 + 3(I_1 - I_2) = 0$$

For mesh 2:

$$-3(I_1 - I_2) + 5(I_2 + I_3) = 0$$

For mesh 3:

$$-5(I_2 + I_3) + 20V - 4(I_3 + I_4) = 0$$

For mesh 4:

$$4(I_3 + I_4) + 6I_4 = 0$$

$$V_x = 5(I_2 + I_3)$$

$$\left[\begin{array}{ccccc} 2+3 & -3 & 0 & 0 & 0 \\ -3 & 3+5 & 5 & 0 & 0 \\ 0 & -5 & -5-4 & -4 & 0 \\ 0 & 0 & 4 & 4+6 & 0 \\ 0 & 5 & 5 & 0 & -1 \end{array} \right] \left[\begin{array}{c} I_1 \\ I_2 \\ I_3 \\ I_4 \\ V_x \end{array} \right] = \left[\begin{array}{c} 10 \\ 0 \\ -20 \\ 0 \\ 0 \end{array} \right]$$

A b c

$$\gg A = [2+3 \ -3 \ 0 \ 0 \ 0; -3 \ 3+5 \ 5 \ 0 \ 0;$$

$$0 \ -5 \ -5-4 \ -4 \ 0; 0 \ 0 \ 4 \ 4+6 \ 0;$$

$$0 \ 5 \ 5 \ 0 \ -1]$$

3

$$A = \begin{bmatrix} 5 & -3 & 0 & 0 & 0 \\ -3 & 8 & 5 & 0 & 0 \\ 0 & -5 & -9 & -4 & 0 \\ 0 & 0 & 4 & 10 & 0 \\ 0 & 5 & 5 & 0 & -1 \end{bmatrix}$$

$$\gg c = [10; 0; -20; 0; 0]$$

OR

$$c = [10 \ 0 \ -20 \ 0 \ 0]'$$

$$c = \begin{bmatrix} 10 \\ 0 \\ -20 \\ 0 \\ 0 \end{bmatrix}$$

>> $b = \text{inv}(a) * c$


$$b = \begin{matrix} \\ \\ \\ \end{matrix}$$

Or

$$b = A \setminus c$$

>> $A * b$
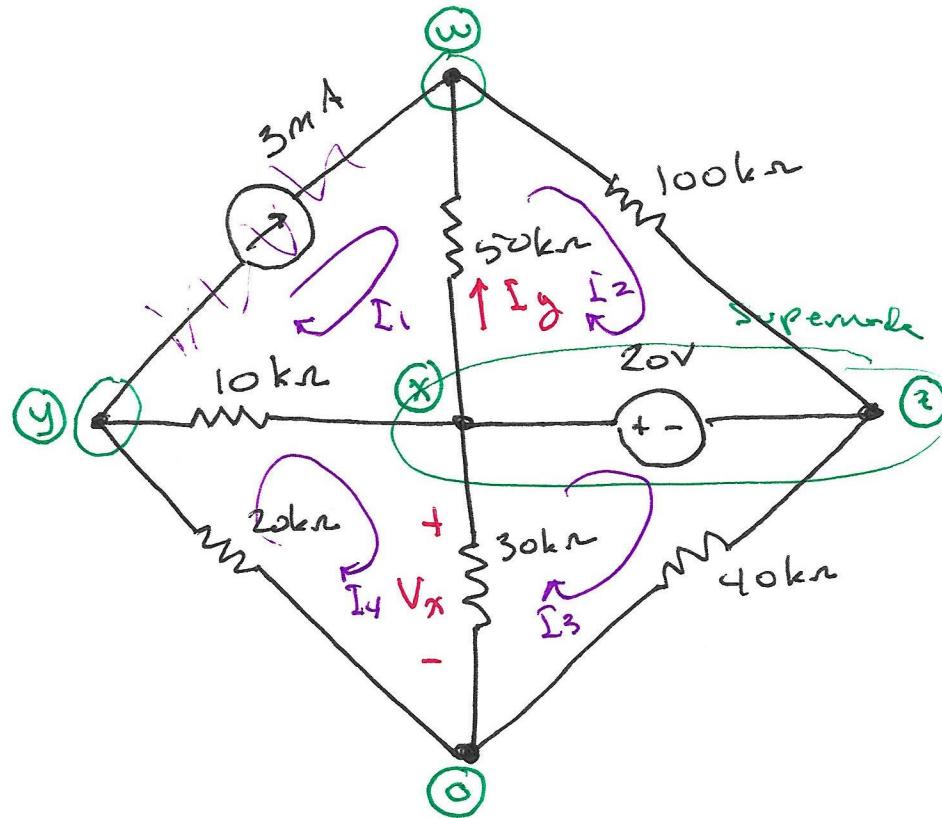
$$\text{ans} = \begin{matrix} c_1 \\ c_2 \\ c_3 \\ c_4 \\ c_5 \end{matrix}$$



5 eqns for nodal analysis to completely solve.

6 eqns for mesh analysis to completely solve.

Nodal Analysis Approach

$$V_x - V_z = 20 \quad (\text{constraint})$$

$$3 \times 10^{-3} + \frac{V_y - V_x}{10 \times 10^3} + \frac{V_y}{20 \times 10^3} = 0 \quad (\text{KCL at node } y)$$

$$3 \times 10^{-3} + \frac{V_x - V_w}{50 \times 10^3} + \frac{V_z - V_w}{100 \times 10^3} = 0 \quad (\text{KCL at node } w)$$

$$\frac{V_z - V_w}{100 \times 10^3} + \frac{V_x - V_w}{50 \times 10^3} + \frac{V_x - V_y}{10 \times 10^3} + \frac{V_x}{30 \times 10^3} + \frac{V_z}{40 \times 10^3} = 0$$

$$I_y = \frac{V_x - V_w}{50 \times 10^3} \quad (\text{definition of } I_y) \quad (\text{KCL at supernode})$$

Mesh Analysis Approach

$$I_1 = 3 \times 10^{-3} \quad (\text{constraint})$$

$$100 \times 10^3 \Sigma_2 - 20 + 50 \times 10^3 (\Sigma_2 - \Sigma_1) = 0 \quad (\text{KVL for mesh 2})$$

$$20 + 40 \times 10^3 \Sigma_3 + 30 \times 10^3 (\Sigma_3 - \Sigma_4) = 0 \quad (\text{KVL for mesh 3})$$

$$10 \times 10^3 (\Sigma_4 - \Sigma_1) + 30 \times 10^3 (\Sigma_4 - \Sigma_3) + 20 \times 10^3 \Sigma_4 = 0 \quad (\text{KVL for mesh 4})$$


$$\Sigma_y = I_2 - \Sigma_1 \quad (\text{definition of } \Sigma_y)$$

$$V_x = 30 \times 10^3 (\Sigma_4 - \Sigma_3) \quad (\text{definition of } V_x)$$

LTspice

Simulation Program with Integrated Circuit Emphasis
~~Linear Technology~~ Analog Devices

8

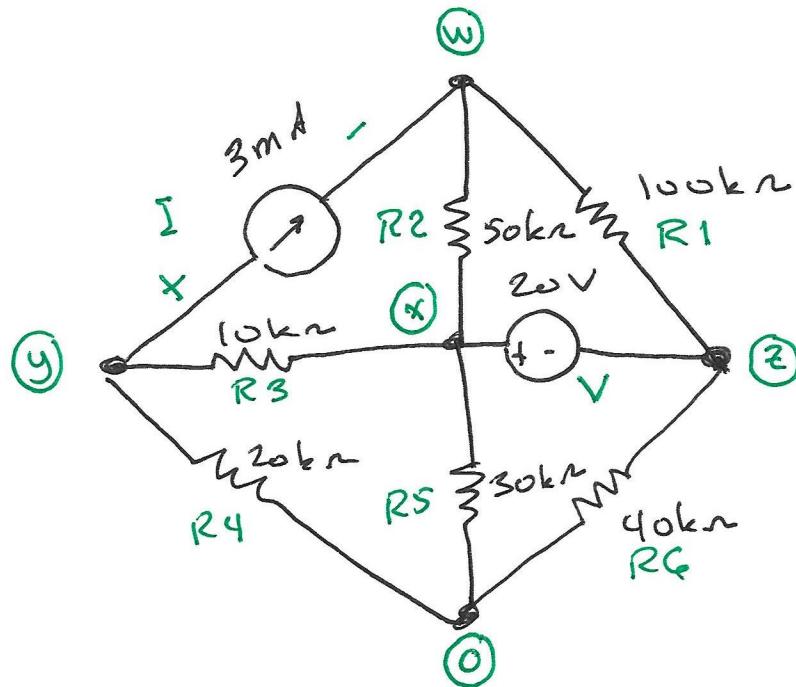

Spice assumes every component satisfies the passive sign convention.

.003

3×10^{-3}



$M_{EG} = 10^6$

I	y	w	DC	3m
R2	w	x	50k	
R1	w	z	100k	
R3	y	x	10k	
V	x	z	DC	20
R4	y	o	20k	
R5	x	o	30k	
R6	z	o	40k	
OP				