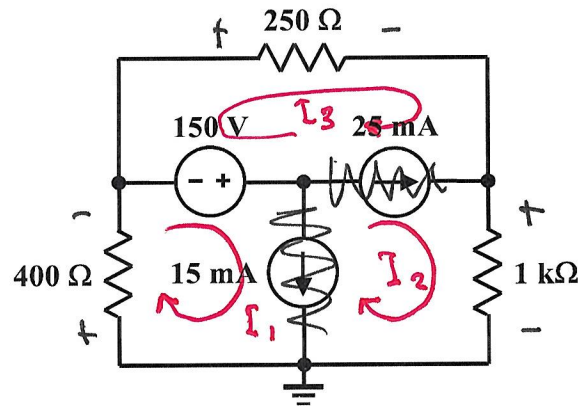


EE 2240
Homework Problem #028

Define mesh currents and express the mesh equations in the matrix form discussed in class.



Do not attempt to solve the equations.


$$I_2 - I_3 = 25 \text{ mA}$$

$$I_1 - I_2 = 15 \text{ mA}$$

$$250 I_3 + 1000 I_2 + 400 I_1 = 0$$

In matrix form:
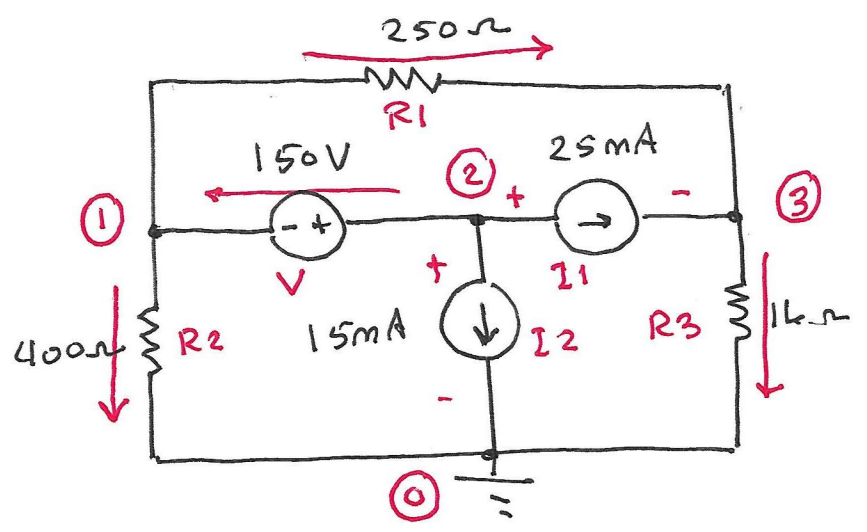
$$\begin{bmatrix} 0 & 1 & -1 \\ 1 & -1 & 0 \\ 400 & 1000 & 250 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 25 \times 10^{-3} \\ 15 \times 10^{-3} \\ 0 \end{bmatrix}$$




Netlist

Title ←


R1	1	3	250
V	2	1	DC 150
I1	2	3	DC 25m
R2	1	0	400
I2	2	0	DC 15m
R3	3	0	1k

.op

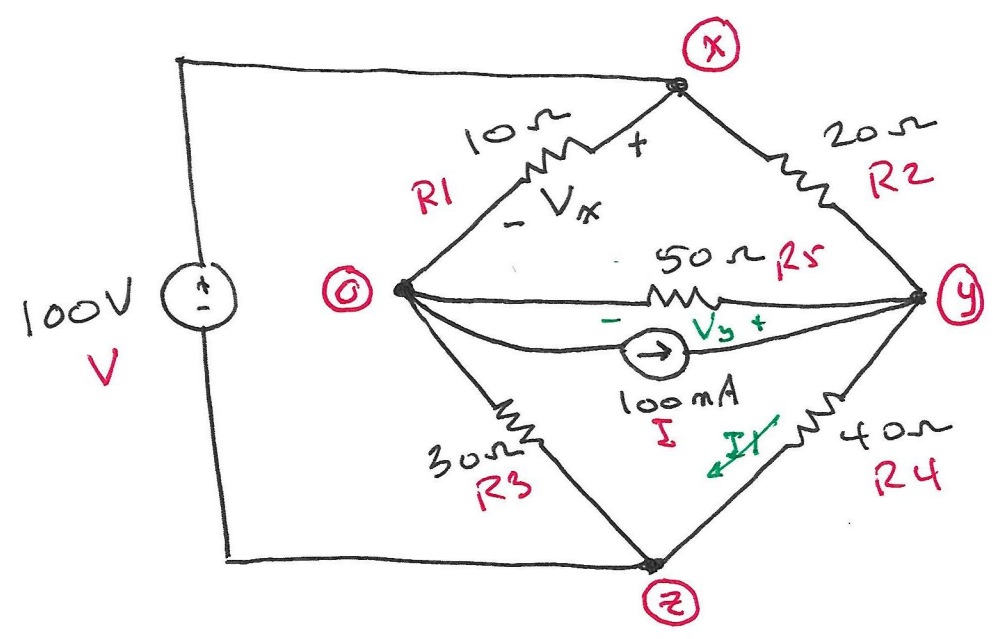.end ← LTSpice puts this in automatically




Linearity and Proportionality

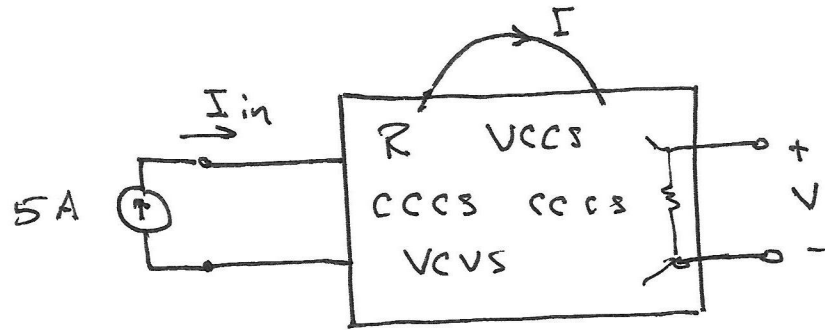



With $I_{in} = 5A$, $I = 4mA$ and $V = 6V$.

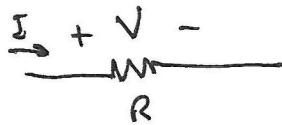What would I and V be if I_{in} is changed to $10A$?



$$V = RI$$

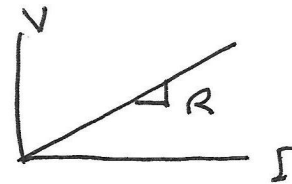

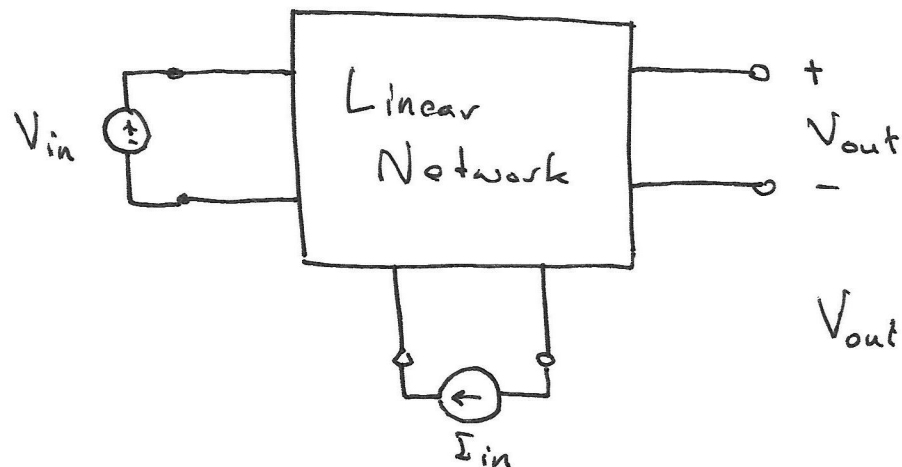

$$V_{out} = \alpha V_{in} + \beta I_{in}$$

When $V_{in} = 10V$ and $I_{in} = 5mA$, $V_{out} = 7V$ } experimental data
 When $V_{in} = 20V$ and $I_{in} = 3mA$, $V_{out} = 5V$ }

Determine α and β , and then calculate V_{out}
 when $V_{in} = 15V$ and $I_{in} = 4mA$.

$$10\alpha + 5 \times 10^{-3} \beta = 7$$

$$20\alpha + 3 \times 10^{-3} \beta = 5$$

In matrix form:

$$\begin{bmatrix} 10 & 5 \times 10^{-3} \\ 20 & 3 \times 10^{-3} \end{bmatrix} \begin{bmatrix} \alpha \\ \beta \end{bmatrix} = \begin{bmatrix} 7 \\ 5 \end{bmatrix}$$

$$\alpha = ? \quad \beta = ?$$

Superposition next.