


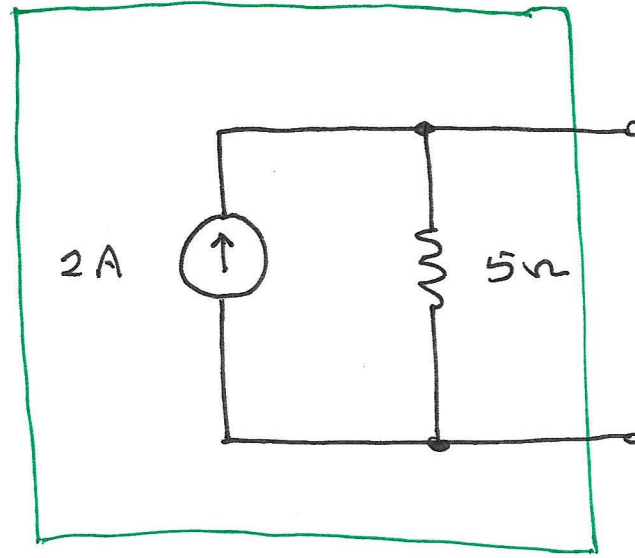
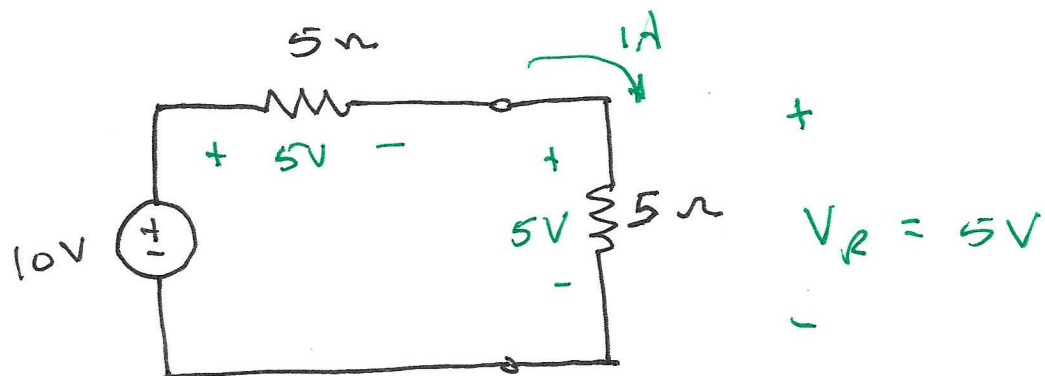
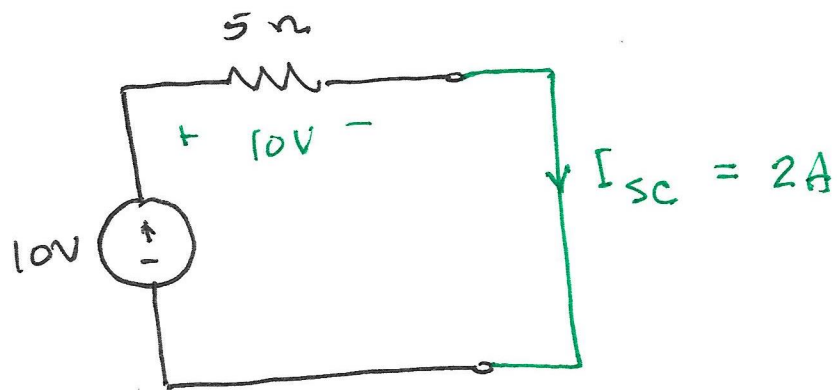
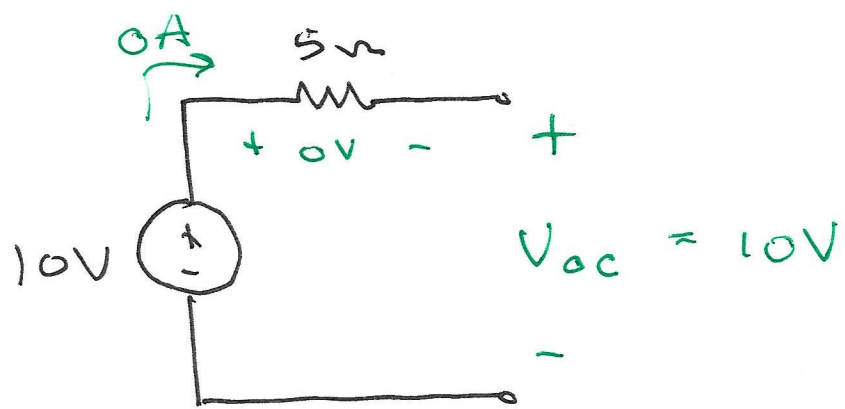




Circuit A

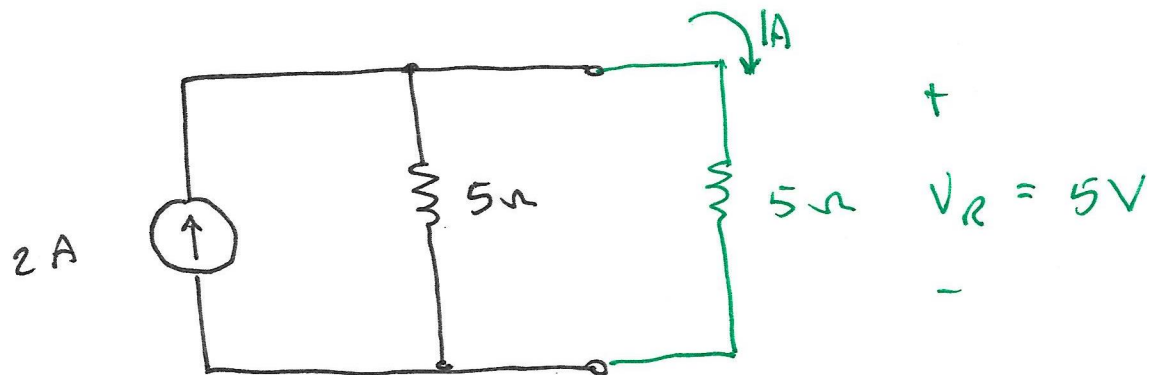



Circuit B

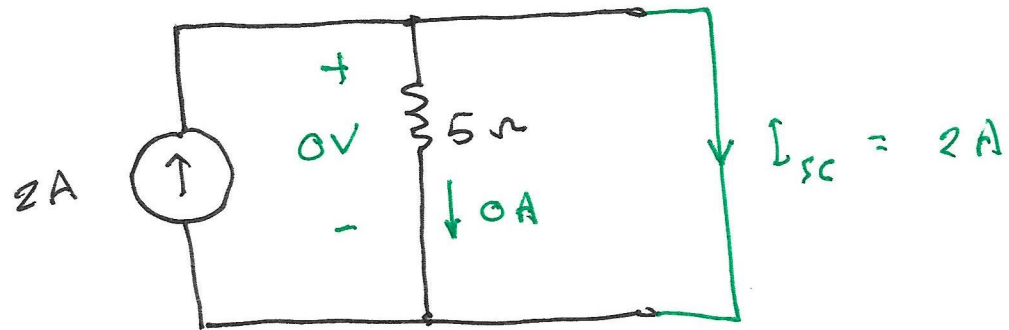


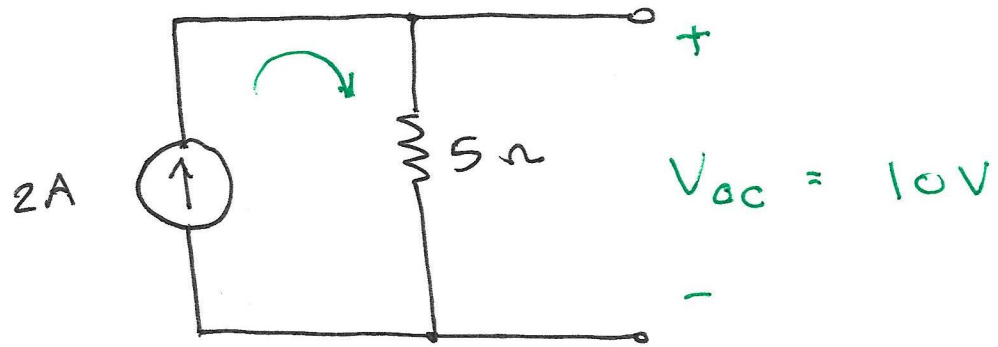


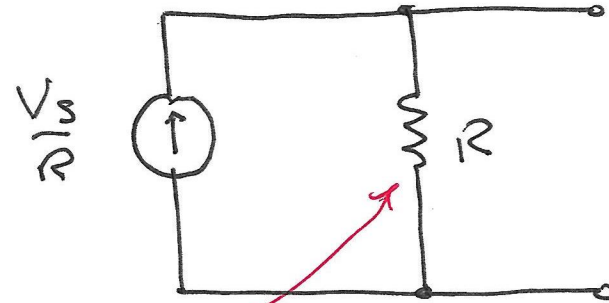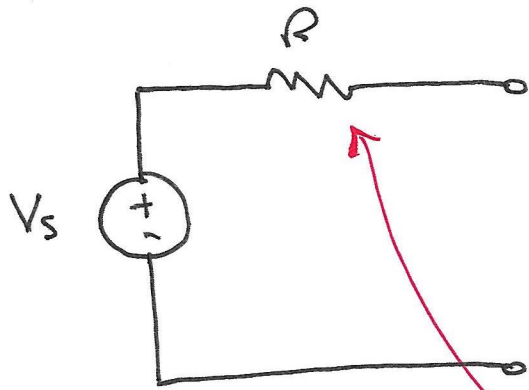


Same value

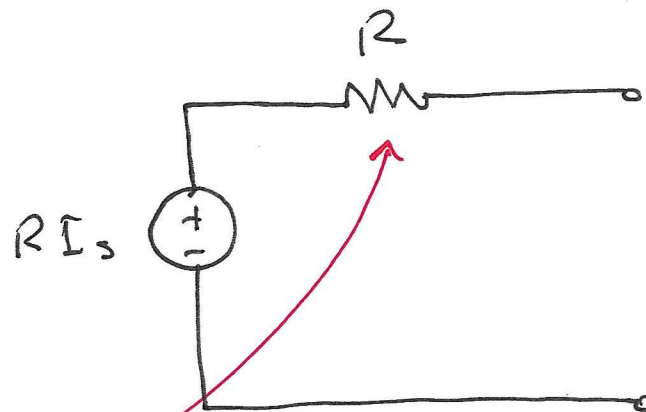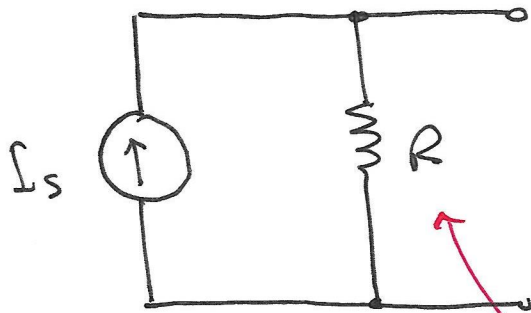


Same value

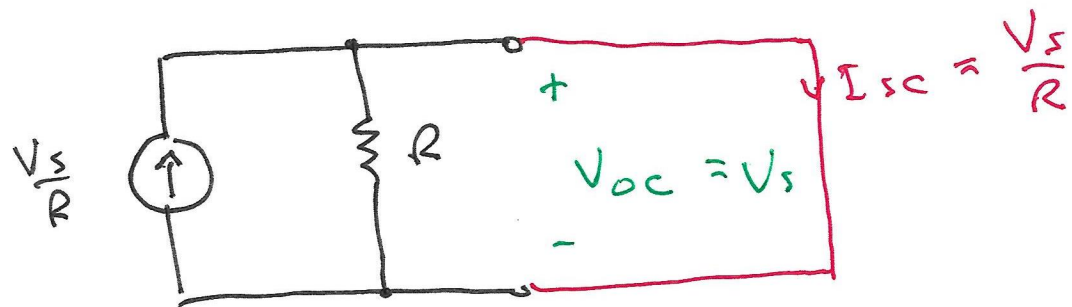
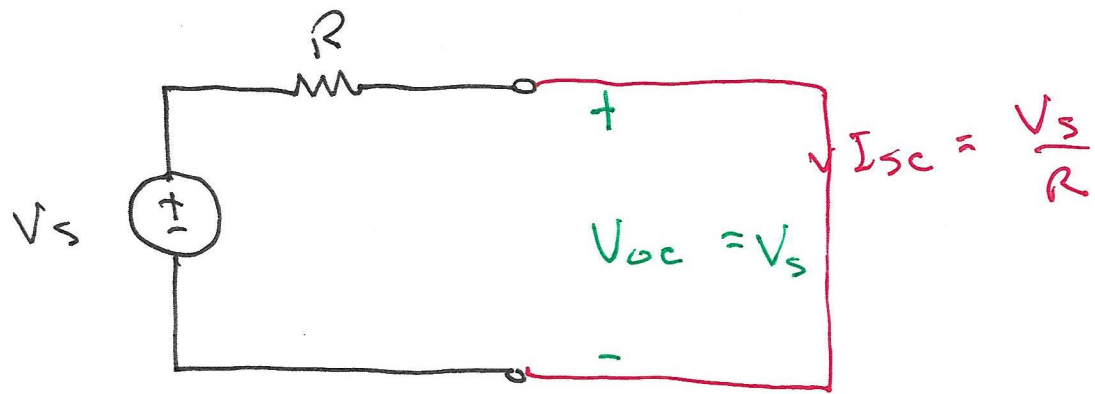





Source Transformation

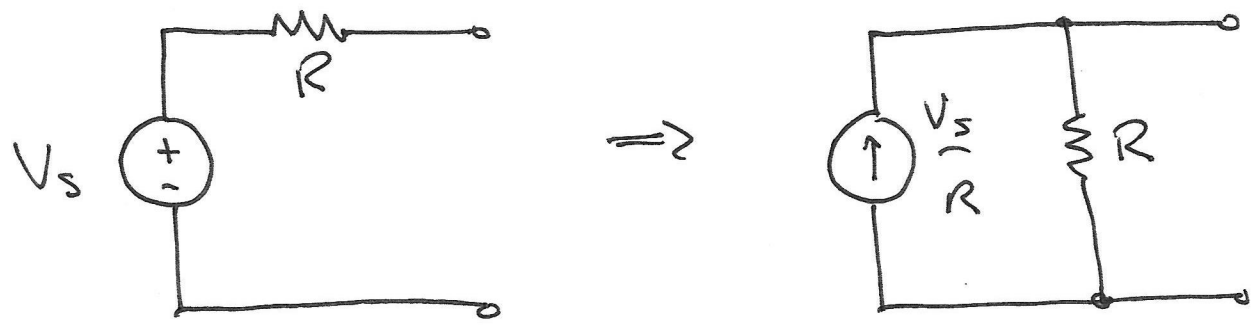

or

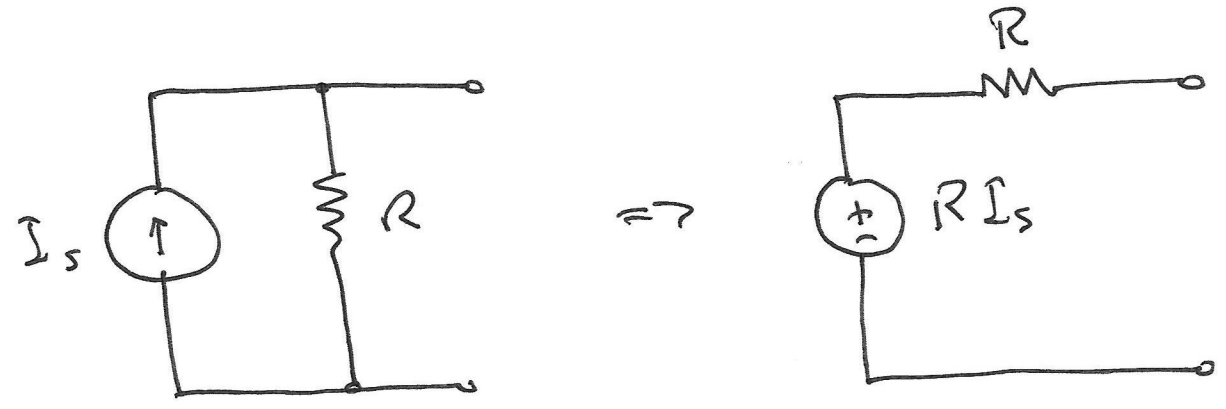

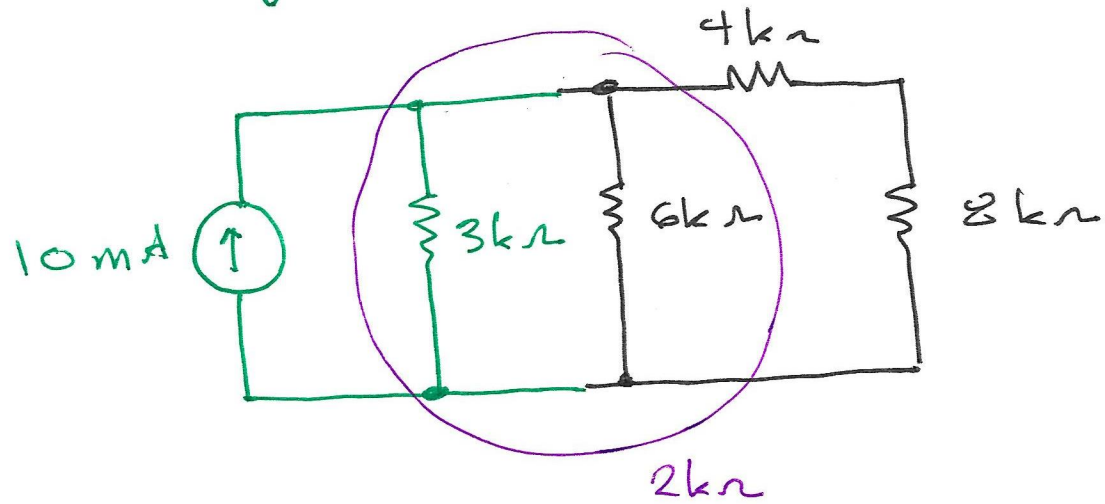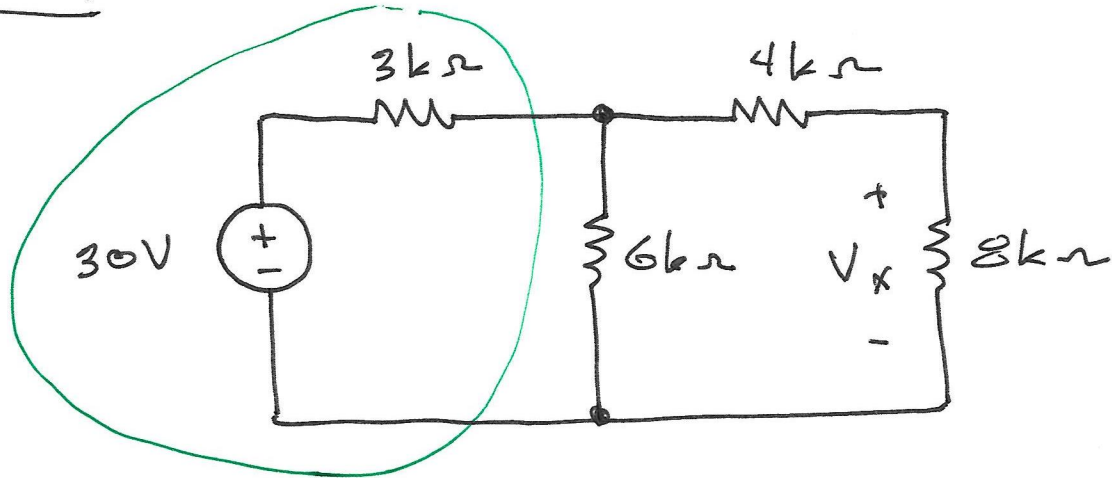Example

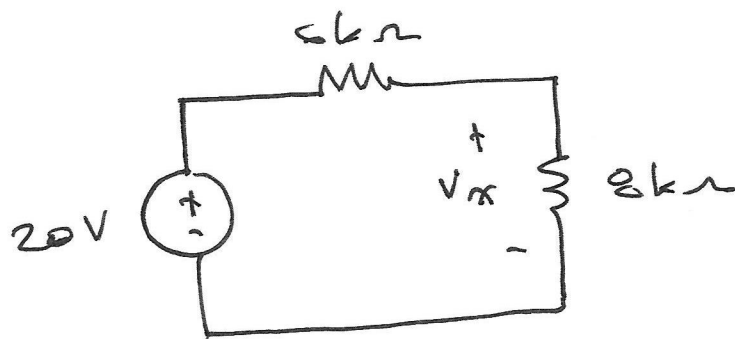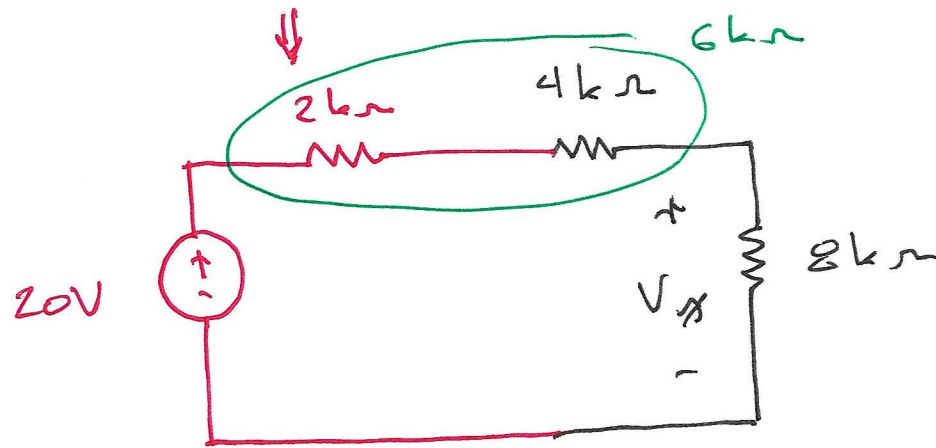
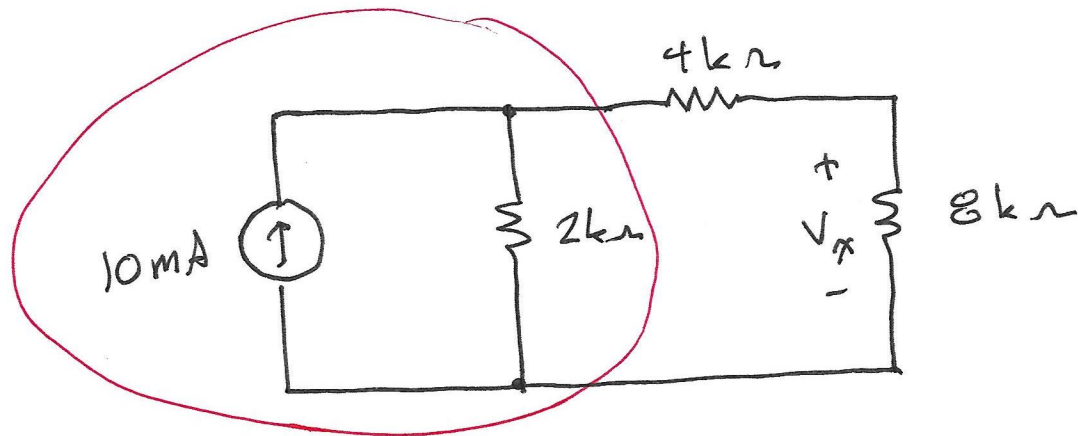


$$V_x = \frac{8}{6+8} \cdot 20$$


$$= \frac{160}{14}$$

$$= \frac{100}{9} \text{ V}$$

Thévenin's Theorem

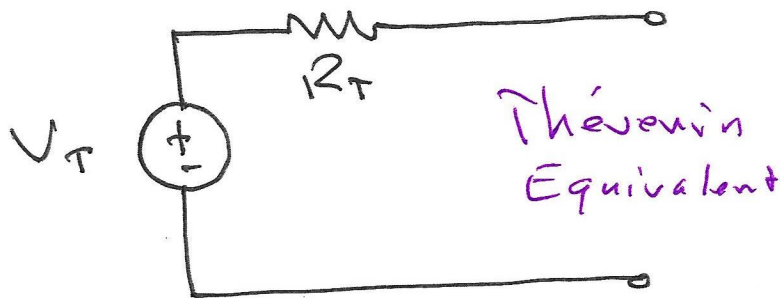
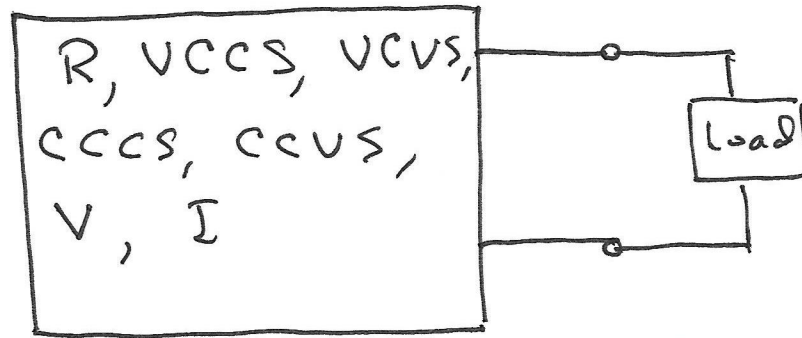




Norton's Theorem⁹

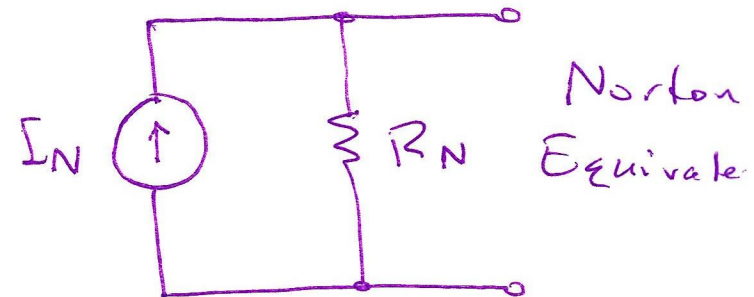

$$R_N = R_T$$
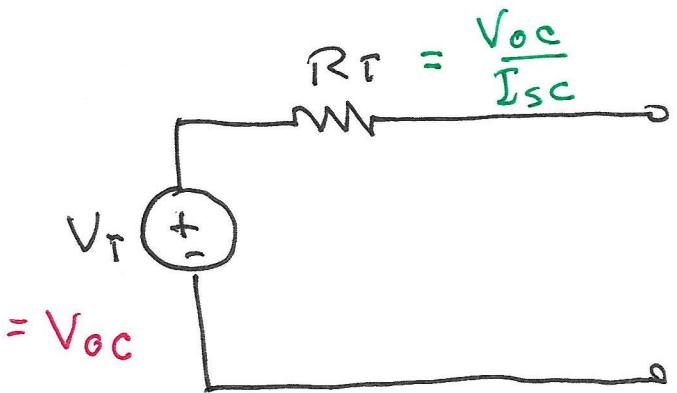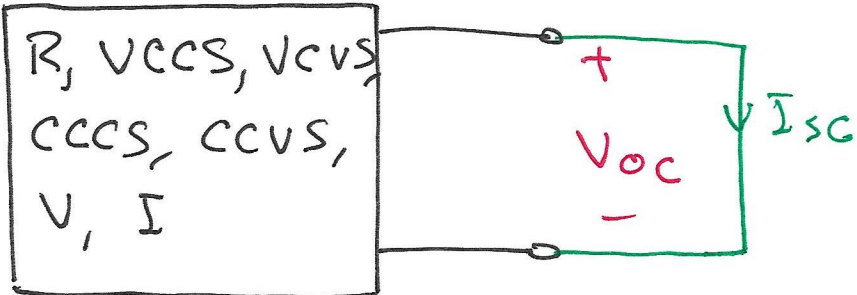
$$V_T = R_N I_N \quad \text{or} \quad I_N = \frac{V_T}{R_T}$$




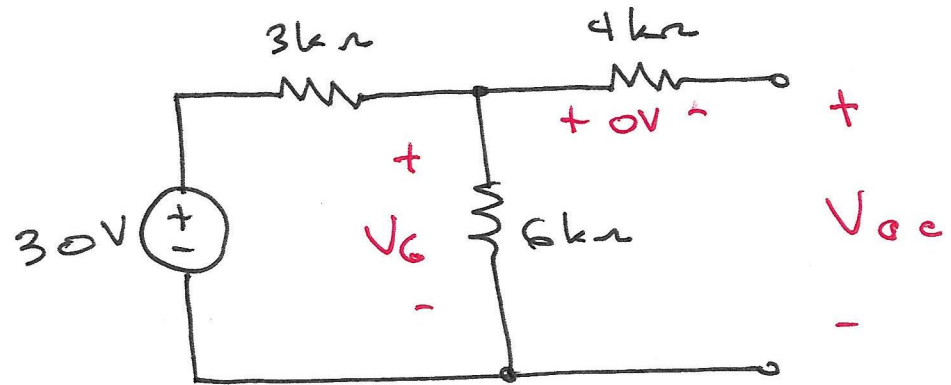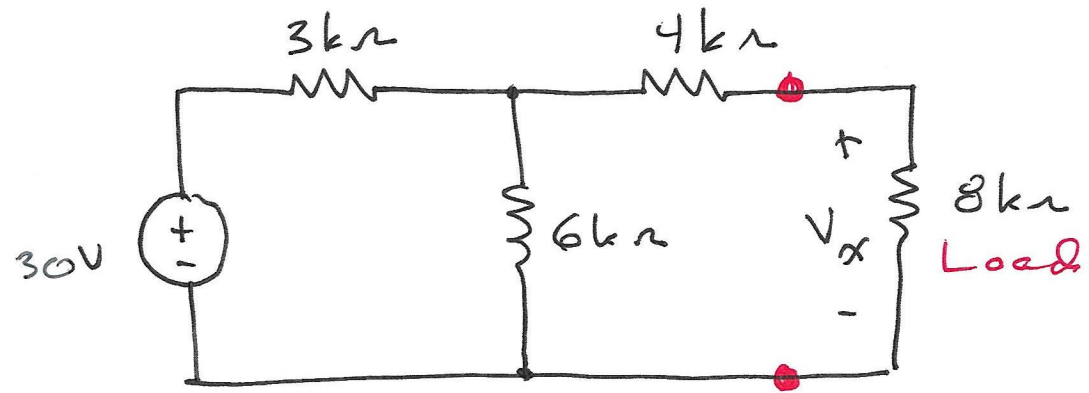

$$V_6 = \frac{6}{3+6} \cdot 30V$$

$$= 20V$$

$$V_{oc} = V_6 = 20V$$

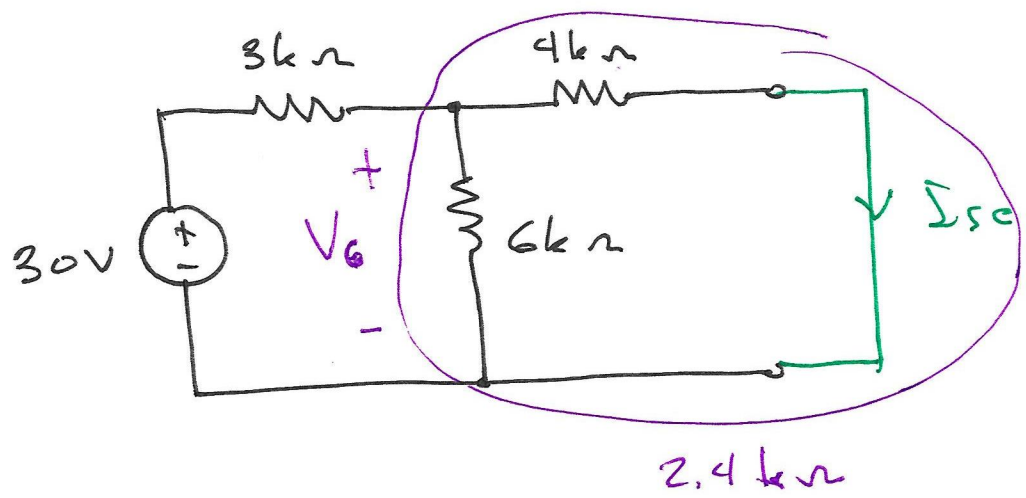


$$V_6 = \frac{2.4}{5.4} \cdot 30V$$

$$= \frac{12}{27} \cdot \frac{30}{10}$$

$$= \frac{120}{9} = \frac{40}{3} V$$

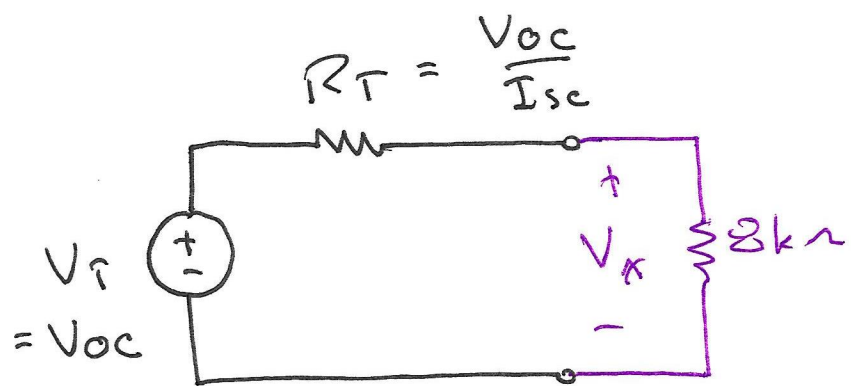
$$I_{sc} = \frac{\frac{40}{3}}{4k} = \frac{10}{3} mA$$



$$V_T = V_{oc} = 20V$$

$$R_T = \frac{20}{\frac{10}{3} \text{ mA}}$$

$$= 6k\Omega$$


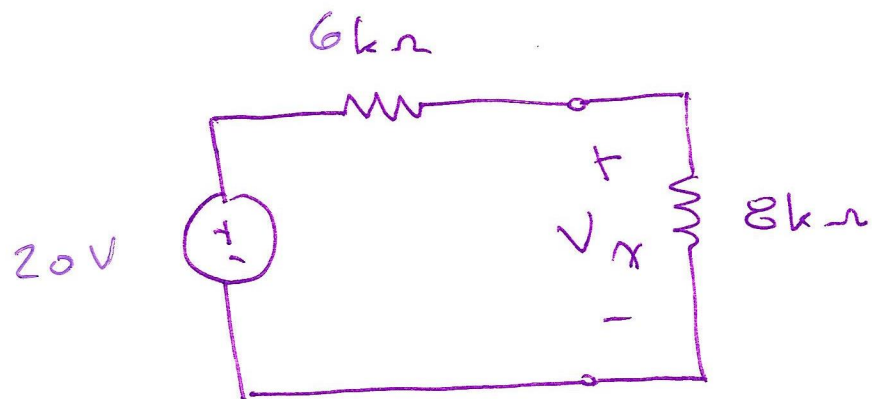



$$V_x = \frac{8}{6+8} \cdot 20$$

$$= \frac{4}{7} \cdot 20$$

$$= \frac{80}{7} \text{ V}$$

Operational Amplifiers

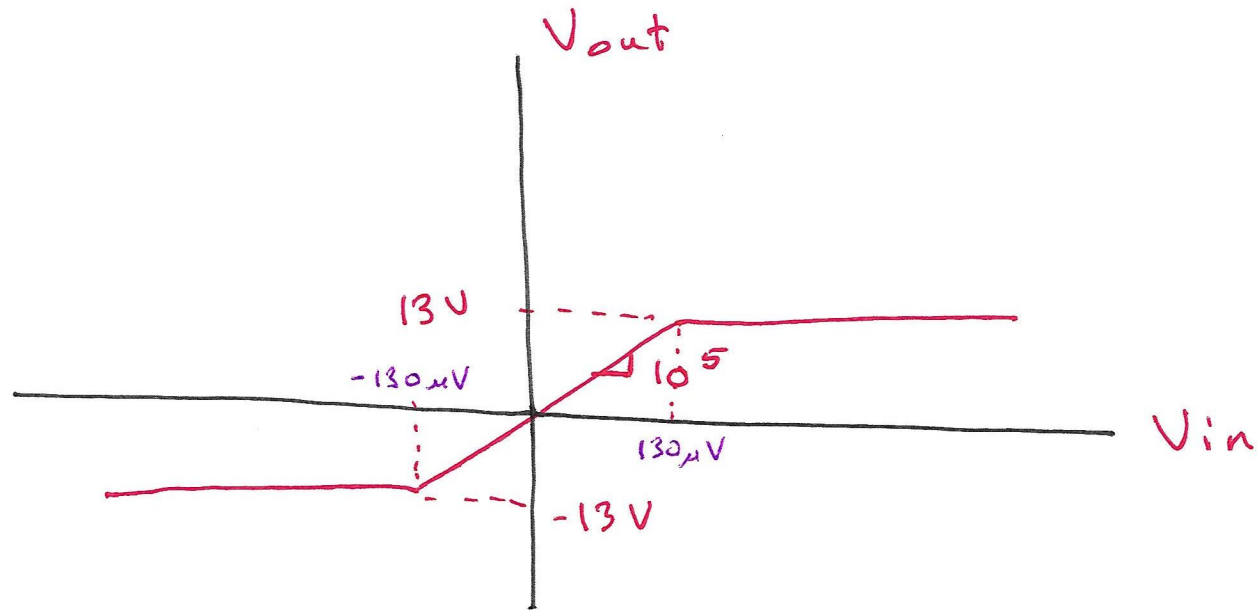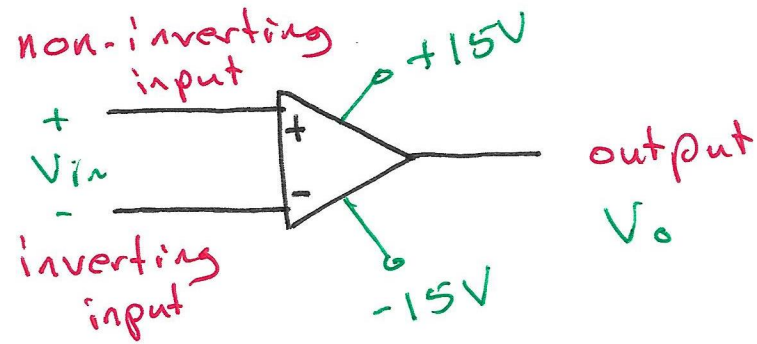

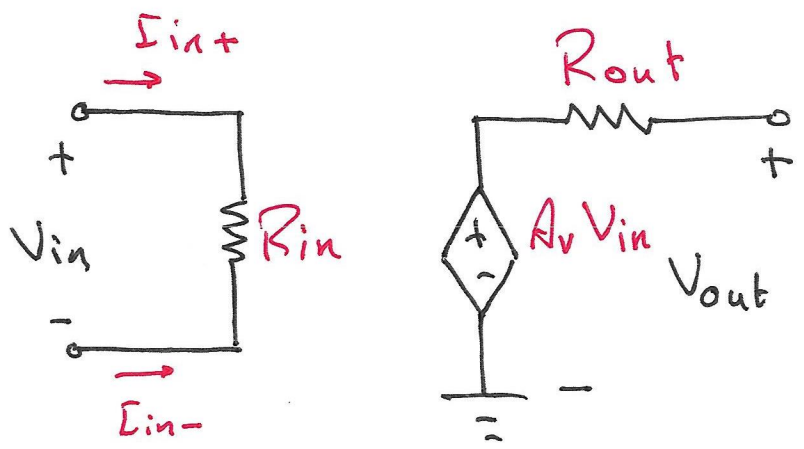

Op Amp

$$A_v \approx 10^5$$

$$R_{in} \approx 2M\Omega$$

$$R_{out} \approx 75\Omega$$

} LM741

For an ideal OpAmp:

$$V_{in} = 0$$

$$R_{in} = \infty$$

$$R_{out} = 0$$

$$A_v = \infty$$

$$I_{in} = 0$$

