
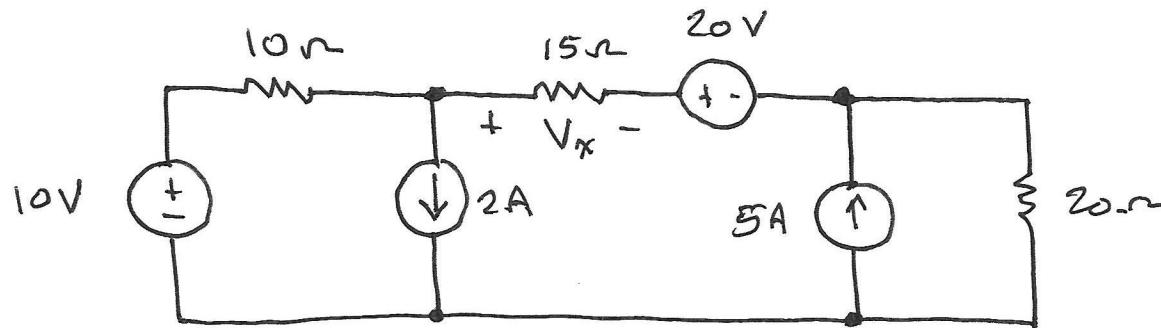


Superposition Example 1

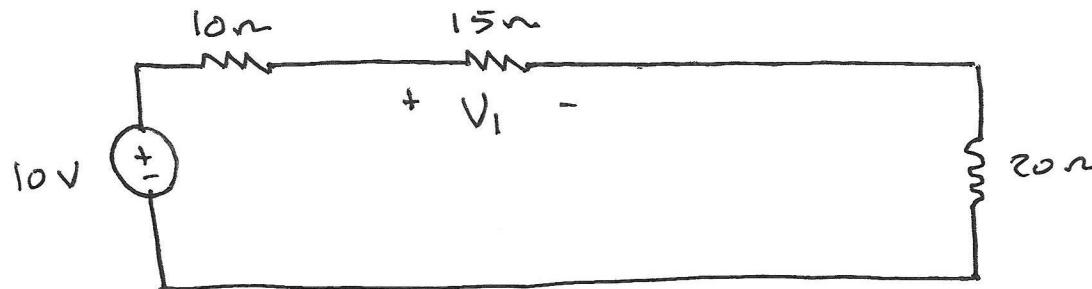


Determine the value of V_x using superposition

Circuit 1:




$$\begin{aligned}
 V_1 &= \frac{15\Omega}{10\Omega + 15\Omega + 20\Omega} \cdot 10 \\
 &= \frac{15}{45} \cdot 10 \\
 &= \frac{10}{3} \text{ V}
 \end{aligned}$$

Circuit 2:

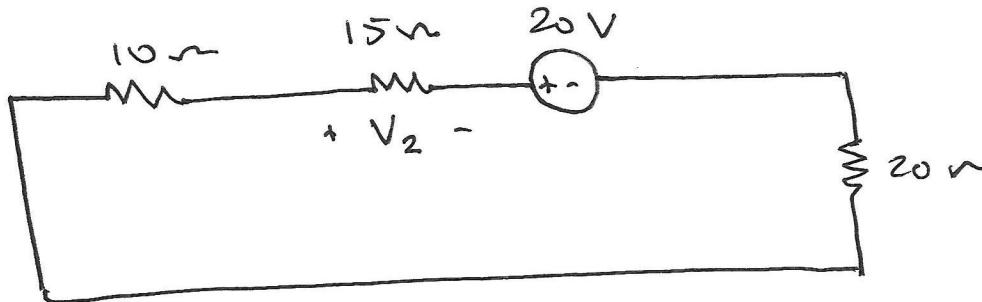


$$\begin{aligned}
 V_2 &= -\frac{15\Omega}{45\Omega} \cdot 20 \\
 &= -\frac{20}{3} \text{ V}
 \end{aligned}$$

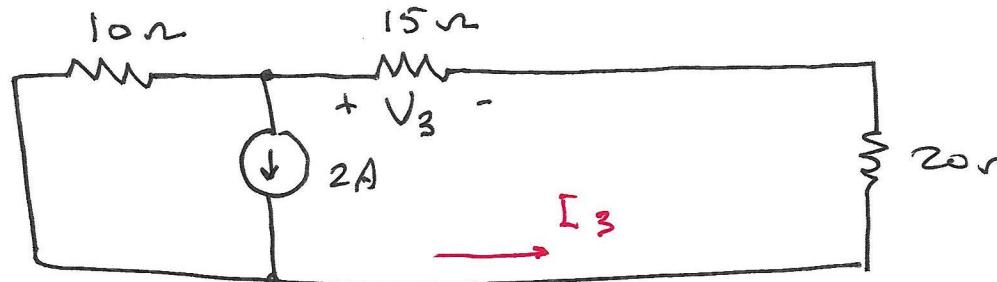Circuit 3:

$$\begin{aligned}
 I_3 &= \frac{10\text{ }\Omega}{10\text{ }\Omega + 35\text{ }\Omega} \cdot 2\text{ A} \\
 &= \frac{10}{45} \cdot 2\text{ A} \\
 &= \frac{2}{9} \cdot 2\text{ A} \\
 &= \frac{4}{9}\text{ A}
 \end{aligned}$$

$$\begin{aligned}
 V_3 &= -(15\text{ }\Omega) I_3 = -\frac{60}{9}\text{ V} \\
 &= -\frac{20}{3}\text{ V}
 \end{aligned}$$

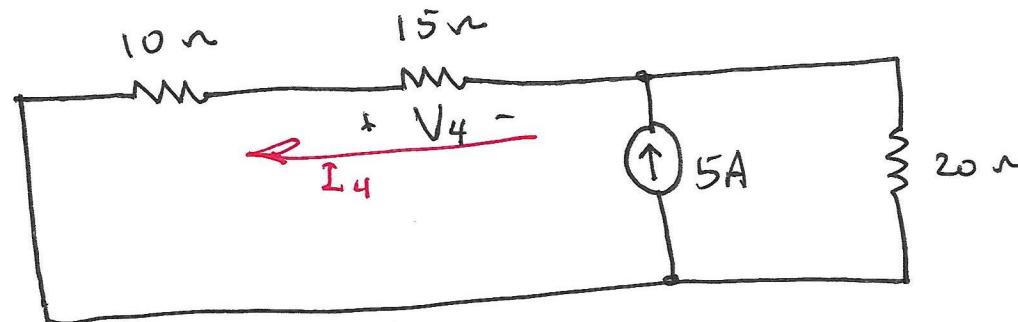
Circuit 4:

$$\begin{aligned}
 I_4 &= \frac{20\text{ }\Omega}{45\text{ }\Omega} \cdot 5\text{ A} \\
 &= \frac{20}{9}\text{ A}
 \end{aligned}$$

$$\begin{aligned}
 V_4 &= -(15\text{ }\Omega)(I_4) = -\frac{300}{9}\text{ V} \\
 &= -\frac{100}{3}\text{ V}
 \end{aligned}$$


$$\begin{aligned}
 V_x &= V_1 + V_2 + V_3 + V_4 \\
 &= \frac{10}{3} - \frac{20}{3} - \frac{20}{3} - \frac{100}{3} = -\frac{130}{3}\text{ V}
 \end{aligned}$$

Superposition Example 2:

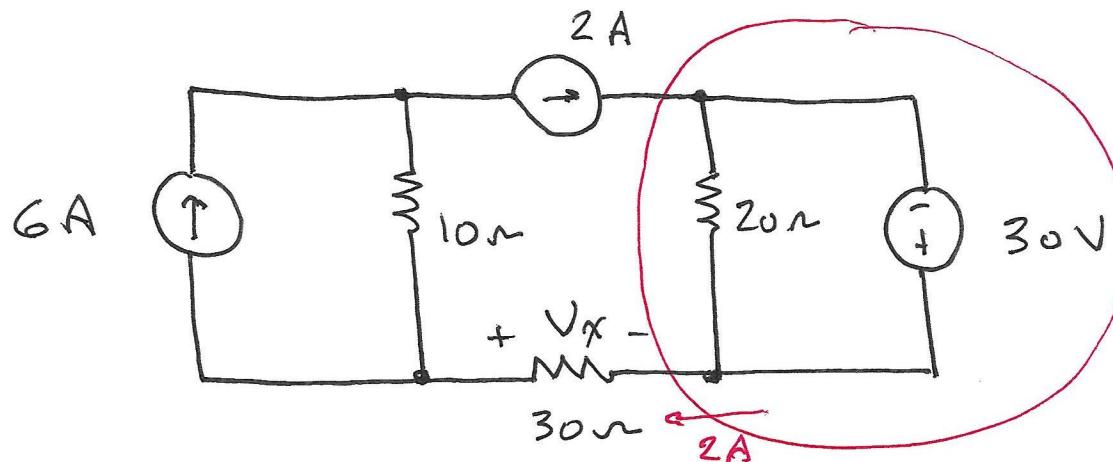


$$\begin{aligned}V_x &= - (30\Omega) I_2 \\&= - 60V\end{aligned}$$

Circuit 1:

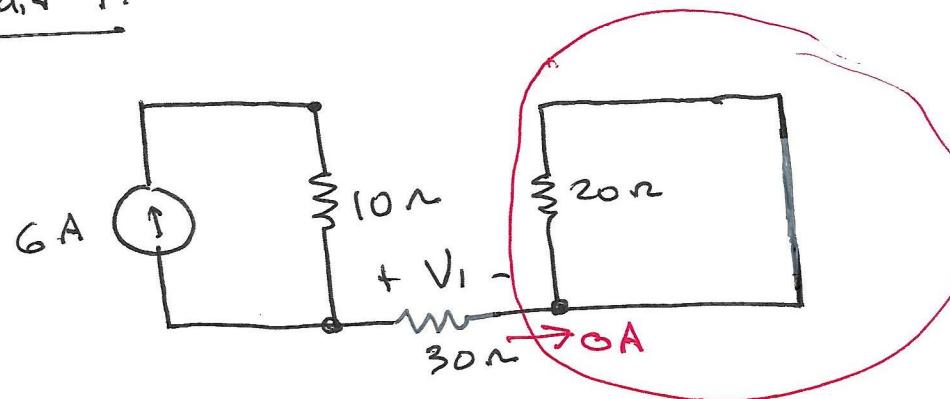


$$V_1 = 0$$


Circuit 2:

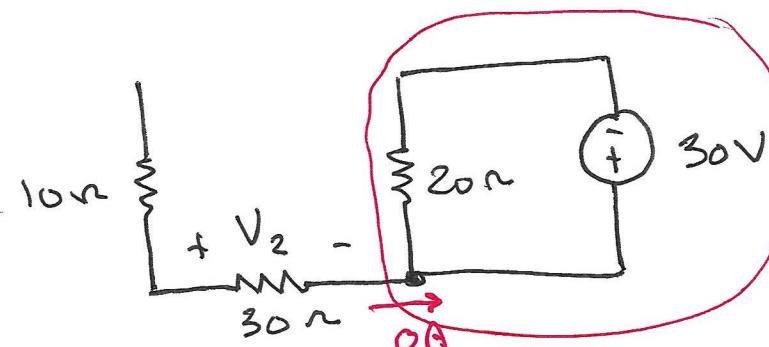


$$V_2 = 0$$

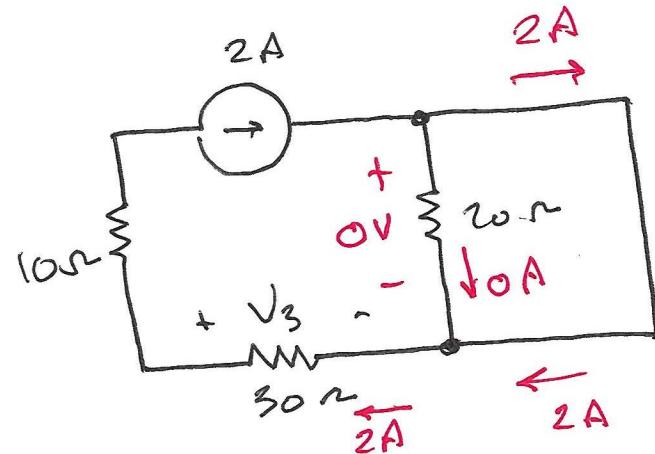Circuit 3:
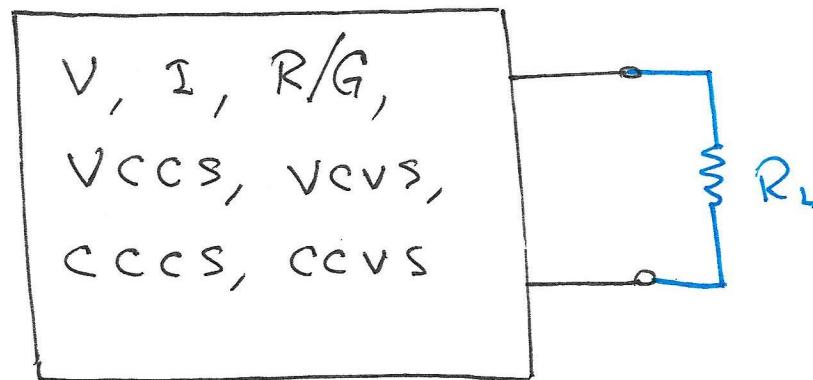
$$\begin{aligned} V_3 &= -(30\Omega)(2A) \\ &= -60V \end{aligned}$$



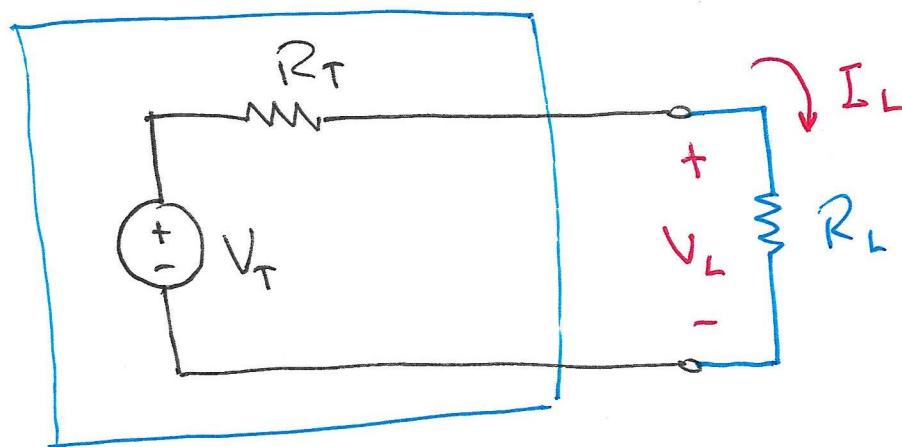What value of R_L will absorb maximum power?



R_L is called the load resistor.

Thévenin equivalent circuit of the box.

$$I_L = \frac{V_T}{R_T + R_L}$$

$$V_L = \frac{R_L}{R_T + R_L} V_T$$

$$P_L = V_L I_L = \frac{R_L V_T^2}{(R_T + R_L)^2}$$

$$P_L = \frac{R_L V_T^2}{(R_T + R_L)^2}$$

What value of R_L makes P_L a maximum?

$$\frac{dP_L}{dR_L} = \frac{(R_T + R_L)^2 V_T^2 - 2R_L V_T^2 (R_T + R_L)}{(R_T + R_L)^4}$$

Set $\frac{dP_L}{dR_L} = 0$ and solve for R_L .

$$(R_T + R_L) \cancel{V_T^2} - 2R_L \cancel{V_T^2} (R_T + R_L) = 0$$


$$R_T + R_L - 2R_L = 0$$

$R_L = R_T$ for maximum power delivered to the load.

Maximum Power Transfer Theorem


Choose $R_L = R_T = R_N$ for

maximum power delivered to the load


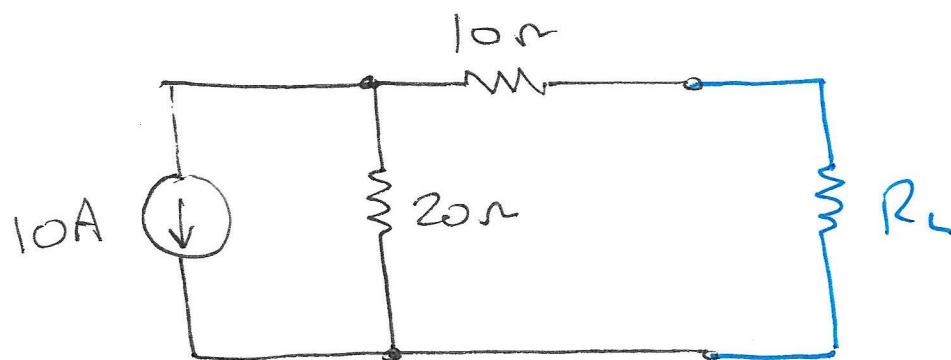


Choose R_L to absorb maximum power.

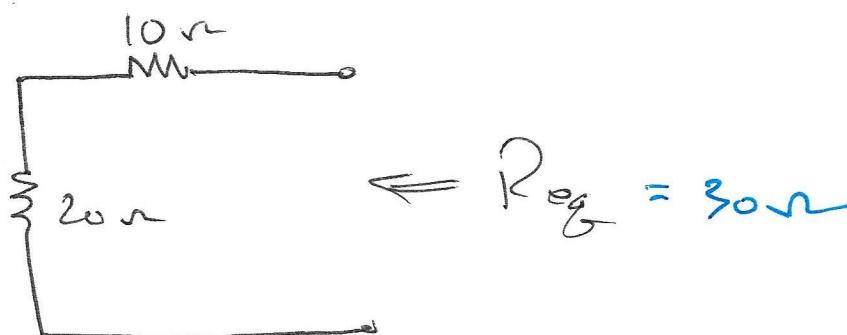
To find R_T or R_N ,
turn off the 10A source
and calculate the equivalent
resistance w.r.t. the output
terminals.




$$R_T = R_N = R_{eq}$$

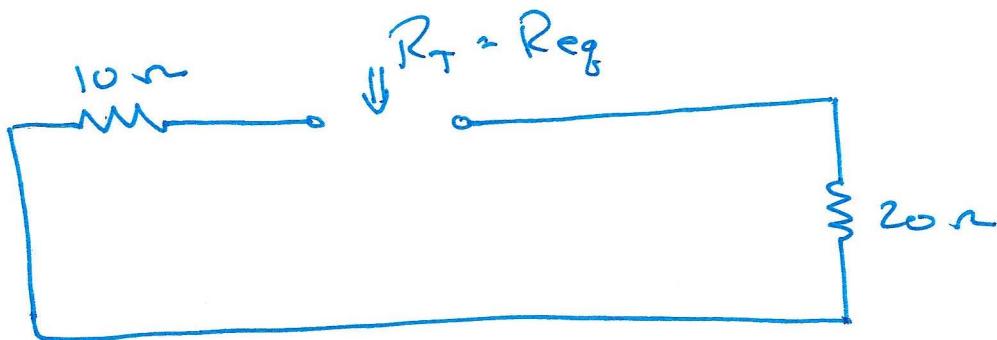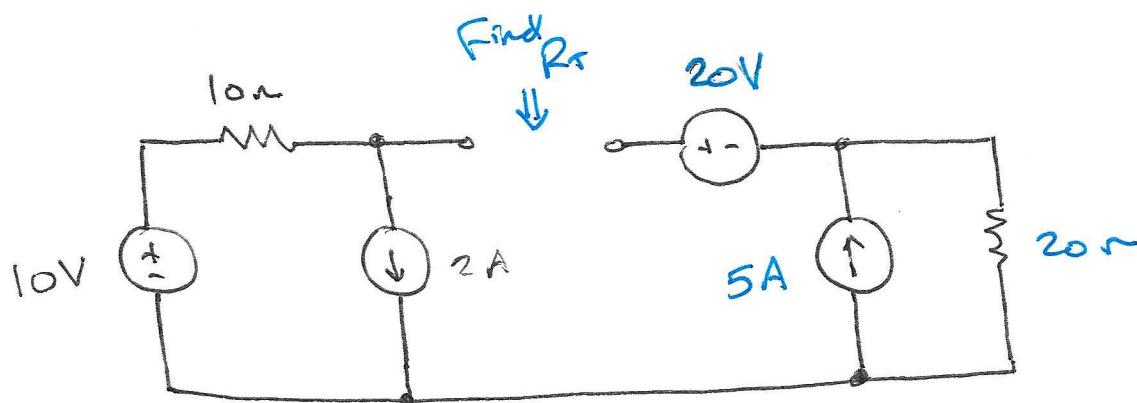

$$R_T = 10\Omega + 20\Omega = 30\Omega$$

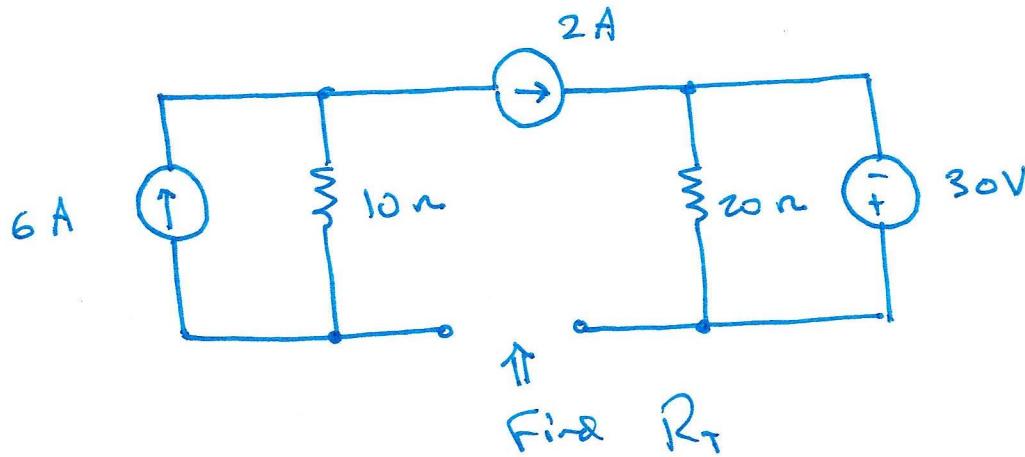

Turn off all independent sources:

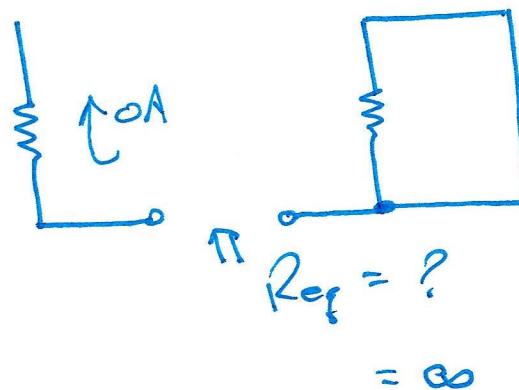

$$\ddot{x} + 2\dot{x} + 3x = 0$$

Can we build a circuit that will solve this
Ordinary Differential Equation (ODE) ?