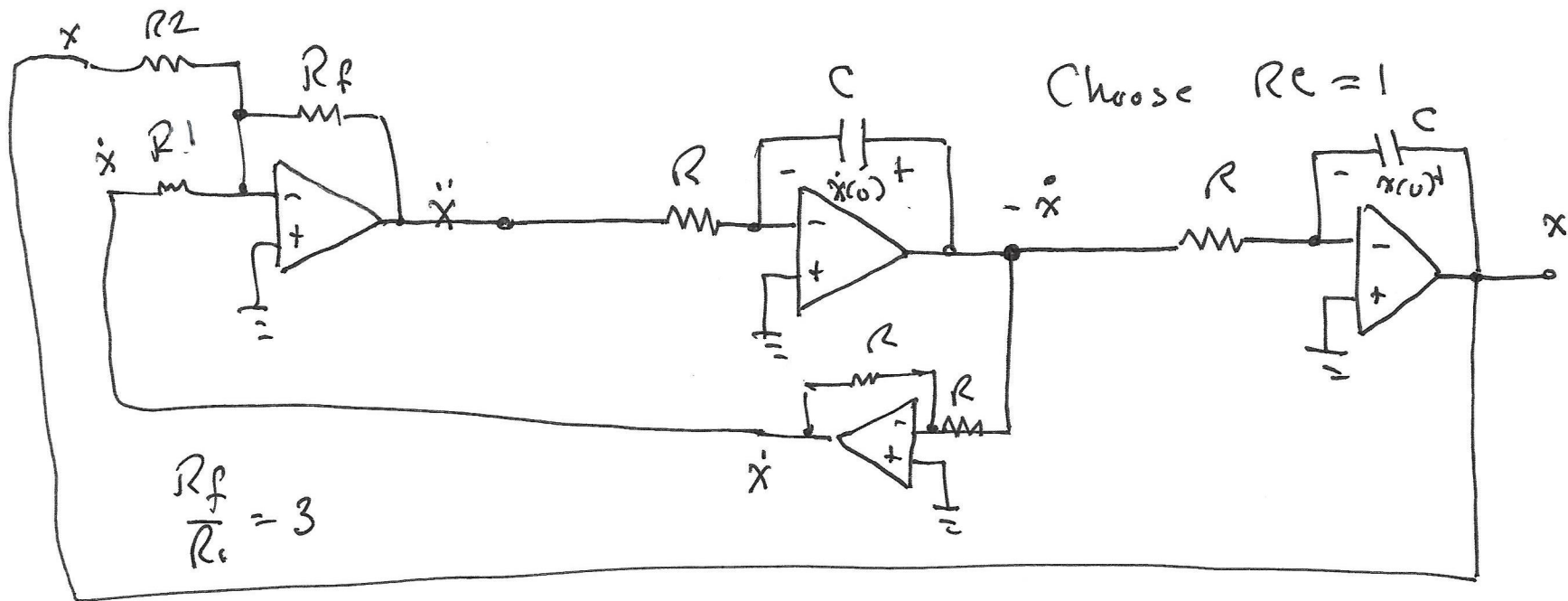


$$\ddot{x} + 3\dot{x} + 2x = 0$$

$$\ddot{x} = -3\dot{x} - 2x$$

Design an analog computer to solve for x .



$$\frac{R_f}{R_1} = 3$$

$$\frac{R_f}{R_2} = 2$$

Exam # 2 will be available next Thursday, November 4, and due the following Tuesday, November 9.


No class on Thursday, November 4.

Homework	20%
Exam 1	20%
Exam 2	20%
Final Exam	40%
	<hr/>
	100%

$$A \ddot{x} + B \dot{x} + C x = f(t)$$

$$\Rightarrow \ddot{x} + \frac{B}{A} \dot{x} + \frac{C}{A} x = \frac{1}{A} f(t)$$
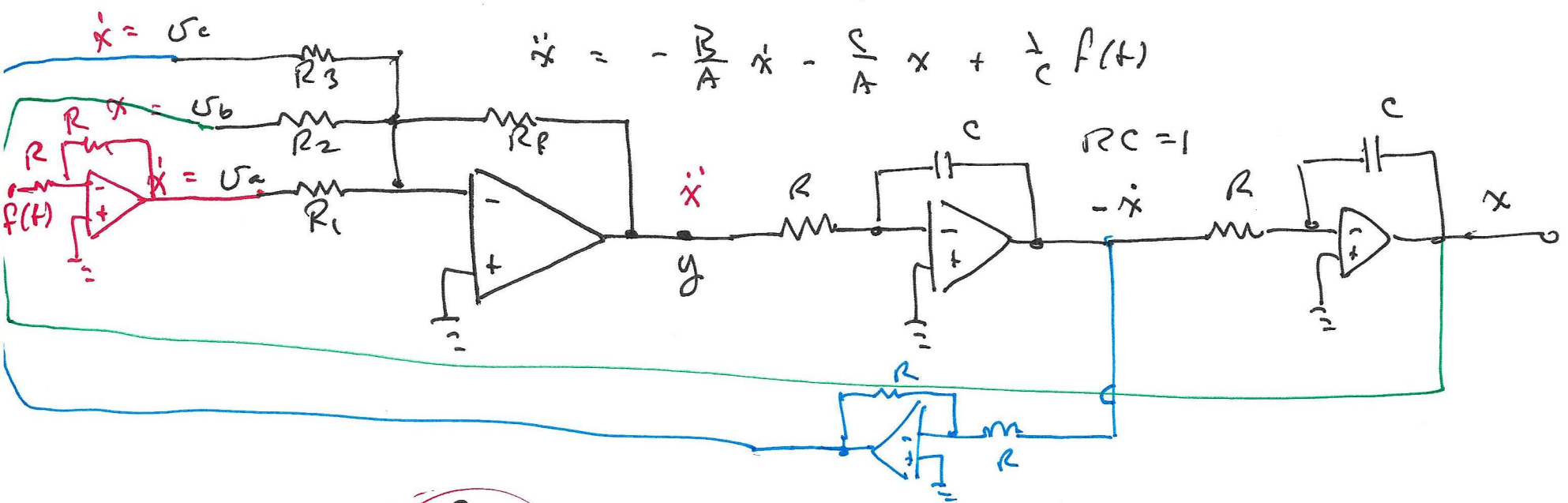
$$\ddot{x} = -\frac{B}{A} \dot{x} - \frac{C}{A} x + \frac{1}{A} f(t)$$



$$y = -\frac{R_f}{R_3} U_c - \frac{R_f}{R_2} U_b - \frac{R_f}{R_1} U_a$$

$$\frac{R_f}{R_3} = \frac{B}{A}$$

$$\frac{R_f}{R_2} = \frac{C}{A}$$

$$\frac{R_f}{R_1} = \frac{1}{C}$$

For example, $A = 2, B = 6, C = 1$

$$\frac{R_f}{R_3} = \frac{6}{2} = \frac{B}{A}$$

$$\frac{R_f}{R_2} = \frac{C}{A} = \frac{1}{2}$$

$$\frac{R_f}{R_1} = \frac{1}{C} = 1$$

$$\frac{R_f}{R_3} = \frac{2}{2} = 3$$

$$\frac{R_f}{R_2} = \frac{1}{2}$$

$$\frac{R_f}{R_1} = 1$$

Choose $R_f = 10 \text{ k}\Omega$

$$\frac{10 \text{ k}\Omega}{R_3} = 3 \Rightarrow R_3 = \frac{10}{3} \text{ k}\Omega$$


$$\frac{10 \text{ k}\Omega}{R_2} = \frac{1}{2} \Rightarrow R_2 = 20 \text{ k}\Omega$$

$$\frac{10 \text{ k}\Omega}{R_1} = 1 \Rightarrow R_1 = 10 \text{ k}\Omega$$

For the integrators, $RC = 1$

Arbitrarily Choose $R = 10k\Omega$

$$C = \frac{1}{10000} = 100\mu F$$

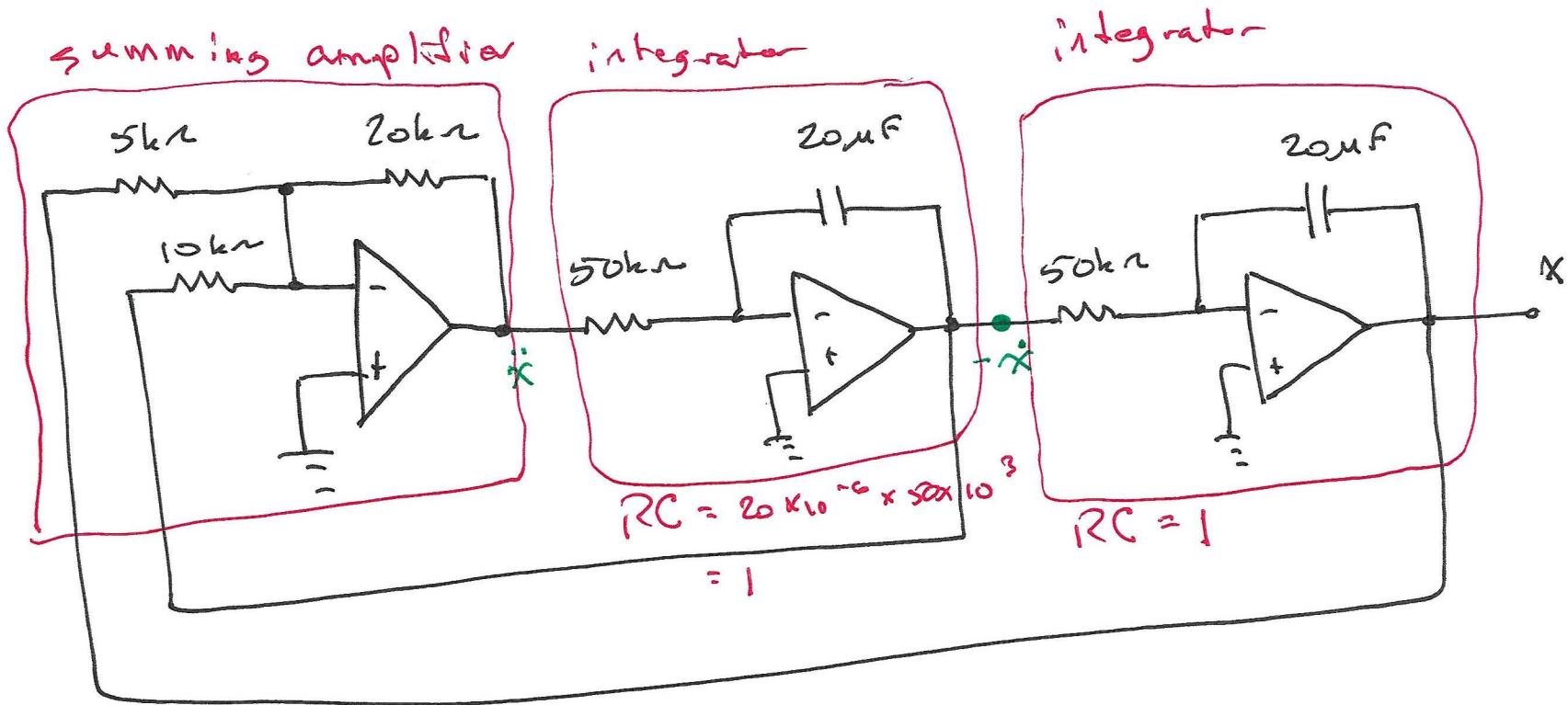


2nd order because there are 2 integrators

$$\ddot{x} = -\frac{20k\Omega}{5k\Omega} x - \frac{20k\Omega}{10k\Omega} (-\dot{x})$$

$$= -4x + 2\dot{x}$$

$$\boxed{\ddot{x} - 2\dot{x} + 4x = 0}$$

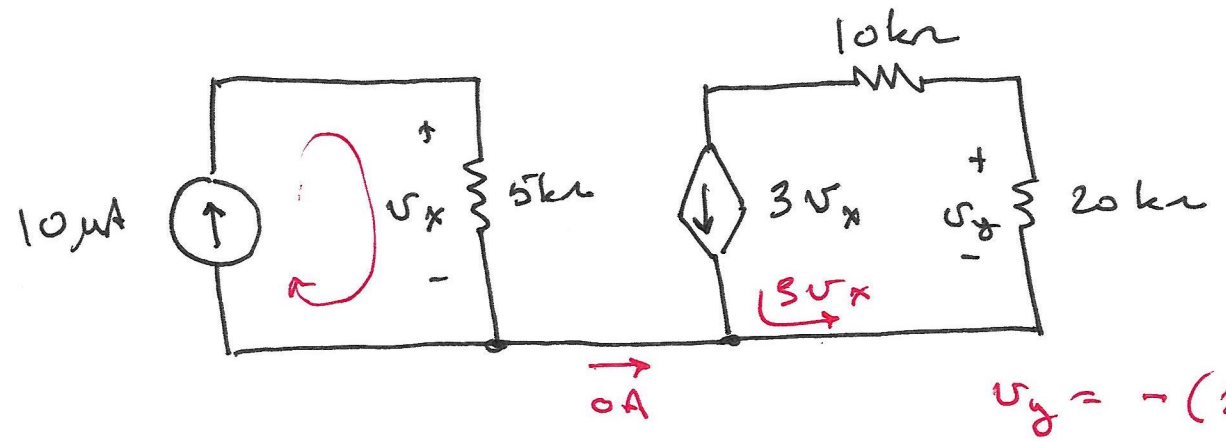


Find V_y .

$$V_y = -(20k\Omega) 3V_x$$


$$V_x = (5k\Omega) (10\mu A) = 50mV$$

$$V_y = -(20k\Omega) \underbrace{3(50mV)}_{\text{amperes}}$$


$$= -3kV$$

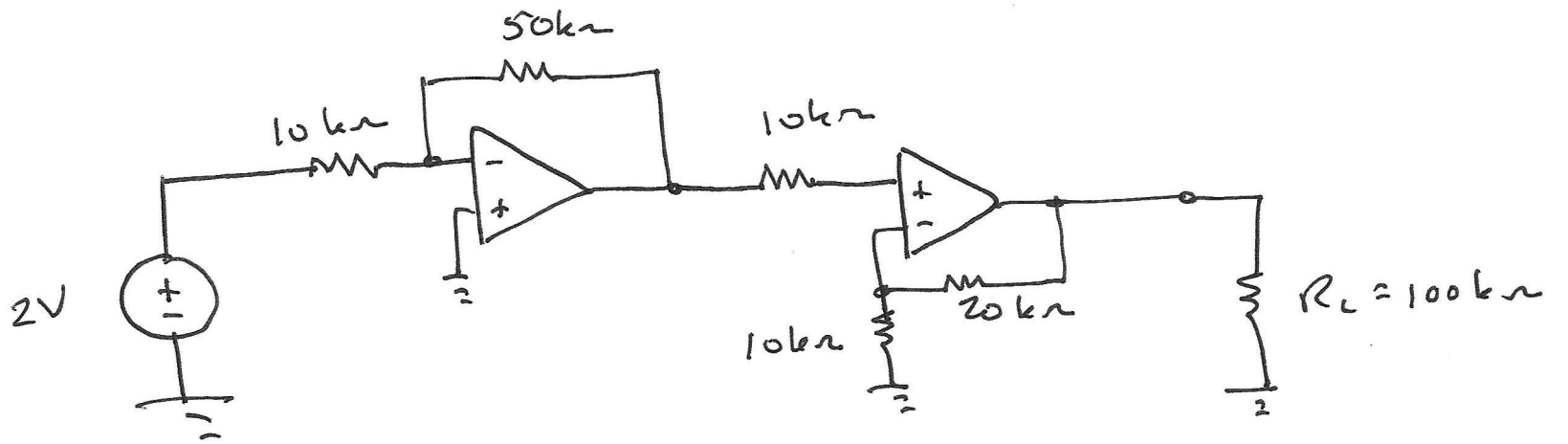

The opamps are ideal.

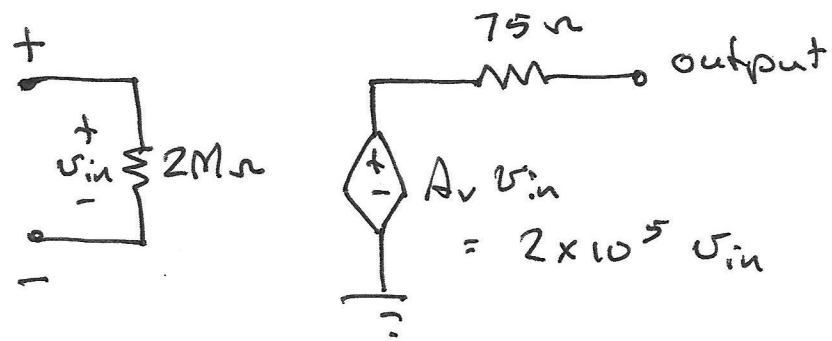

Close Model for an "ideal" Op Amp

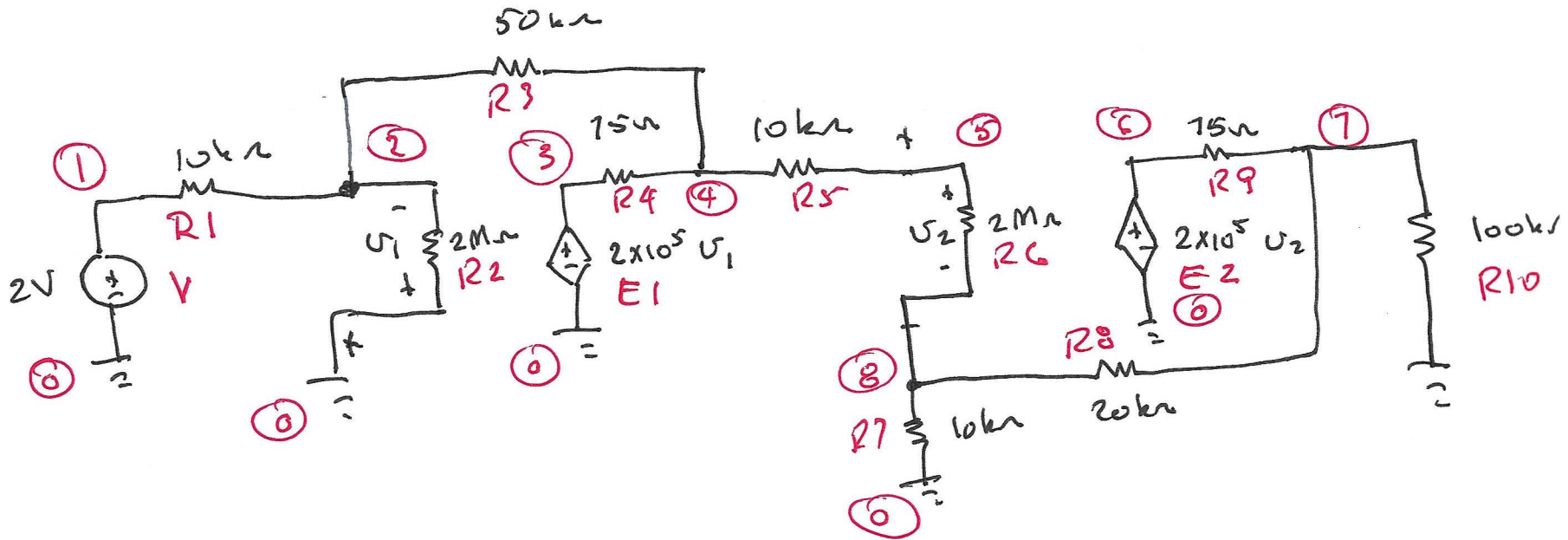



V	1	0	DC	2		
R1	1	2	10k			
R2	2	0	2MEG			
R3	2	4	50k			
R4	3	4	75			
E1	3	0	0	2		2E5
R5	4	5	10k			
R6	5	8	2MEG			
R7	8	0	10k			
R8	8	7	20k			
R9	6	7	75			
E2	6	0	5	8		2E5
R10	7	0	100k			
op						

