
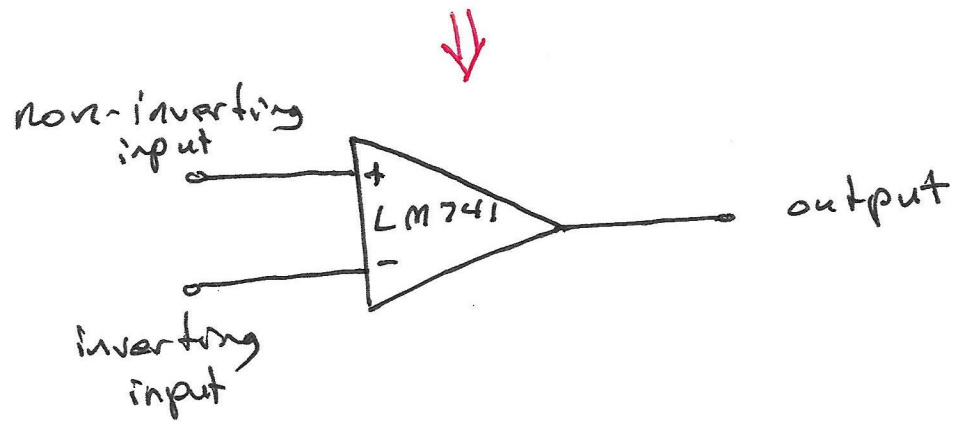


Each opamp is a LM741 opamp from National Semiconductor.

Simulate with LTspice


Define a subcircuit for the LM741 opamp.

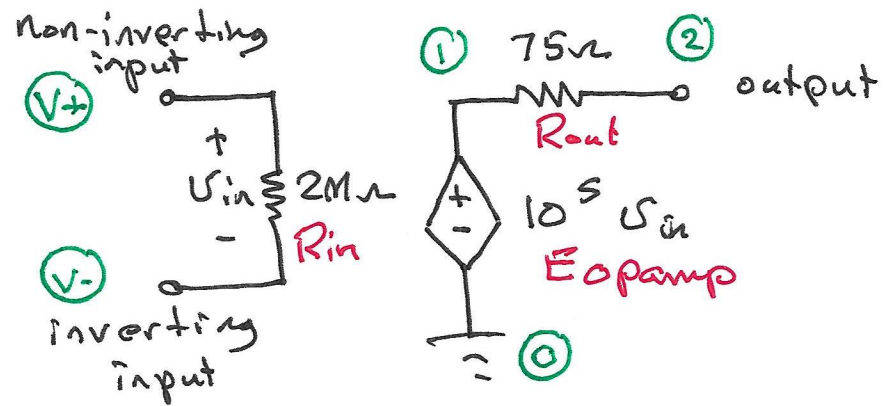

Subcircuit definition for the opamp:

```
.subckt LM741 V+ V- 2  
Rin V+ V- 2MEG  
Eopamp 1 0 V+ V- 1E5  
Rout 1 2 75  
.ends
```

For the integrator:

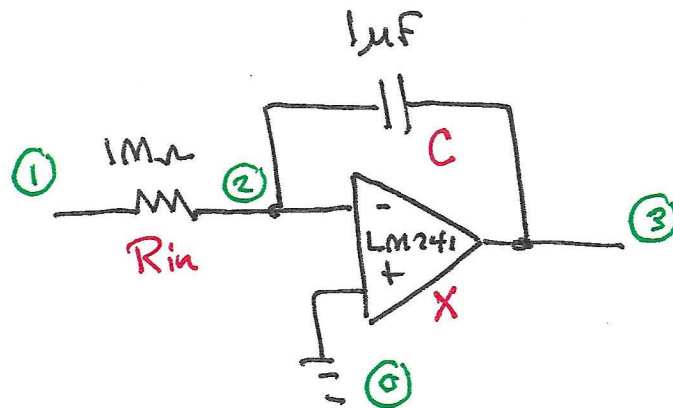

Subcircuit definition:

```
.subckt integrator 1 3
Rin 1 2 1MEG
C 2 3 1u
X 0 2 3 LM741
.ends
```

Using the subcircuits just discussed:

~~TITLE~~ automatically inserted by LTspice

```
Vin 1 0 DC 4
R1 1 2 10k
R2 7 2 10k
R3 9 2 10k
R4 2 3 100k
X1 0 2 3 LM741
X5 3 5 integrator
X6 5 7 integrator
R7 7 0 50k
R5 9 8 50k
R6 8 5 10k
X4 0 8 9 LM741
```

```
.subckt LM741 V+ V- 2
Rin V+ V- 2MEG
Eopamp 1 0 V+ V- 1E5
Rout 1 2 75
.ends
```

insert the LM741 subcircuit once

```
.subckt integrator 1 3
Rin 1 2 1MEG
C 2 3 1u
X 0 2 3 LM741
.ends
```


insert the integrator subcircuit once

```
.op
.end automatically inserted by LTspice
```

Download and install the LM741.MOD model.

Documents \ LTspice XVII \ sub \ LM741.MOD

This model requires 5 connections:

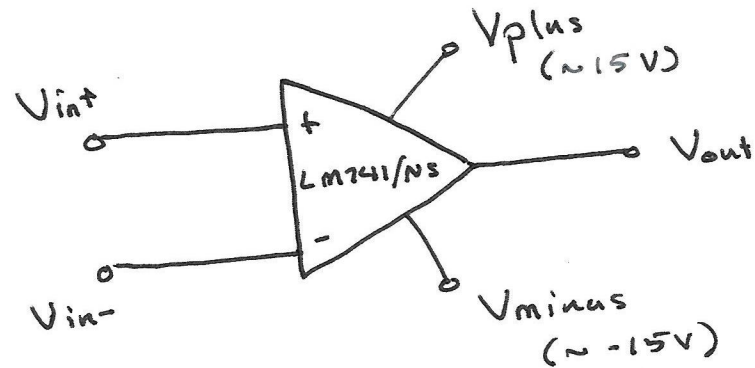

Using the National Semiconductor model for the LM741:

7

~~TITLE~~ automatically inserted by LTspice

```
Vin 1 0 DC 4
R1 1 2 10k
R2 7 2 10k
R3 9 2 10k
R4 2 3 100k
X1 0 2 V+ V- 3 LM741/NS
X5 3 5 V+ V- integrator
X6 5 7 V+ V- integrator
R7 7 0 50k
R5 9 8 50k
R6 8 5 10k
X4 0 8 V+ V- 9 LM741/NS
```

```
V+15 V+ 0 DC 15
```

```
V-15 V- 0 DC -15
```

```
.LIB LM741.MOD
```

```
.subckt integrator 1 3 V+15 V-15
```

```
Rin 1 2 1MEG
```


```
C 2 3 1u
```

```
X 0 2 V+15 V-15 3 LM741/NS
```

```
.ends
```

```
.op
```

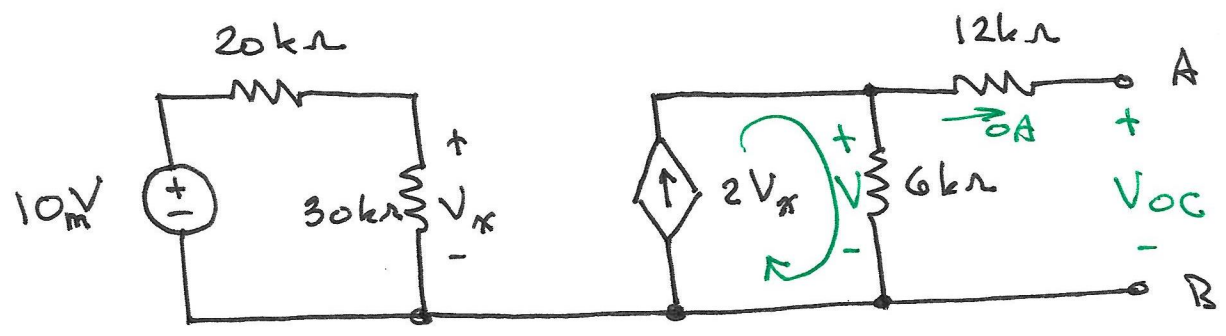~~word~~ automatically inserted by LTspice




Find the Thévenin equivalent circuit w.r.t. terminals A,

$$V_x = \frac{3}{5} 10\text{mV} = 6\text{mV}$$

$$2V_x = 12\text{mA}$$
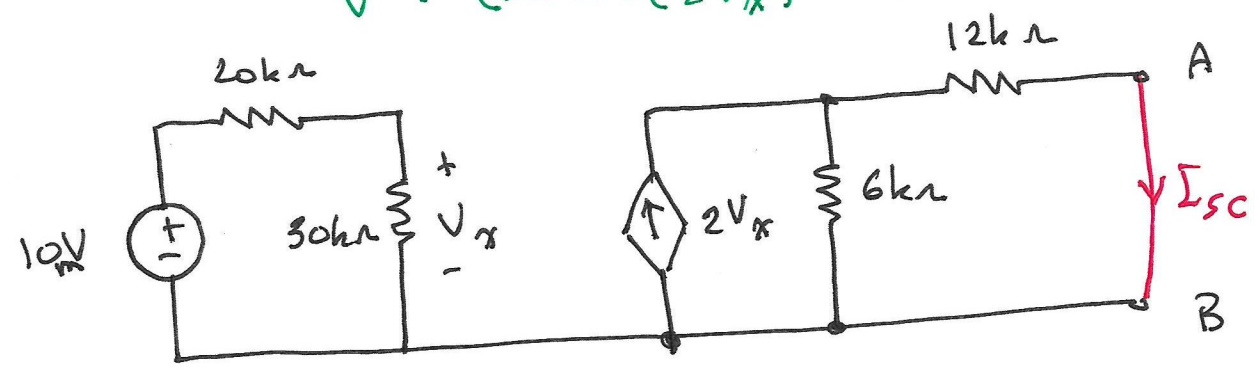
$$V = (6\text{k}\Omega)(2V_x) = 72\text{V} = V_{oc}$$




$$V_x = 6\text{mV}$$

$$2V_x = 12\text{mA}$$


$$I_{sc} = \frac{6}{18} (12\text{mA}) = 4\text{mA}$$

Thévenin equivalent:


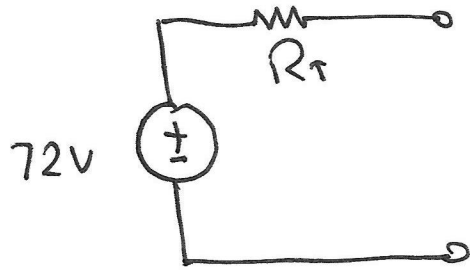


$$R_T = \frac{V_{oc}}{I_{sc}} = \frac{72V}{4mA} = 18k\Omega$$

Norton equivalent:

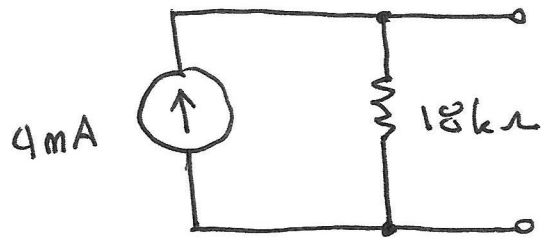

CCCS

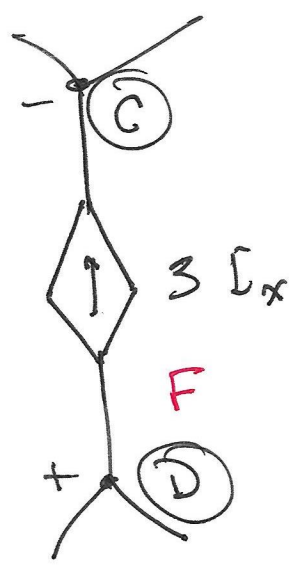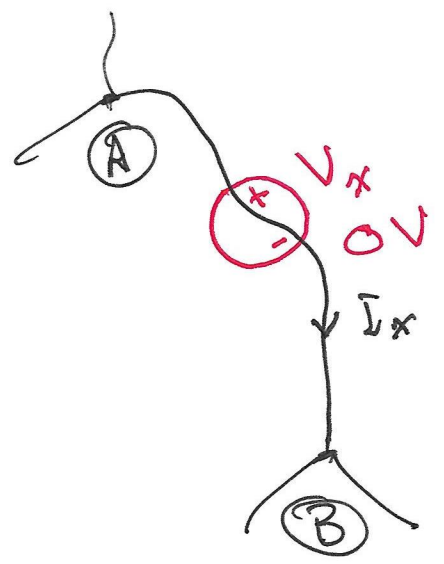

VCVS	E	
CCCS	F	✓
VCCS	G	
CCVS	H	✓

F	D	C	V_x	3
V_x	A	B	DC	0