

$$V_R = RC \dot{V}_C$$

$$V_C + V_R = 0$$

$$V_C + R C \dot{V}_C = 0$$

$$\dot{V}_C + \frac{1}{RC} V_C = 0$$

Assume $V_C = K e^{\alpha t}$

$$\alpha K e^{\alpha t} + \frac{1}{RC} K e^{\alpha t} = 0$$

$$K e^{\alpha t} (\alpha + \frac{1}{RC}) = 0$$


$$\alpha + \frac{1}{RC} = 0$$

characteristic
equation


$$\alpha = -\frac{1}{RC}$$

$\tau = RC$ is called the time constant

Similarly, for an RL circuit:

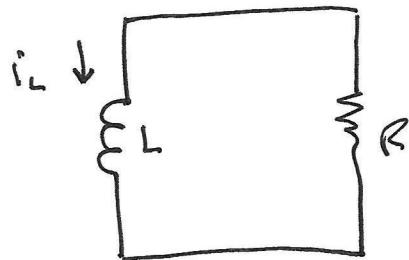
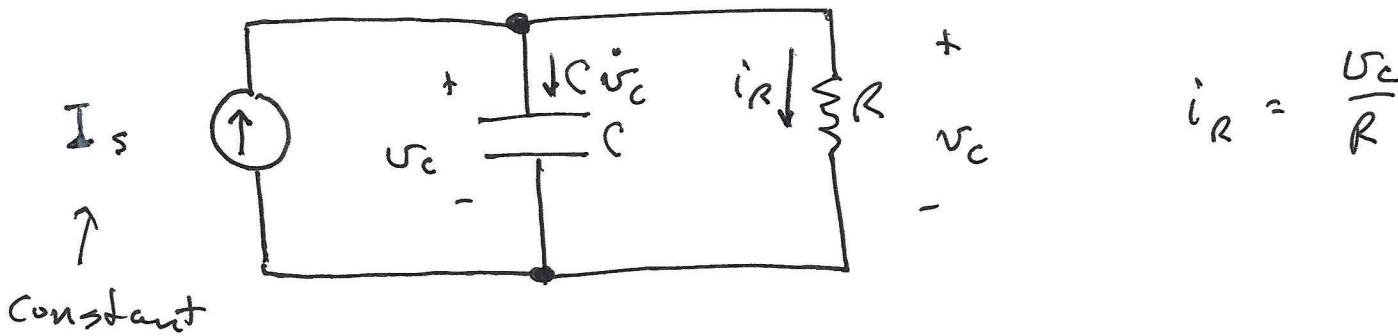
$$i_L(t) = K e^{-\alpha t} \quad \text{where } \alpha = \frac{R}{L} \quad \text{or} \quad \tau = \frac{L}{R}$$




$$i_R = \frac{V_c}{R}$$

$$C \dot{V}_c + i_R = I_s$$

$$C \dot{V}_c + \frac{V_c}{R} = I_s$$
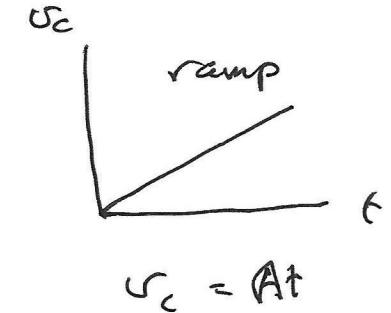
$$\dot{v}_c + \frac{1}{RC} v_c = \frac{I_s}{C}$$



$$v_c = K_1 e^{\alpha t} + K_2$$

$$\underbrace{\alpha K_1 e^{\alpha t}}_{\dot{v}_c} + 0 + \underbrace{\frac{K_1}{RC} e^{\alpha t} + \frac{K_2}{RC}}_{\frac{1}{RC} v_c} = \frac{I_s}{C}$$

$$K_1 e^{\alpha t} \left(\alpha + \frac{1}{RC} \right) + \frac{K_2}{RC} = \frac{I_s}{C}$$

$$K_1 e^{\alpha t} \left(\alpha + \frac{1}{RC} \right) = 0$$

$$\alpha + \frac{1}{RC} = 0$$

characteristic
equation

Same as before!

$$\frac{K_2}{RC} = \frac{I_s}{C} \Rightarrow K_2 = RI_s$$

$$v_c(t) = K_1 e^{\alpha t} + R I_s$$



$$\lim_{t \rightarrow \infty} v_c(t) = R I_s = \underbrace{v_c(\infty)}$$

final value
of $v_c(t)$

$$v_c(t) = K_1 e^{\alpha t} + v_c(\infty)$$

For large values of t , $i_c(t) \rightarrow 0$

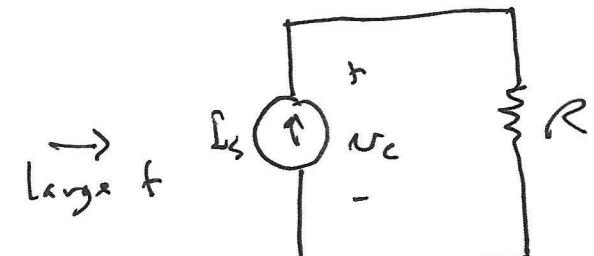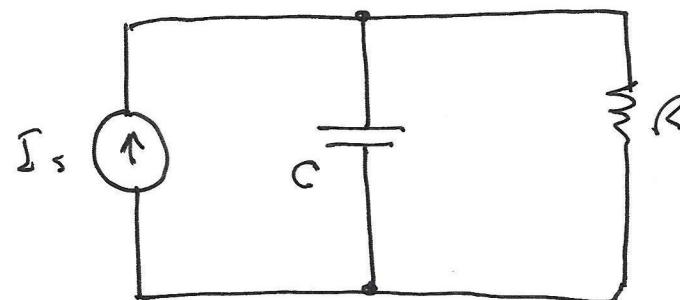The capacitor behaves like an open circuit for large value of t .



$$v_c(\infty) = R I_s$$

How do we find K_1 ?

$$\alpha = -\frac{1}{RC} \quad \text{or} \quad T = \frac{1}{RC}$$

$$V_c(\infty) = RI_s$$

$$V_c(t) = K_1 e^{\alpha t} + V_c(\infty)$$


$$\Rightarrow V_c(t) = K_1 e^{-t/RC} + RI_s$$

$$V_c(0) = K_1 + V_c(\infty)$$

$$\therefore K_1 = V_c(0) - V_c(\infty)$$

So, in general, for an RC circuit,
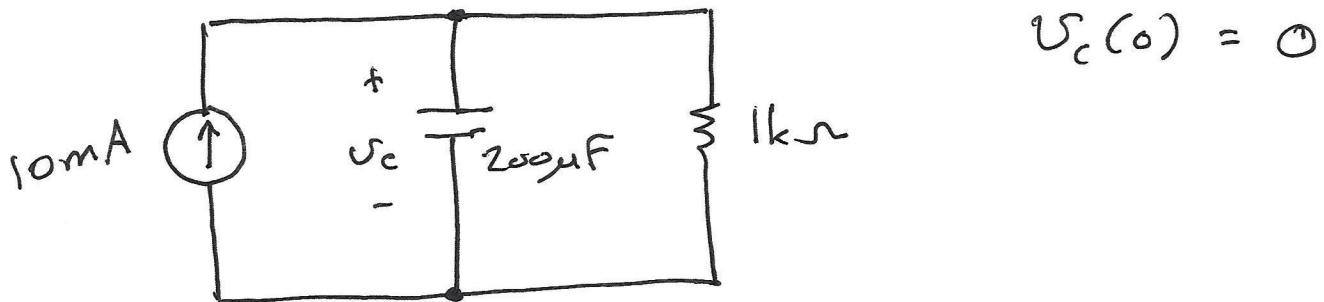
$$V_c(t) = [V_c(0) - V_c(\infty)] e^{-t/RC} + V_c(\infty)$$



$$V_c(0) = 0$$

Determine $V_c(t)$ for $t \geq 0$.

We know:


$$V_c(t) = [V_c(0) - V_c(\infty)] e^{-t/RC} + V_c(\infty)$$

$$\text{Here } \tau = RC = 1000 \times 200 \times 10^{-6} = 0.2 \text{ s}$$

$$V_c(0) = 0 \quad (\text{given})$$

$$V_c(\infty) = (1k\Omega)(10mA) = 10V$$
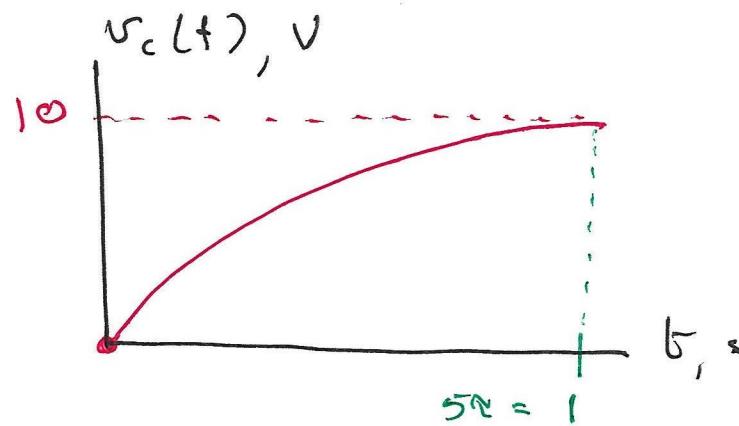
$$\begin{aligned} \therefore V_c(t) &= (0 - 10) e^{-t/0.2} + 10 \\ &= -10e^{-5t} + 10 \quad V, t \geq 0 \end{aligned}$$




Revise the problem to have $V_c(0) = 5 \text{ V}$


$$V_c(t) = [V_c(0) - V_c(\infty)] e^{-t/\tau} + V_c(\infty)$$

$$V_c(\infty) = 10 \text{ V}$$

$$\tau = RC = 0.2 \text{ s}$$
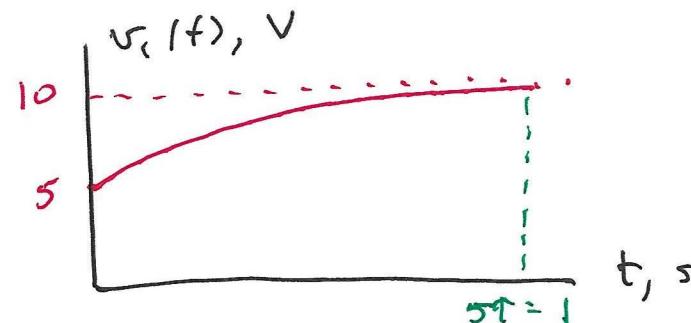
$$\begin{aligned} V_c(t) &= [5 - 10] e^{-t/0.2} + 10 \\ &= -5 e^{-5t} + 10 \quad V, \quad t \geq 0 \end{aligned}$$



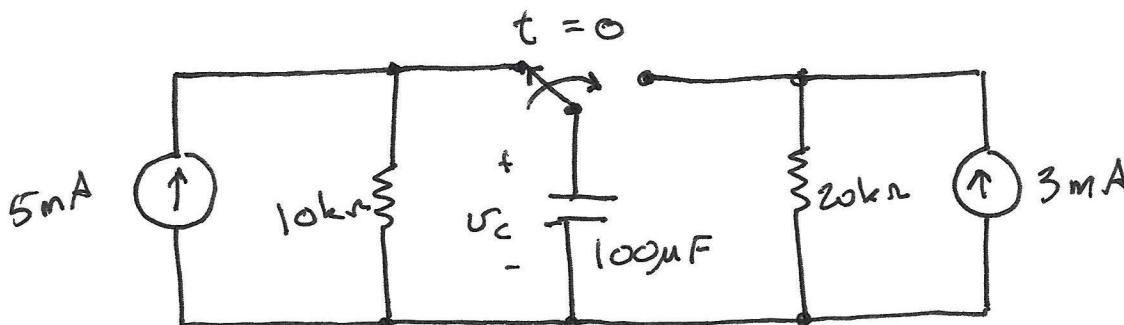

Determine
 $v_c(t)$ for
 $t \geq 0$.

$$R_{\text{LHS}} = 1 \times$$

1. Find $v_c(0^-)$. $v_c(0^-) = (10k\Omega)(5mA) = 50V$

2. $v_c(0^+) = v_c(0^-) = 50V$

$v_c(0^+)$ is the initial value for the capacitor voltage after the switch is moved.

3. For the circuit on the r.h.s.:

$$\tau = (20k\Omega)(100\mu F) = 2s$$

$$v_c(\infty) = (3mA)(20k\Omega) = 60V$$

$$\begin{aligned} \therefore v_c(t) &= [v_c(0) - v_c(\infty)] e^{-t/\tau} + v_c(\infty) \\ &= (50 - 60) e^{-t/2} + 60 \\ &= -10 e^{-t/2} + 60 \quad V, \quad t \geq 0 \end{aligned}$$

