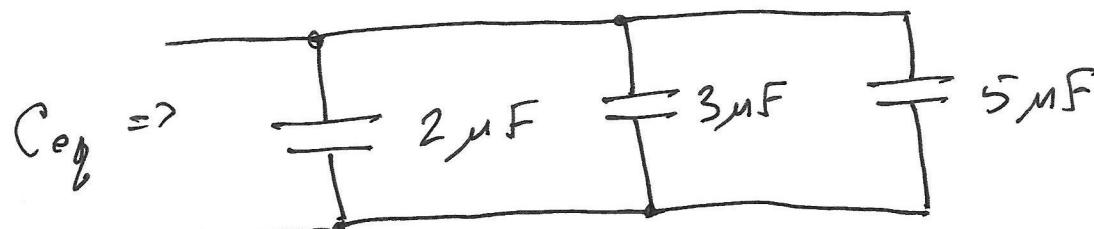


$$i_1 = C_1 \dot{v}, \quad i_2 = C_2 \dot{v} \quad \dots \quad i_n = C_n \dot{v}$$

$$\begin{aligned} i &= i_1 + i_2 + \dots + i_n \\ &= C_1 \dot{v} + C_2 \dot{v} + \dots + C_n \dot{v} \end{aligned}$$


$$i = \underbrace{(C_1 + C_2 + \dots + C_n)}_{C_{eq}} \dot{v}$$

$$C_{eq} = C_1 + C_2 + \dots + C_n$$



$$C_{eq} = (2 + 3 + 5) \mu F = 10 \mu F$$

## Capacitors in Series

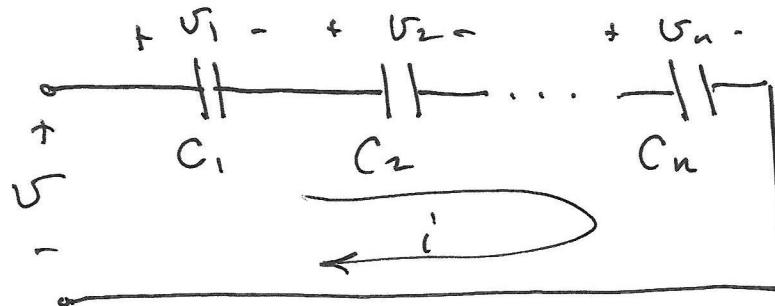


$$v = \underbrace{\frac{1}{C_1} \int idt}_{v_1} + \underbrace{\frac{1}{C_2} \int idt}_{v_2} + \dots + \underbrace{\frac{1}{C_n} \int idt}_{v_n}$$

$$v = \underbrace{\left( \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right)}_{\frac{1}{C_{eq}}} \int idt$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

# Inductors in Parallel

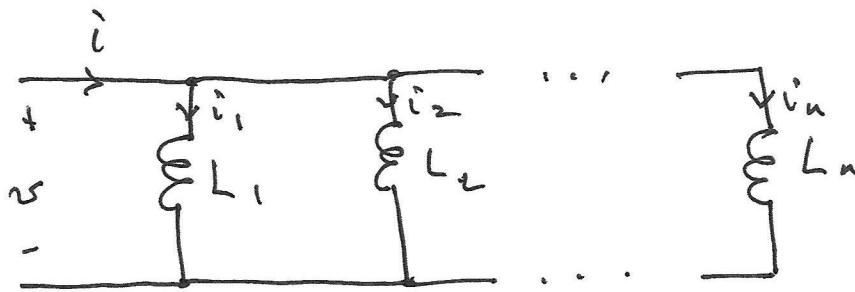


$$i = \underbrace{\frac{1}{L_1} \int v dt}_{i_1} + \underbrace{\frac{1}{L_2} \int v dt}_{i_2} + \dots + \underbrace{\frac{1}{L_n} \int v dt}_{i_n}$$

$$i = \underbrace{\left( \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right)}_{\frac{1}{L_{\text{eq}}}} \int v dt$$

$$\frac{1}{L_{\text{eq}}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$

### Inductors in Series

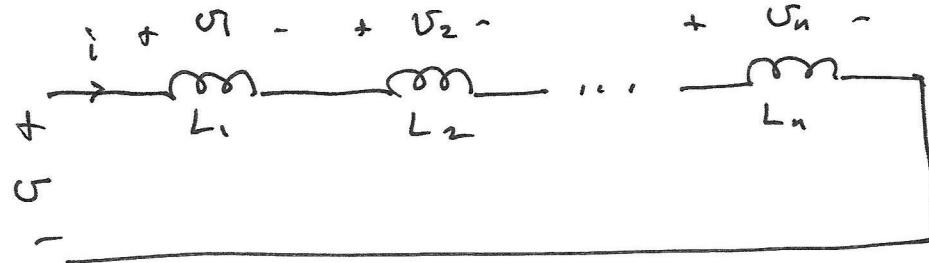



$$U_1 = L_1 \frac{di}{dt} \quad U_2 = L_2 \frac{di}{dt} \quad \dots \quad U_n = L_n \frac{di}{dt}$$

$$U = U_1 + U_2 + \dots + U_n$$

$$= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_n \frac{di}{dt}$$

$$U = \underbrace{(L_1 + L_2 + \dots + L_n)}_{L_{eq}} \frac{di}{dt}$$

$$L_{eq} = L_1 + L_2 + \dots + L_n$$

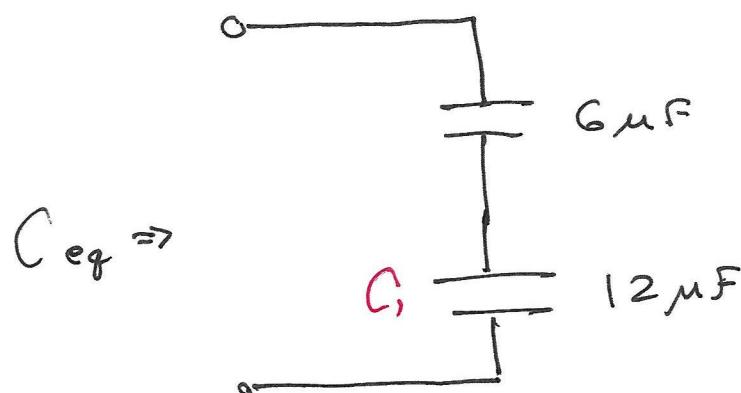
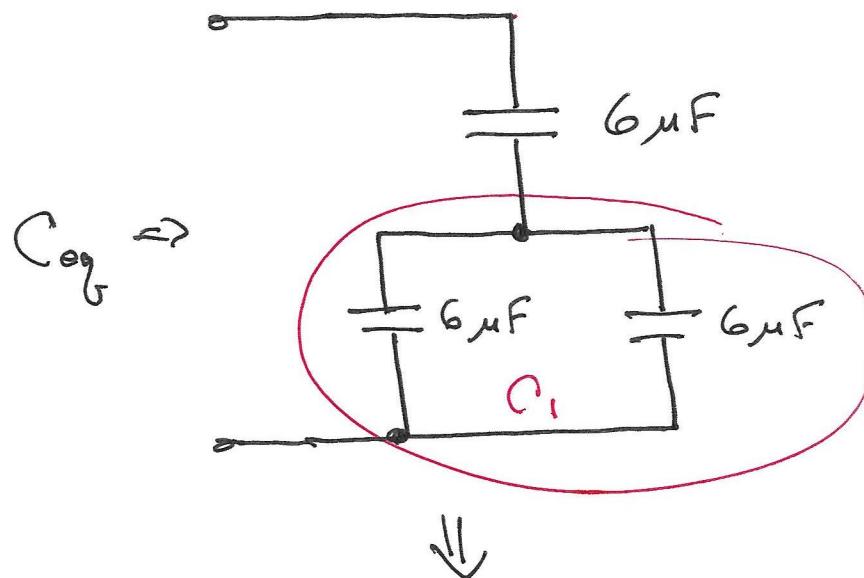


$$C_1 = 6\mu F + 6\mu F = 12\mu F$$


$$\begin{aligned}\frac{1}{C_{eq}} &= \frac{1}{6\mu F} + \frac{1}{12\mu F} \\ &= \frac{3}{12\mu F} = \frac{1}{4\mu F}\end{aligned}$$

$$C_{eq} = 4\mu F$$

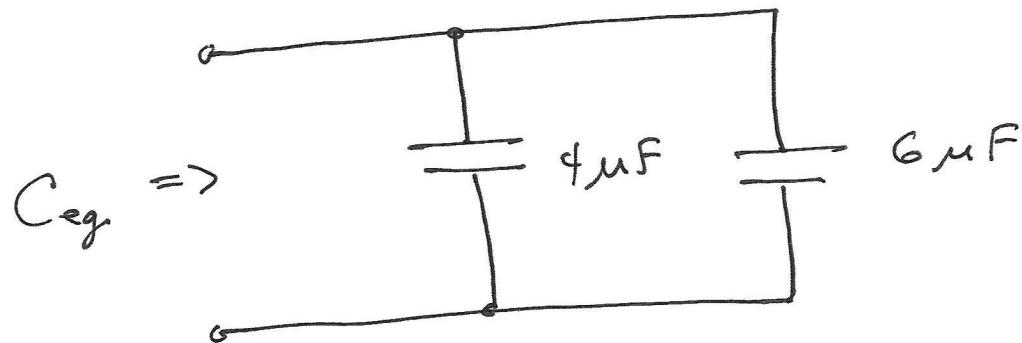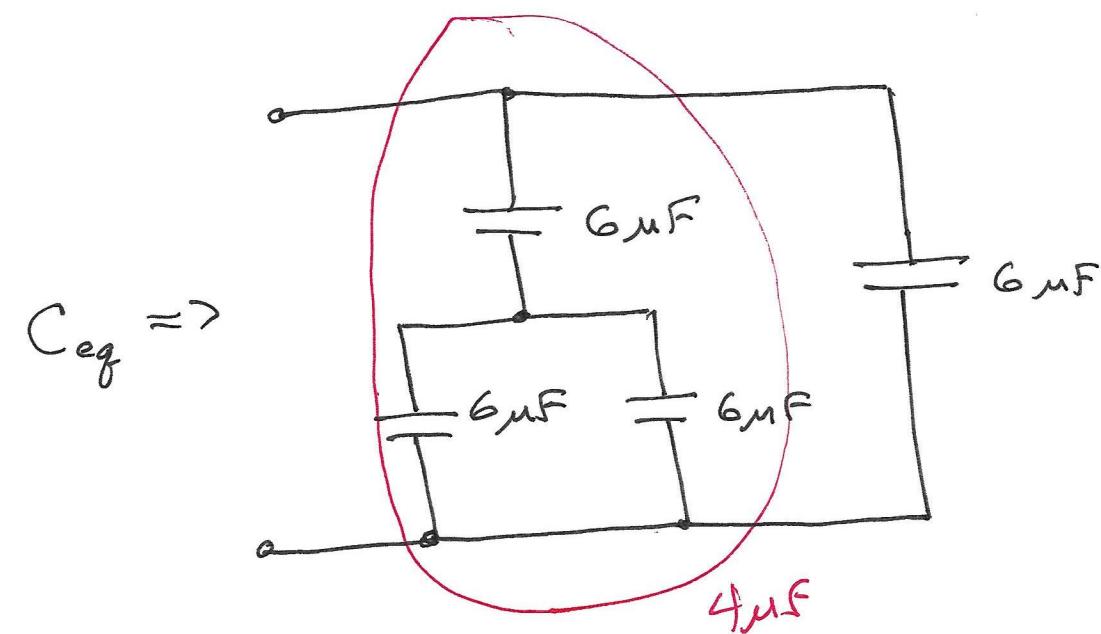
$$\text{or } C_{eq} = \frac{6 \cdot 12}{6 + 12} = 4\mu F$$




$$C_{eq} = 10\ \mu F$$

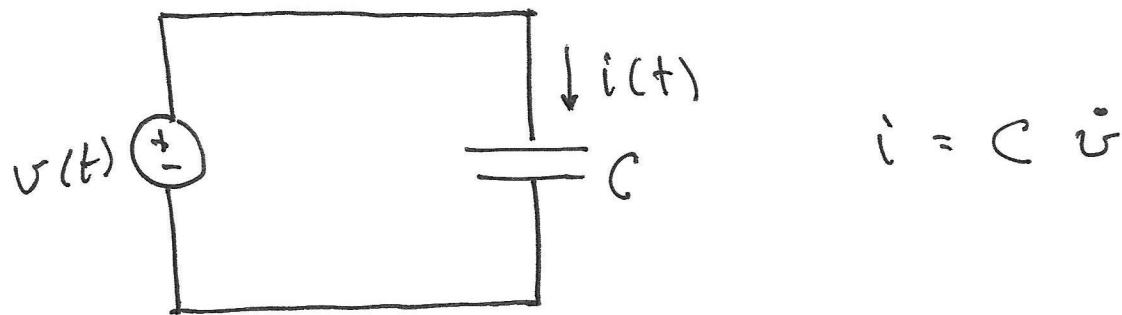




$$\dot{i} = C \dot{v}$$

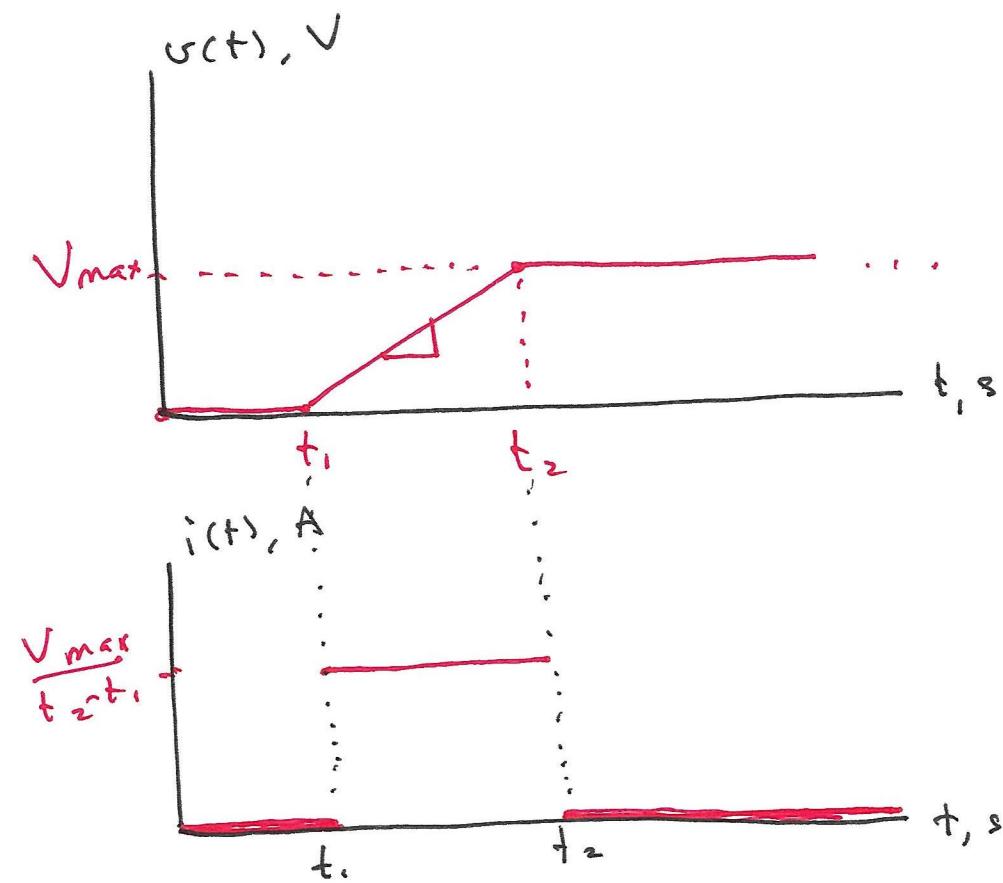

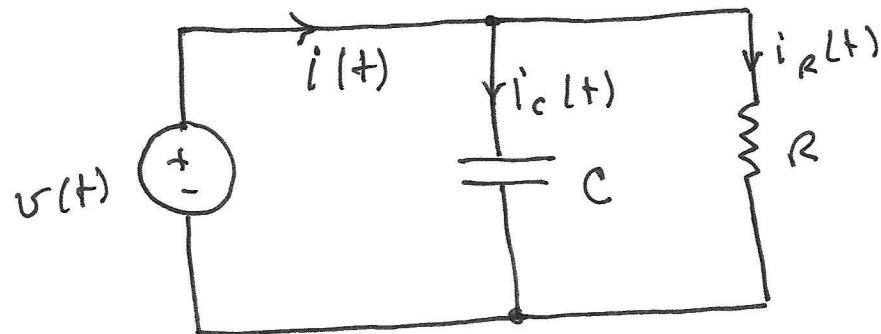
$$\dot{i} = \frac{V_{max}}{t_2 - t_1}, \quad t_1 < t < t_2$$






$$i_R(t) = \frac{v(t)}{R}$$

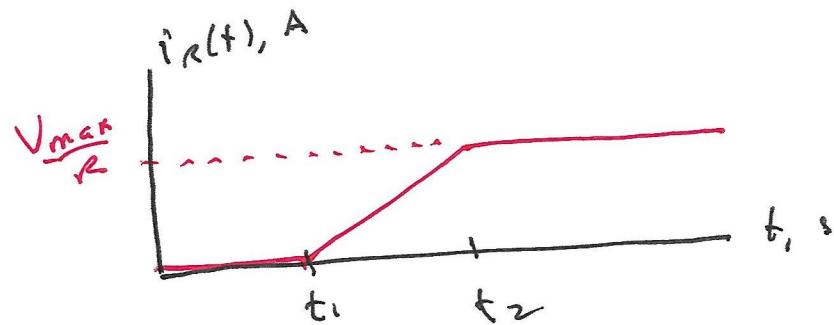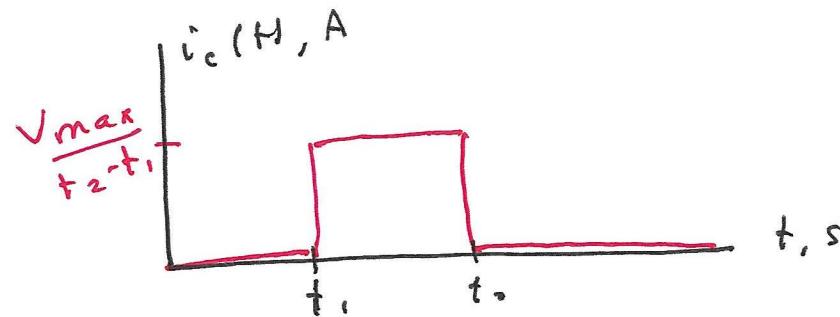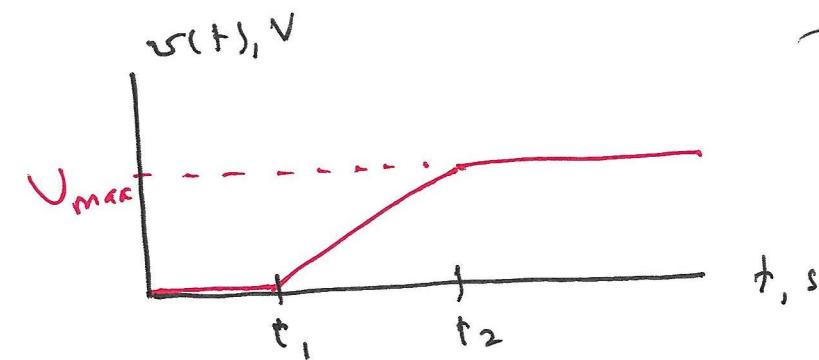

$$i(t) = i_c(t) + i_R(t)$$

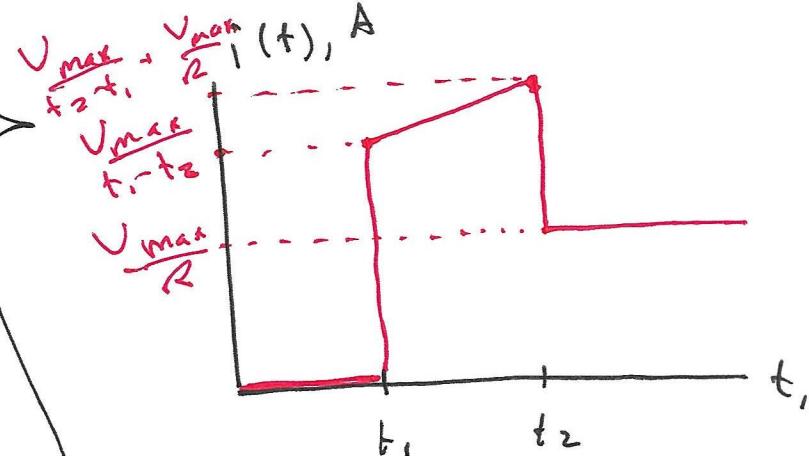


T

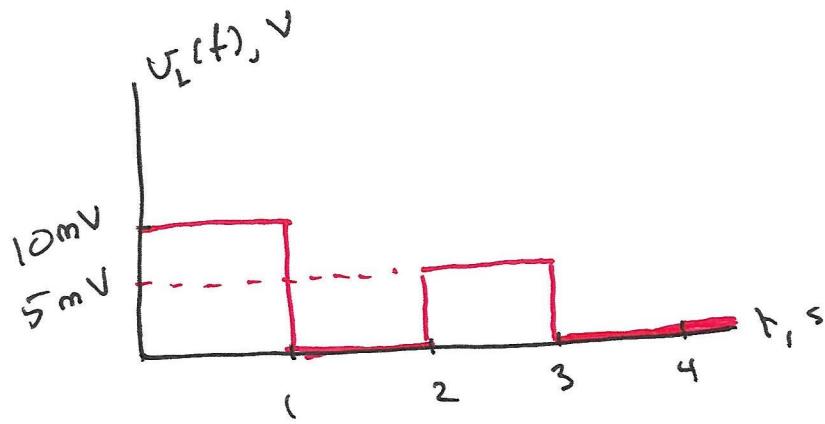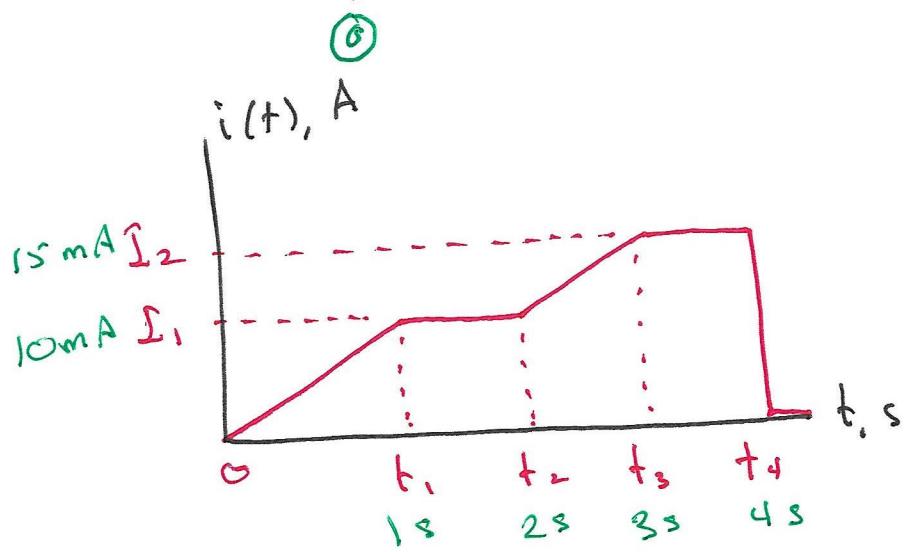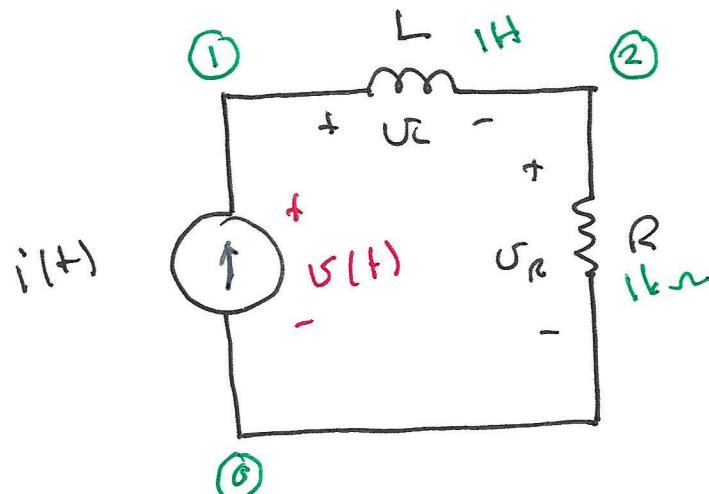

$$U_L = L \frac{di}{dt}$$


$$U_R = R i(t)$$

$$U_R(t), \text{V}$$

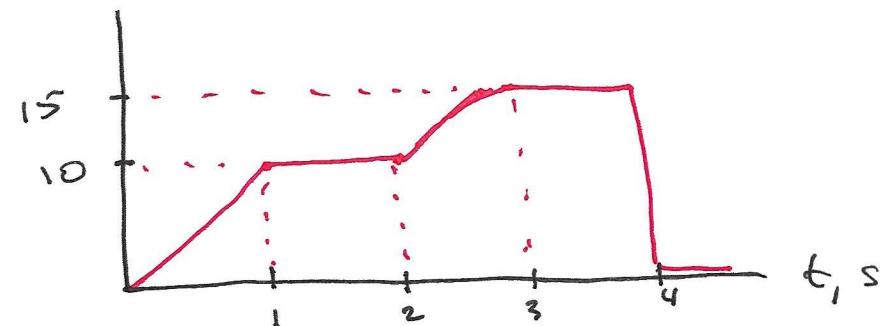

$$U(t) = U_R(t) + U_L(t)$$

$$U(t), \text{V}$$

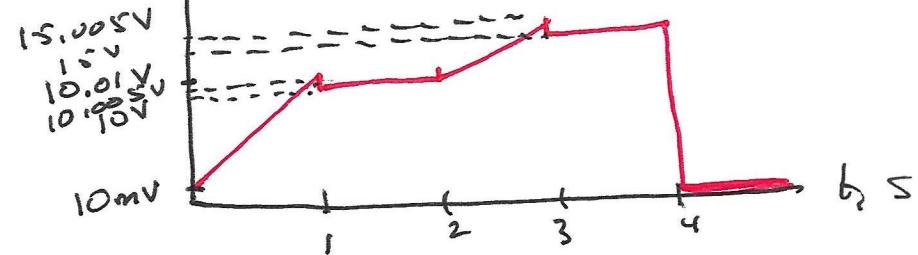

I 0 1 PWL(0 0, 1 10m, 2 10m, 3 15m, 4 15m,  
+ 4.001 0)  
L 1 2 1 IC=0  
R 2 0 1k  
.TRAN 5m