
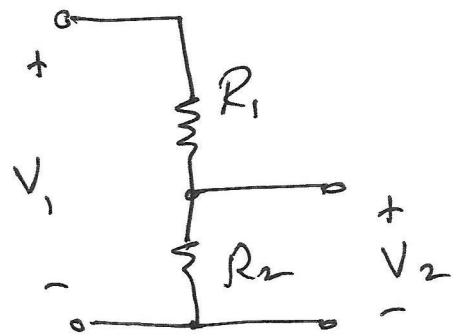


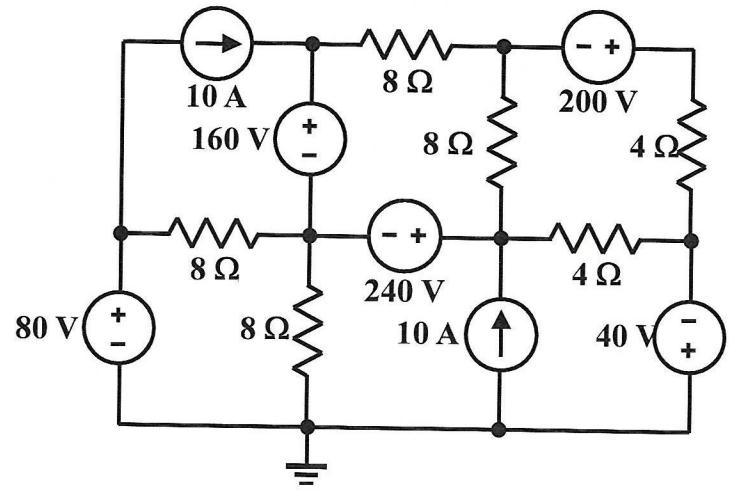
Symbolic Circuit Analysis with MATLAB (SCAM)




$$\frac{V_2}{V_1} = \frac{R_2}{R_1 + R_2}$$




Label components

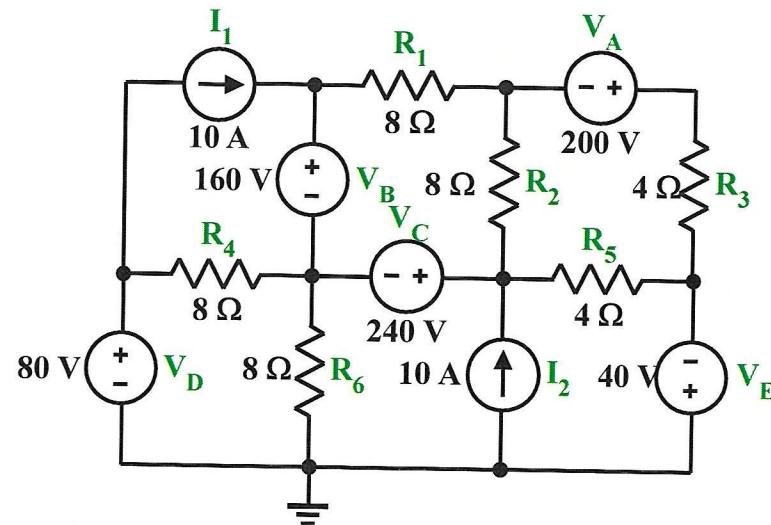

Label nodes

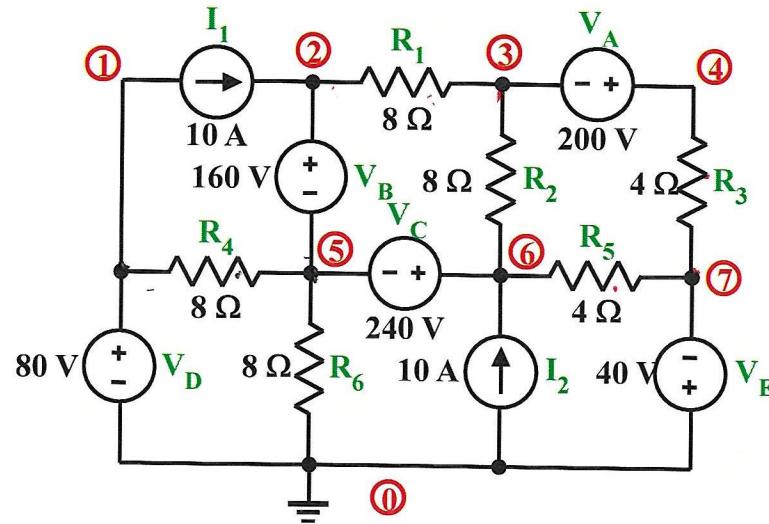

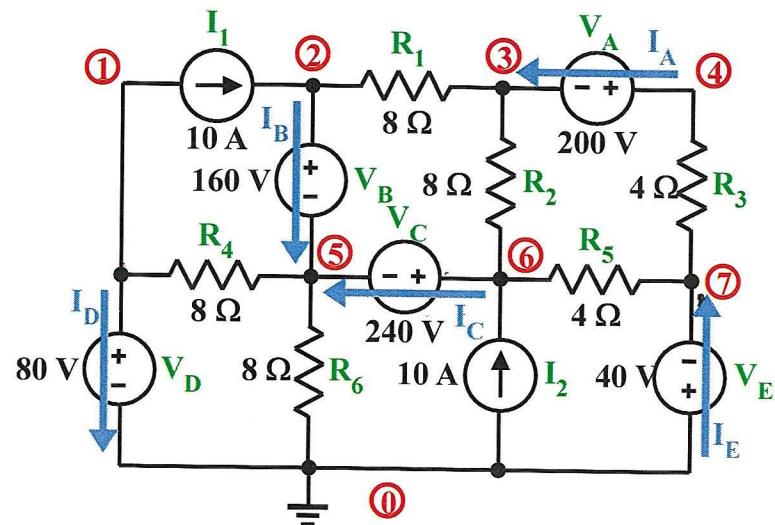Define voltage-source currents (must satisfy the PSC)



Write KCL at each node (except the reference node), with independent current sources on the rhs

$$\text{Node 1: } \frac{V_1 - V_5}{R_4} + I_D = -I_1$$

$$\text{Node 2: } \frac{V_2 - V_3}{R_1} + I_B = I_1$$

$$\text{Node 3: } \frac{V_3 - V_2}{R_1} + \frac{V_3 - V_6}{R_2} - I_A = 0$$

$$\text{Node 4: } I_A + \frac{V_4 - V_7}{R_3} = 0$$

$$\text{Node 5: } -I_B + \frac{V_5 - V_1}{R_4} + \frac{V_5 - V_6}{R_6} - I_C = 0$$

$$\text{Node 6: } I_C + \frac{V_6 - V_3}{R_2} + \frac{V_6 - V_7}{R_5} = I_2$$

$$\text{Node 7: } \frac{V_7 - V_4}{R_3} + \frac{V_7 - V_6}{R_5} - I_E = 0$$

$$\text{Node 0: } -I_D - \frac{V_5}{R_6} + I_E = -I_2$$

this is redundant

Write constraint equation for each voltage source

$$V_A: \quad V_3 - V_4 = V_A \quad \cancel{\text{X}}$$

$$V_B: \quad V_2 - V_5 = V_B$$

$$V_C: \quad V_6 - V_5 = V_C$$

$$V_D: \quad V_1 = V_D$$

$$V_E: \quad -V_7 = V_E$$

	V_1	V_2	V_3	V_4	V_5	V_6	V_7	I_A	I_B	I_C	I_D	I_E
N_1	$\frac{1}{R_4}$				$\frac{1}{R_4}$							1
N_2		$\frac{1}{R_1}$	$-\frac{1}{R_1}$						1			
N_3		$-\frac{1}{R_1}$	$\frac{1}{R_1}$	$\frac{1}{R_2}$			$-\frac{1}{R_2}$			-1		
N_4				$\frac{1}{R_3}$				$-\frac{1}{R_3}$	1			
N_5	$\frac{1}{R_4}$				$\frac{1}{R_4} + \frac{1}{R_5}$					-1	-1	
N_6				$-\frac{1}{R_2}$			$\frac{1}{R_2} + \frac{1}{R_5}$	$-\frac{1}{R_5}$			1	
N_7				$-\frac{1}{R_3}$			$-\frac{1}{R_5}$	$\frac{1}{R_3} + \frac{1}{R_5}$				-1
V_A			-1	1								
V_B		1			-1							
V_C					-1	1						
V_D	1											
V_E							-1					

$$\begin{array}{c}
 \mathbf{V}_1 \\
 \mathbf{V}_2 \\
 \mathbf{V}_3 \\
 \mathbf{V}_4 \\
 \mathbf{V}_5 \\
 \mathbf{V}_6 \\
 \mathbf{V}_7 \\
 \mathbf{I}_A \\
 \mathbf{I}_B \\
 \mathbf{I}_C \\
 \mathbf{I}_D \\
 \mathbf{I}_E
 \end{array}
 \times
 \begin{array}{c}
 -\mathbf{I}_1 \\
 \mathbf{I}_1 \\
 \mathbf{0} \\
 \mathbf{0} \\
 \mathbf{0} \\
 \mathbf{I}_2 \\
 \mathbf{0} \\
 \mathbf{V}_A \\
 \mathbf{V}_B \\
 \mathbf{V}_C \\
 \mathbf{V}_D \\
 \mathbf{V}_E
 \end{array}
 =
 \begin{array}{c}
 \mathbf{V}_1 \\
 \mathbf{I}_1 \\
 \mathbf{0} \\
 \mathbf{0} \\
 \mathbf{0} \\
 \mathbf{I}_2 \\
 \mathbf{0} \\
 \mathbf{V}_A \\
 \mathbf{V}_B \\
 \mathbf{V}_C \\
 \mathbf{V}_D \\
 \mathbf{V}_E
 \end{array}$$

A

```
>> fname="My_Example.cir";
>> ISU_scam
```

Started -- please be patient.

Netlist:

```
I1 1 2 10
R1 2 3 8
VA 4 3 200
VB 2 5 160
R2 3 6 8
R3 4 7 4
R4 1 5 8
VC 6 5 240
R5 6 7 4
VD 1 0 80
R6 5 0 8
I2 0 6 10
VE 0 7 40
```

The A matrix:

```
[ 1/R4,      0,      0,      0,      -1/R4,      0,      0,      0,      0,      0,      0,      0,      1,      0]
[ 0, 1/R1,      -1/R1,      0,      0,      0,      0,      0,      0,      0,      1,      0,      0,      0]
[ 0, -1/R1, 1/R1 + 1/R2,      0,      0,      0,      -1/R2,      0,      0,      -1,      0,      0,      0,      0]
[ 0,      0,      0, 1/R3,      0,      0,      0,      0,      -1/R3,      1,      0,      0,      0,      0]
[-1/R4,      0,      0,      0, 1/R4 + 1/R6,      0,      0,      0,      -1/R3,      1,      0,      0,      0,      0]
[ 0,      0,      -1/R2,      0,      0, 1/R2 + 1/R5,      0,      0,      0,      0,      -1,      -1,      0,      0]
[ 0,      0,      0, -1/R3,      0,      0,      -1/R5, 1/R3 + 1/R5,      0,      0,      0,      0,      0,      -1]
[ 0,      0,      -1,      1,      0,      0,      0,      0,      0,      0,      0,      0,      0,      0]
[ 0,      1,      0,      0,      -1,      0,      0,      0,      0,      0,      0,      0,      0,      0]
[ 0,      0,      0,      0,      -1,      1,      0,      0,      0,      0,      0,      0,      0,      0]
[ 1,      0,      0,      0,      0,      0,      0,      0,      0,      0,      0,      0,      0,      0]
[ 0,      0,      0,      0,      0,      0,      0,      0,      -1,      0,      0,      0,      0,      0]
```

The x vector:

v_1

```
v_2  
v_3  
v_4  
v_5  
v_6  
v_7  
I_VA  
I_VB  
I_VC  
I_VD  
I_VE
```

The z vector:

```
-I1  
I1  
0  
0  
0  
I2  
0  
VA  
VB  
VC  
VD  
VE
```

The matrix equation:

```
I_VD + v_1/R4 - v_5/R4 == -I1  
I_VB + v_2/R1 - v_3/R1 == I1  
v_3*(1/R1 + 1/R2) - v_2/R1 - v_6/R2 - I_VA == 0  
I_VA + v_4/R3 - v_7/R3 == 0  
v_5*(1/R4 + 1/R6) - I_VC - v_1/R4 - I_VB == 0  
I_VC - v_3/R2 - v_7/R5 + v_6*(1/R2 + 1/R5) == I2  
v_7*(1/R3 + 1/R5) - v_4/R3 - v_6/R5 - I_VE == 0  
v_4 - v_3 == VA
```

```

v_2 - v_5 == VB
v_6 - v_5 == VC
v_1 == VD
-v_7 == VE

```

The solution:

$v_1 == VD$

```

v_2 == (R1*R2*R4*R5*VB - R2*R4*R5*R6*VA - R1*R4*R5*R6*VA + R1*R2*R4*R6*VB + R1*R3*R4*R5*VB + R1*R2*R5*R6*VB
+ R1*R3*R4*R6*VB + R2*R3*R4*R5*VB + R1*R3*R5*R6*VB + R2*R3*R4*R6*VB + R1*R4*R5*R6*VB + R2*R3*R5*R6*VB -
R1*R2*R4*R6*VC - R1*R3*R4*R6*VC - R2*R3*R4*R6*VC - R1*R4*R5*R6*VC + R1*R2*R5*R6*VD + R1*R3*R5*R6*VD +
R2*R3*R5*R6*VD - R1*R2*R4*R6*VE - R1*R3*R4*R6*VE - R2*R3*R4*R6*VE - R1*R4*R5*R6*VE - R2*R4*R5*R6*VE +
I1*R1*R2*R4*R5*R6 + I1*R1*R3*R4*R5*R6 + I2*R1*R2*R4*R5*R6 + I1*R2*R3*R4*R5*R6 + I2*R1*R3*R4*R5*R6 +
I2*R2*R3*R4*R5*R6)/(R1*R2*R4*R5 + R1*R2*R4*R6 + R1*R3*R4*R5 + R1*R2*R5*R6 + R1*R3*R4*R6 + R2*R3*R4*R5 +
R1*R3*R5*R6 + R2*R3*R4*R6 + R1*R4*R5*R6 + R2*R3*R5*R6 + R2*R4*R5*R6)

v_3 == -(R1*R2*R4*R5*VA + R1*R2*R4*R6*VA + R1*R2*R5*R6*VA + R1*R4*R5*R6*VA + R2*R4*R5*R6*VA - R2*R3*R4*R5*VB
- R2*R3*R4*R6*VB - R2*R3*R5*R6*VB - R1*R3*R4*R5*VC - R1*R3*R5*R6*VC + R2*R3*R4*R6*VC - R1*R3*R5*R6*VD -
R2*R3*R5*R6*VD + R1*R2*R4*R5*VE + R1*R2*R4*R6*VE + R1*R2*R5*R6*VE + R1*R3*R4*R6*VE + R2*R3*R4*R6*VE +
R1*R4*R5*R6*VE + R2*R4*R5*R6*VE - I1*R1*R3*R4*R5*R6 - I1*R2*R3*R4*R5*R6 - I2*R1*R3*R4*R5*R6 -
I2*R2*R3*R4*R5*R6)/(R1*R2*R4*R5 + R1*R2*R4*R6 + R1*R3*R4*R5 + R1*R2*R5*R6 + R1*R3*R4*R6 + R2*R3*R4*R5 +
R1*R3*R5*R6 + R2*R3*R4*R6 + R1*R4*R5*R6 + R2*R3*R5*R6 + R2*R4*R5*R6)

v_4 == (R1*R3*R4*R5*VA + R1*R3*R4*R6*VA + R2*R3*R4*R5*VA + R1*R3*R5*R6*VA + R2*R3*R4*R6*VA + R2*R3*R5*R6*VA
+ R2*R3*R4*R5*VB + R2*R3*R4*R6*VB + R2*R3*R5*R6*VB + R1*R3*R4*R5*VC + R1*R3*R5*R6*VC - R2*R3*R4*R6*VC +
R1*R3*R5*R6*VD + R2*R3*R5*R6*VD - R1*R2*R4*R5*VE - R1*R2*R4*R6*VE - R1*R2*R5*R6*VE - R1*R3*R4*R6*VE -
R2*R3*R4*R6*VE - R1*R4*R5*R6*VE - R2*R4*R5*R6*VE + I1*R1*R3*R4*R5*R6 + I1*R2*R3*R4*R5*R6 + I2*R1*R3*R4*R5*R6
+ I2*R2*R3*R4*R5*R6)/(R1*R2*R4*R5 + R1*R2*R4*R6 + R1*R3*R4*R5 + R1*R2*R5*R6 + R1*R3*R4*R6 + R2*R3*R4*R5 +
R1*R3*R5*R6 + R2*R3*R4*R6 + R1*R4*R5*R6 + R2*R3*R5*R6 + R2*R4*R5*R6)

v_5 == -(R6*(R1*R4*R5*VA + R2*R4*R5*VA + R2*R4*R5*VB + R1*R2*R4*VC + R1*R3*R4*VC + R2*R3*R4*VC + R1*R4*R5*VC
- R1*R2*R5*VD - R1*R3*R5*VD - R2*R3*R5*VD + R1*R2*R4*VE + R1*R3*R4*VE + R2*R3*R4*VE + R1*R4*R5*VE +
R2*R4*R5*VE - I1*R1*R2*R4*R5 - I1*R1*R3*R4*R5 - I2*R1*R2*R4*R5 - I1*R2*R3*R4*R5 - I2*R1*R3*R4*R5 -
I2*R2*R3*R4*R5))/(R1*R2*R4*R5 + R1*R2*R4*R6 + R1*R3*R4*R5 + R1*R2*R5*R6 + R1*R3*R4*R6 + R2*R3*R4*R5 +
R1*R3*R5*R6 + R2*R3*R4*R6 + R1*R4*R5*R6 + R2*R3*R5*R6 + R2*R4*R5*R6)

```

```

v_6 == (R1*R2*R4*R5*VC - R2*R4*R5*R6*VA - R2*R4*R5*R6*VB - R1*R4*R5*R6*VA + R1*R3*R4*R5*VC + R1*R2*R5*R6*VC
+ R2*R3*R4*R5*VC + R1*R3*R5*R6*VC + R2*R3*R5*R6*VC + R2*R4*R5*R6*VC + R1*R2*R5*R6*VD + R1*R3*R5*R6*VD +
R2*R3*R5*R6*VD - R1*R2*R4*R6*VE - R1*R3*R4*R6*VE - R2*R3*R4*R6*VE - R1*R4*R5*R6*VE - R2*R4*R5*R6*VE +
I1*R1*R2*R4*R5*R6 + I1*R1*R3*R4*R5*R6 + I2*R1*R2*R4*R5*R6 + I1*R2*R3*R4*R5*R6 + I2*R1*R3*R4*R5*R6 +
I2*R2*R3*R4*R5*R6)/(R1*R2*R4*R5 + R1*R2*R4*R6 + R1*R3*R4*R5 + R1*R2*R5*R6 + R1*R3*R4*R6 + R2*R3*R4*R5 +
R1*R3*R5*R6 + R2*R3*R4*R6 + R1*R4*R5*R6 + R2*R3*R5*R6 + R2*R4*R5*R6)

v_7 == -VE

I_VA == -(R1*R4*R5*VA + R1*R4*R6*VA + R2*R4*R5*VA + R1*R5*R6*VA + R2*R4*R6*VA + R2*R5*R6*VA + R2*R4*R5*VB +
R2*R4*R6*VB + R2*R5*R6*VB + R1*R4*R5*VC + R1*R5*R6*VC - R2*R4*R6*VC + R1*R5*R6*VD + R2*R5*R6*VD +
R1*R4*R5*VE + R2*R4*R5*VE + R1*R5*R6*VE + R2*R5*R6*VE + I1*R1*R4*R5*R6 + I1*R2*R4*R5*R6 + I2*R1*R4*R5*R6 +
I2*R2*R4*R5*R6)/(R1*R2*R4*R5 + R1*R2*R4*R6 + R1*R3*R4*R5 + R1*R2*R5*R6 + R1*R3*R4*R6 + R2*R3*R4*R5 +
R1*R3*R5*R6 + R2*R3*R4*R6 + R1*R4*R5*R6 + R2*R3*R5*R6 + R2*R4*R5*R6)

I_VB == (R2*R4*R6*VC - R2*R4*R6*VA - R2*R5*R6*VA - R2*R4*R5*VB - R2*R4*R6*VB - R3*R4*R5*VB - R2*R5*R6*VB -
R3*R4*R6*VB - R3*R5*R6*VB - R4*R5*R6*VB - R2*R4*R5*VA + R3*R4*R5*VC + R3*R4*R6*VC + R3*R5*R6*VC +
R4*R5*R6*VC - R2*R5*R6*VD - R2*R4*R5*VE - R2*R5*R6*VE + I1*R1*R2*R4*R5 + I1*R1*R2*R4*R6 + I1*R1*R3*R4*R5 +
I1*R1*R2*R5*R6 + I1*R1*R3*R4*R6 + I1*R2*R3*R4*R5 + I1*R1*R3*R5*R6 + I1*R2*R3*R4*R6 + I1*R1*R4*R5*R6 +
I1*R2*R3*R5*R6 - I2*R2*R4*R5*R6)/(R1*R2*R4*R5 + R1*R2*R4*R6 + R1*R3*R4*R5 + R1*R2*R5*R6 + R1*R3*R4*R6 +
R2*R3*R4*R5 + R1*R3*R5*R6 + R2*R3*R4*R6 + R1*R4*R5*R6 + R2*R3*R5*R6 + R2*R4*R5*R6)

I_VC == -(R1*R4*R5*VA + R1*R5*R6*VA - R2*R4*R6*VA - R2*R4*R6*VB - R3*R4*R5*VB - R3*R4*R6*VB - R3*R5*R6*VB -
R4*R5*R6*VB + R1*R2*R4*VC + R1*R3*R4*VC + R1*R2*R6*VC + R2*R3*R4*VC + R1*R3*R6*VC + R1*R4*R5*VC +
R2*R3*R6*VC + R1*R5*R6*VC + R2*R4*R6*VC + R3*R4*R5*VC + R3*R4*R6*VC + R3*R5*R6*VC + R4*R5*R6*VC +
R1*R2*R6*VD + R1*R3*R6*VD + R2*R3*R6*VD + R1*R5*R6*VD + R1*R2*R4*VE + R1*R3*R4*VE + R1*R2*R6*VE +
R2*R3*R4*VE + R1*R3*R6*VE + R1*R4*R5*VE + R2*R3*R6*VE + R1*R5*R6*VE + I1*R1*R2*R4*R6 - I2*R1*R2*R4*R5 +
I1*R1*R3*R4*R6 - I2*R1*R3*R4*R5 + I1*R2*R3*R4*R6 - I2*R1*R2*R5*R6 - I2*R2*R3*R4*R5 + I1*R1*R4*R5*R6 -
I2*R1*R3*R5*R6 - I2*R2*R3*R5*R6 - I2*R2*R4*R5*R6)/(R1*R2*R4*R5 + R1*R2*R4*R6 + R1*R3*R4*R5 + R1*R2*R5*R6 +
R1*R3*R4*R6 + R2*R3*R4*R5 + R1*R3*R5*R6 + R2*R3*R4*R6 + R1*R4*R5*R6 + R2*R3*R5*R6 + R2*R4*R5*R6)

I_VD == -(R1*R5*R6*VA + R2*R5*R6*VA + R2*R5*R6*VB + R1*R2*R6*VC + R1*R3*R6*VC + R2*R3*R6*VC + R1*R5*R6*VC +
R1*R2*R5*VD + R1*R2*R6*VD + R1*R3*R5*VD + R1*R3*R6*VD + R2*R3*R5*VD + R2*R3*R6*VD + R1*R5*R6*VD +
R2*R5*R6*VD + R1*R2*R6*VE + R1*R3*R6*VE + R2*R3*R6*VE + R1*R5*R6*VE + R2*R5*R6*VE + I1*R1*R2*R4*R5 +
I1*R1*R2*R4*R6 + I1*R1*R3*R4*R5 + I1*R1*R3*R4*R6 + I1*R2*R3*R4*R5 + I1*R2*R3*R4*R6 - I2*R1*R2*R5*R6 +
I1*R1*R4*R5*R6 - I2*R1*R3*R5*R6 + I1*R2*R4*R5*R6 - I2*R2*R3*R5*R6)/(R1*R2*R4*R5 + R1*R2*R4*R6 + R1*R3*R4*R5

```

```

+ R1*R2*R5*R6 + R1*R3*R4*R6 + R2*R3*R4*R5 + R1*R3*R5*R6 + R2*R3*R4*R6 + R1*R4*R5*R6 + R2*R3*R5*R6 +
R2*R4*R5*R6)

I_VE == -(R1*R4*R5*VA + R2*R4*R5*VA
+ R1*R5*R6*VA + R2*R5*R6*VA + R2*R4*R5*VB + R2*R5*R6*VB + R1*R2*R4*VC + R1*R3*R4*VC + R1*R2*R6*VC +
R2*R3*R4*VC + R1*R3*R6*VC + R1*R4*R5*VC + R2*R3*R6*VC + R1*R5*R6*VC + R1*R2*R6*VD + R1*R3*R6*VD +
R2*R3*R6*VD + R1*R5*R6*VD + R2*R5*R6*VD + R1*R2*R4*VE + R1*R3*R4*VE + R1*R2*R6*VE + R2*R3*R4*VE +
R1*R3*R6*VE + R1*R4*R5*VE + R2*R3*R6*VE + R2*R4*R5*VE + R1*R5*R6*VE + R2*R5*R6*VE + I1*R1*R2*R4*R6 +
I1*R1*R3*R4*R6 + I2*R1*R2*R4*R6 + I1*R2*R3*R4*R6 + I2*R1*R3*R4*R6 + I1*R1*R4*R5*R6 + I2*R2*R3*R4*R6 +
I1*R2*R4*R5*R6 + I2*R1*R4*R5*R6 + I2*R2*R4*R5*R6)/(R1*R2*R4*R5 + R1*R2*R4*R6 + R1*R3*R4*R5 + R1*R2*R5*R6 +
R1*R3*R4*R6 + R2*R3*R4*R5 + R1*R3*R5*R6 + R2*R3*R4*R6 + R1*R4*R5*R6 + R2*R3*R5*R6 + R2*R4*R5*R6)

```

Elapsed time is 4.00561 seconds.


>> eval(z)

>> eval(v-1)
 ↑ lower case

simplify(v-1)


Controlled Sources

VCVS

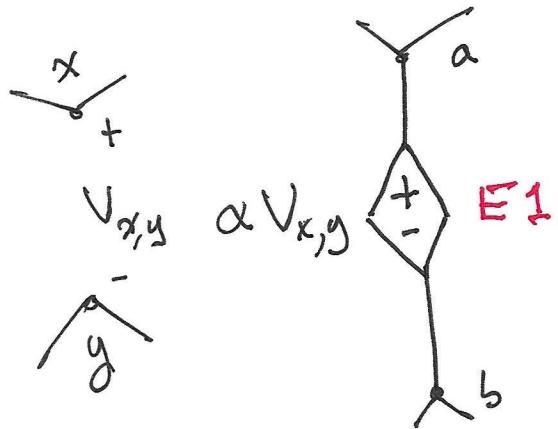



$$E1 \quad a \quad b \quad x \quad g \quad a$$

VCCS

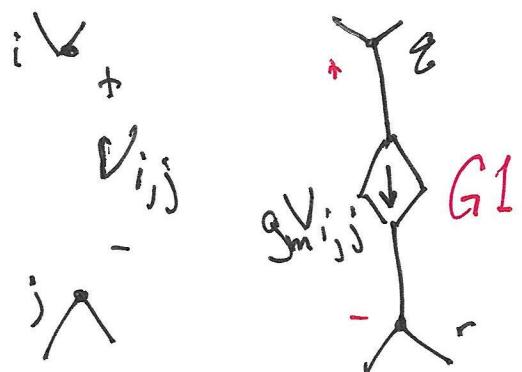



$$G1 \quad + \quad - \quad i \quad j \quad g_m$$

CCVS

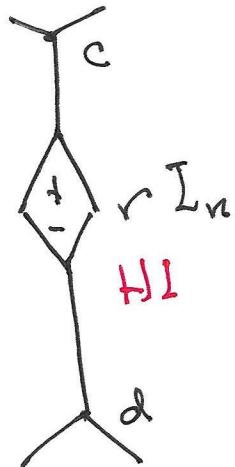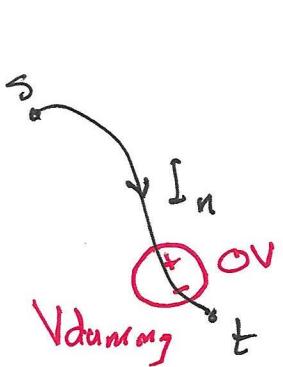

H1 c d V_{dummy} r
 V_{dummy} s t DC o

CCCS

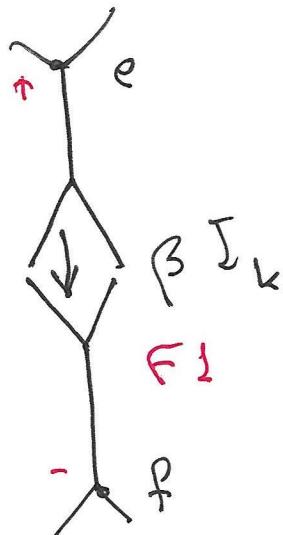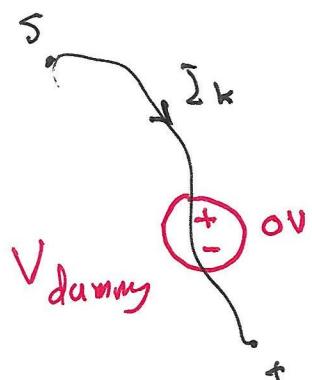

F1 e f V_{dummy} β
 V_{dummy} s t DC o