
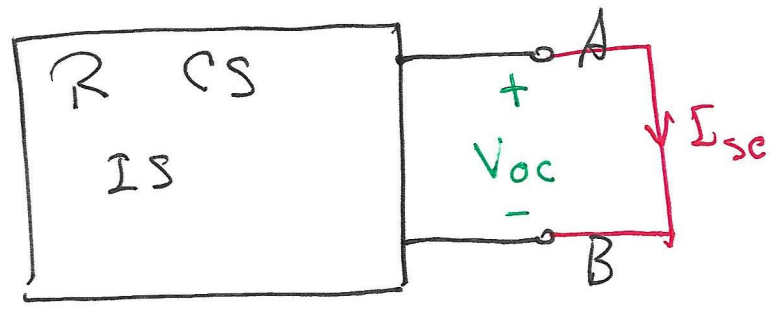


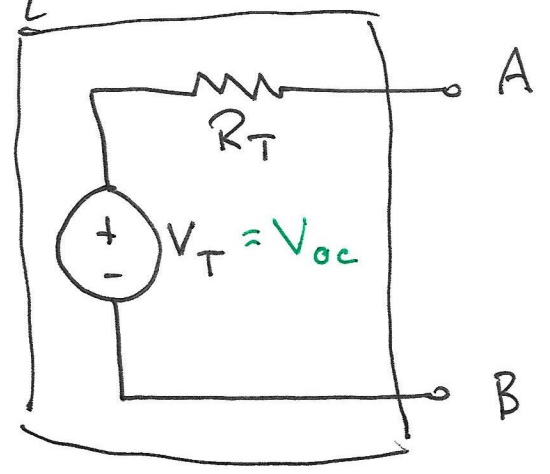
Final Exam is due Tuesday, December 14
by 9:30 AM.




Thevenin
Equivalent



Norton
Equivalent

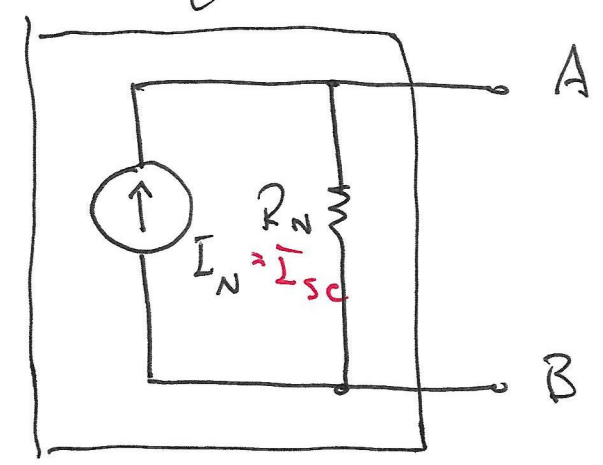

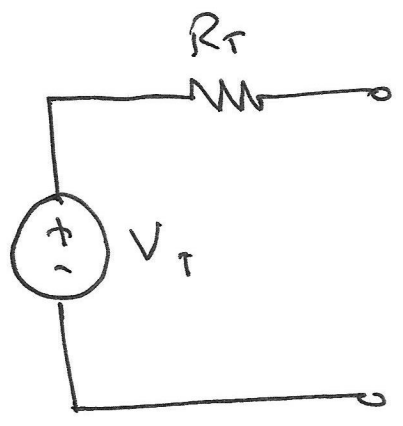
$$\frac{V_{oc}}{I_{sc}} = R_N = R_T = \frac{V_{oc}}{I_{sc}}$$




Thevenin


\Rightarrow

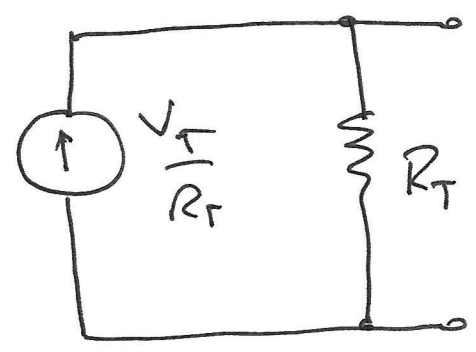


Norton

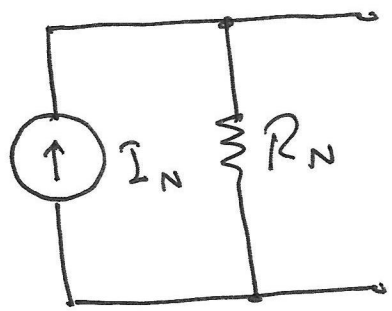


\Rightarrow

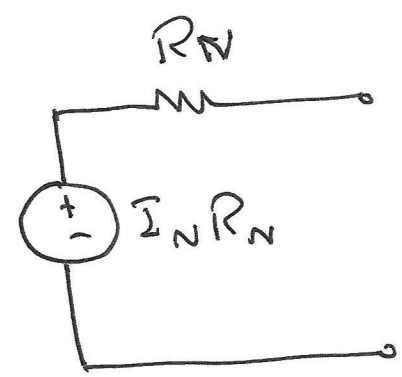


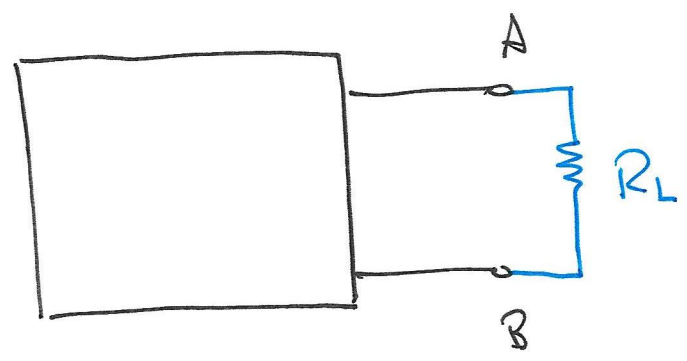

To get maximum power delivered to the load, set


$$R_L = R_T = R_N$$

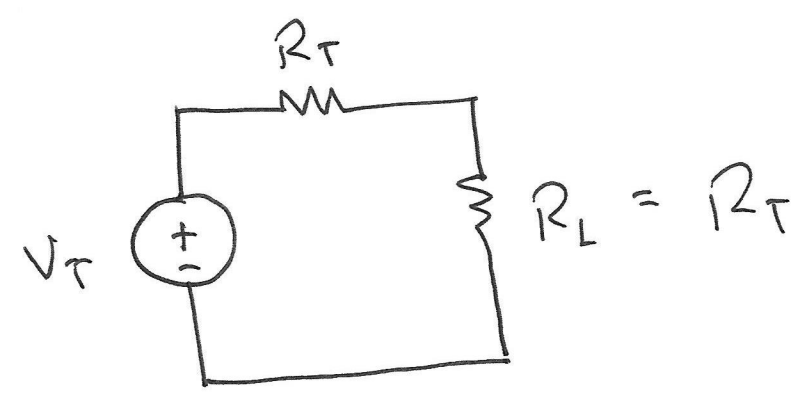

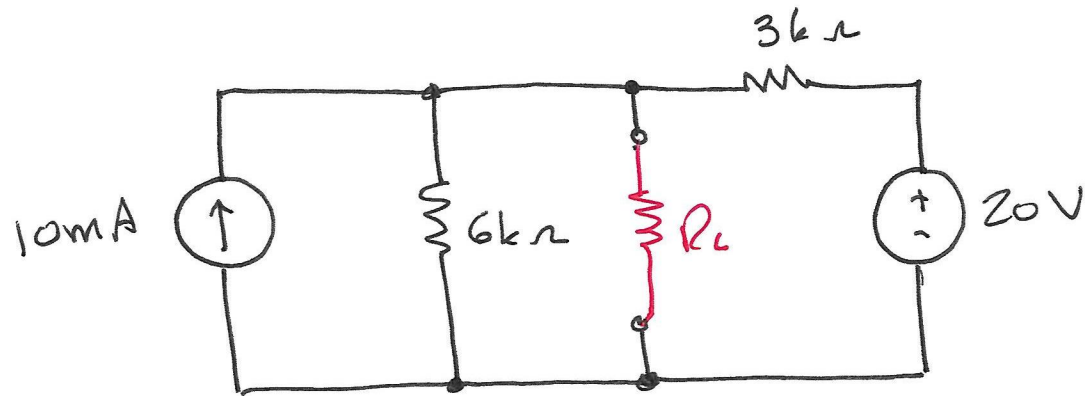


What value should I choose for R_L so that it absorbs maximum power?

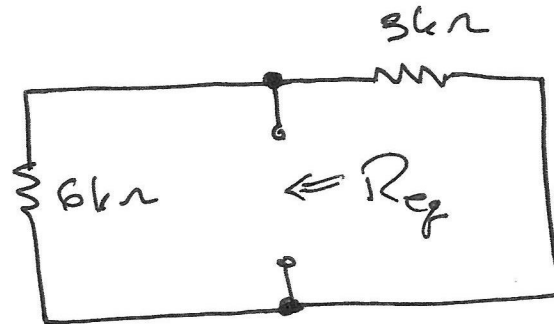To find R_T or R_N , turn off all independent sources and calculate the equivalent resistance w.r.t. the ~~the~~ load terminals.






$$R_{eq} = 6k\Omega \parallel 3k\Omega = 2k\Omega$$
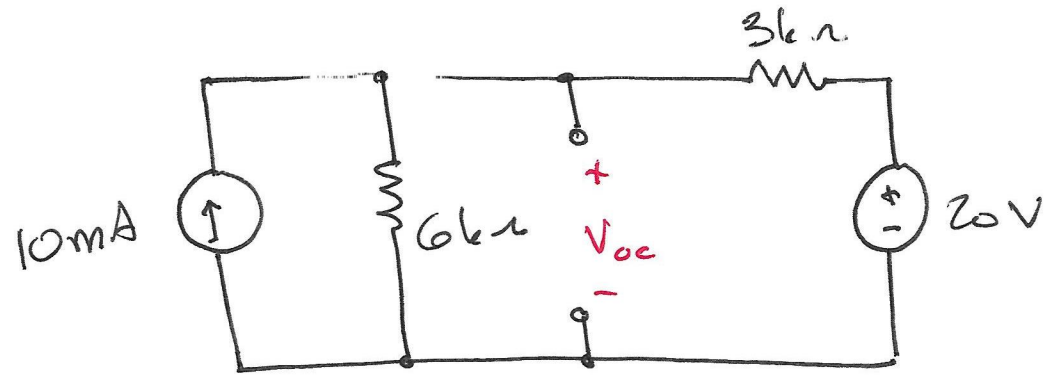
$$R_T = R_N = 2k\Omega \Rightarrow R_L = 2k\Omega \text{ for max. power.}$$




$V_T = V_{OC}$

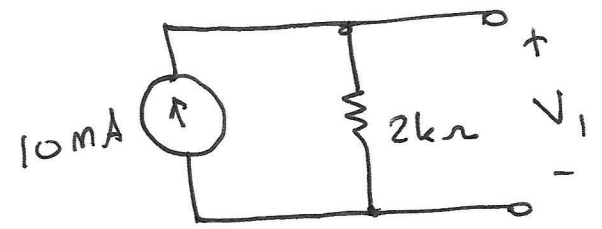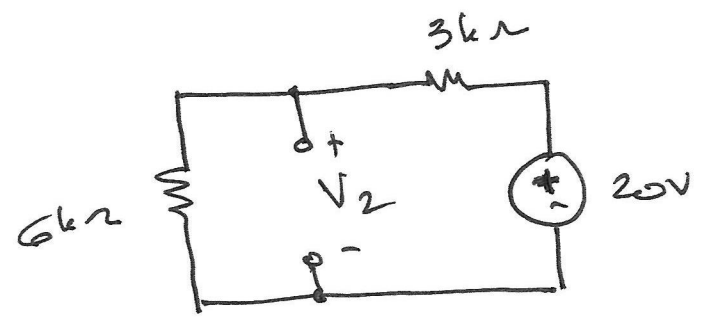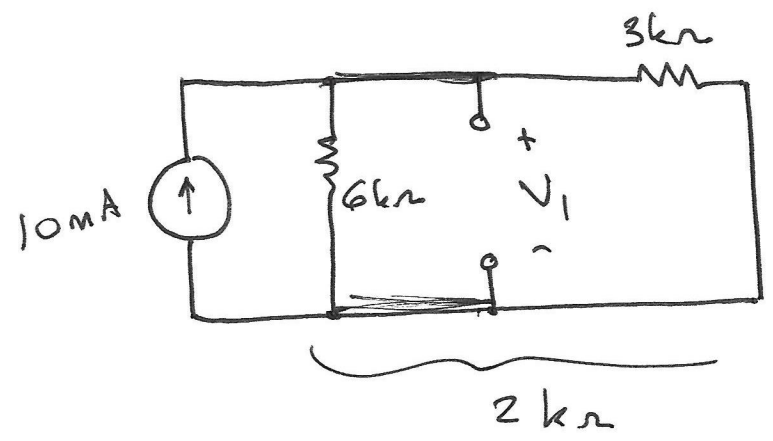

$V_1 = (10mA \times 2k\Omega) = 20V$

$V_2 = \frac{6}{9} \cdot 20V$
 $= \frac{40}{3} V$

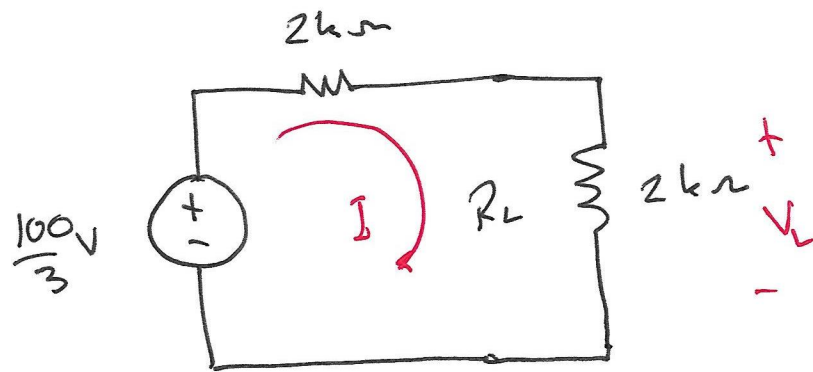$V_{OC} = V_1 + V_2$
 $= 20 + \frac{40}{3}$
 $= \frac{100}{3} V$



$$P_L = ?$$

$$I = \frac{25}{3} \text{ mA}$$

$$V_L = \frac{50}{3} \text{ V}$$

$P = VI$ where V and I satisfy the PSC.
abs.


But $V = RI$

$$= RI^2$$

or $I = \frac{V}{R}$

$$= \frac{V^2}{R}$$
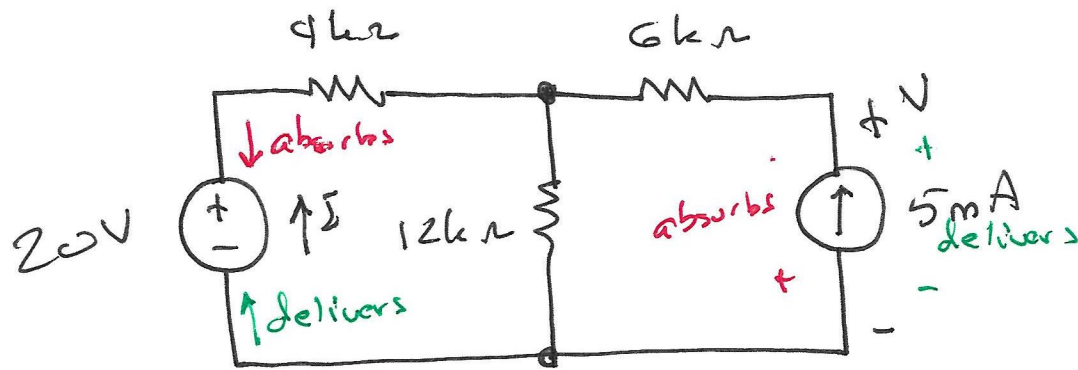
$$P_L = \left(\frac{25}{3} \text{ mA}\right)^2 (2k\Omega) \quad \text{or} \quad \frac{\left(\frac{50}{3}\right)^2}{2k\Omega}$$





8
Which components absorb power, and which deliver power?

Do they satisfy the PSC, or not?

If yes, they absorb power

If no, they deliver power.

The superposition theorem:

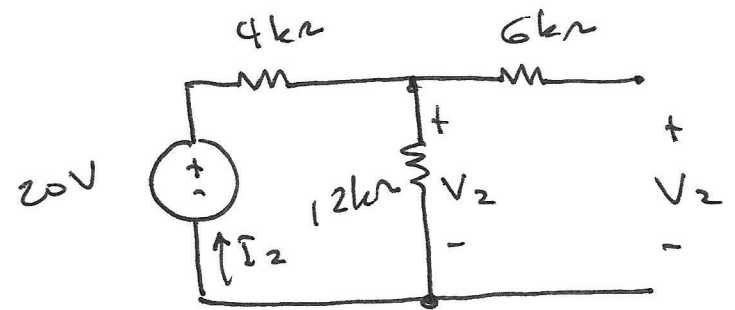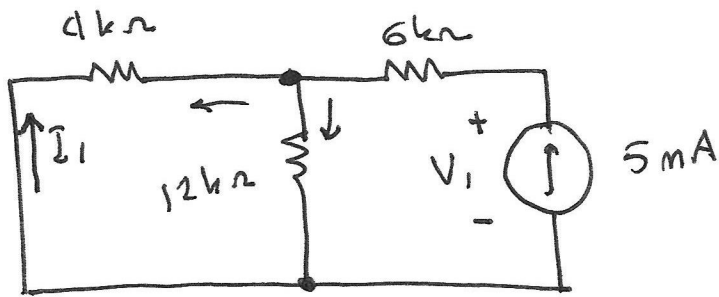

$$I = I_1 + I_2$$

$$V = V_1 + V_2$$

$$I_1 = -\frac{12}{16} \cdot 5 \text{ mA} = -\frac{15}{4} \text{ mA}$$

$$V_1 = (6 \text{ k}\Omega)(5 \text{ mA}) = 45 \text{ V}$$

If $I > 0$, the voltage source delivers power

If $V > 0$, the current source delivers power

$$I_2 = \frac{20 \text{ V}}{16 \text{ k}\Omega} = \frac{5}{4} \text{ mA}$$

$$V_2 = \frac{12}{16} \cdot 20 \text{ V} = 15 \text{ V}$$

$$I = I_1 + I_2 = -\frac{15}{4} \text{ mA} + \frac{5}{4} \text{ mA} = -\frac{10}{4} \text{ mA} = -\frac{5}{2} \text{ mA}$$

\Rightarrow the voltage source satisfies the PSC and
 \therefore absorbs power

$$V = V_1 + V_2 = 45 \text{ V} + 15 \text{ V} = 60 \text{ V}$$

\Rightarrow the current source does not satisfy the PSC and delivers power.