

Name _____
 By writing or printing my name in the space above, I hereby affirm that I have neither given nor received assistance in preparing solutions for this exam.

EE 2240
Exam #2

Due by 8:00AM, Tuesday, November 9, 2021


[open book, open notes, calculator and computer allowed – no internet access]

Work must be neat, orderly, and complete in order to receive partial credit.

LTspice solutions are not allowed.

PLEASE submit your solutions as a single PDF file.

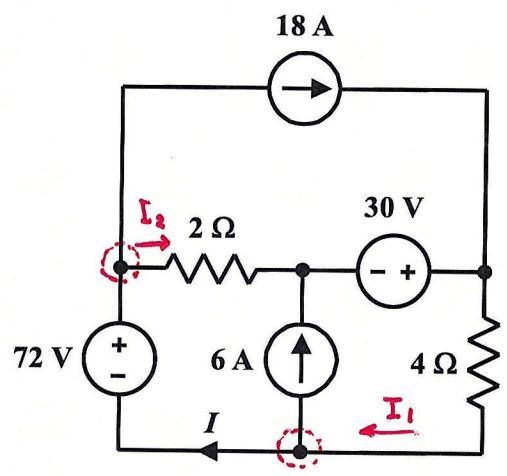- Determine the numerical value of the current I .



$$I_1 = I + 6 \quad (\text{KCL})$$

$$I_2 = I - 18 \quad (\text{KCL})$$

$$-72 + 2I_2 - 30 + 4I_1 = 0 \quad (\text{KVL})$$


$$\Rightarrow -72 + 2(I - 18) - 30 + 4(I + 6) = 0$$

$$6I = 114$$

$$I = 19 \text{ A}$$

2. Determine the numerical value of the voltage V_o .

Method 1

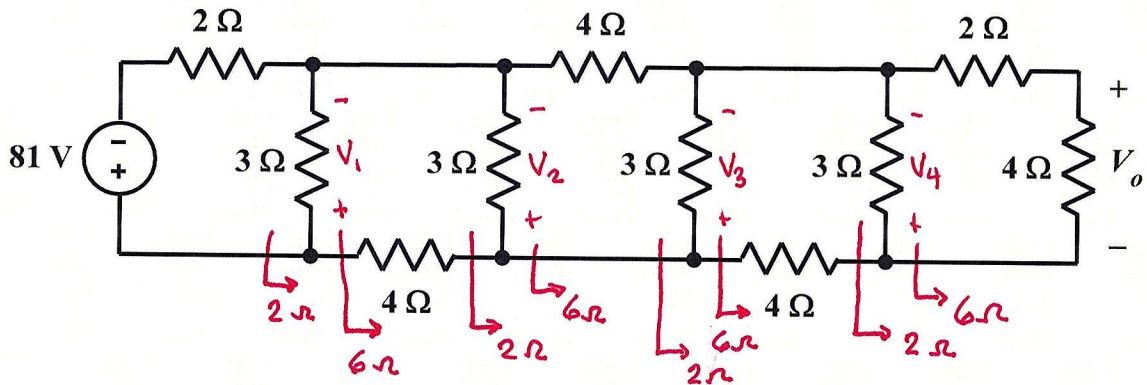

$$V_1 = \frac{2}{2+2} (81) = 40.5 \text{ V}$$

$$V_2 = \frac{2}{4+2} (40.5) = 13.5 \text{ V}$$


$$V_3 = \frac{2}{4+2} (13.5) = 4.5 \text{ V}$$

$$V_4 = \frac{2}{4+2} (4.5) = 1.5 \text{ V}$$

$$V_o = - \frac{4}{4+2} (1.5) = -1 \text{ V}$$

2. Determine the numerical value of the voltage V_o .

Method 2

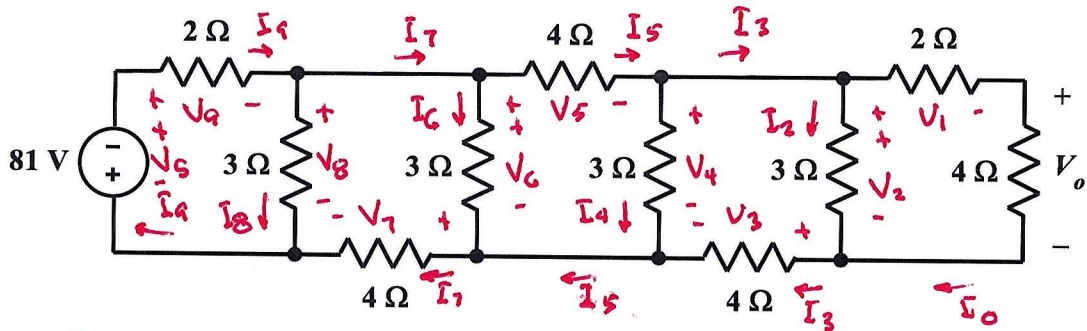

Guess $V_o = 4V$

Then $I_o = 1A$

$V_1 = 2V$

$V_2 = 6V$

$I_2 = 2A$

$I_3 = 3A$

$V_3 = 12V$

$V_4 = 18V$

$I_4 = 6A$

$I_5 = 9A$

$V_5 = 36V$

$V_6 = 54V$

$I_6 = 18A$

$I_7 = 27A$

$V_7 = 108V$

$V_8 = 162V$

$I_8 = 54A$

$I_9 = 81A$



$V_9 = 162V$

$V_5 = 324V$

$$\frac{V_o}{4V} = \frac{-81V}{324V}$$

$\Rightarrow V_o = -1V$

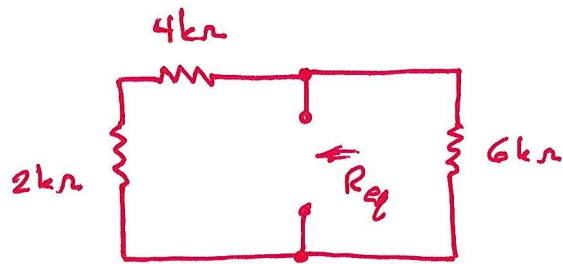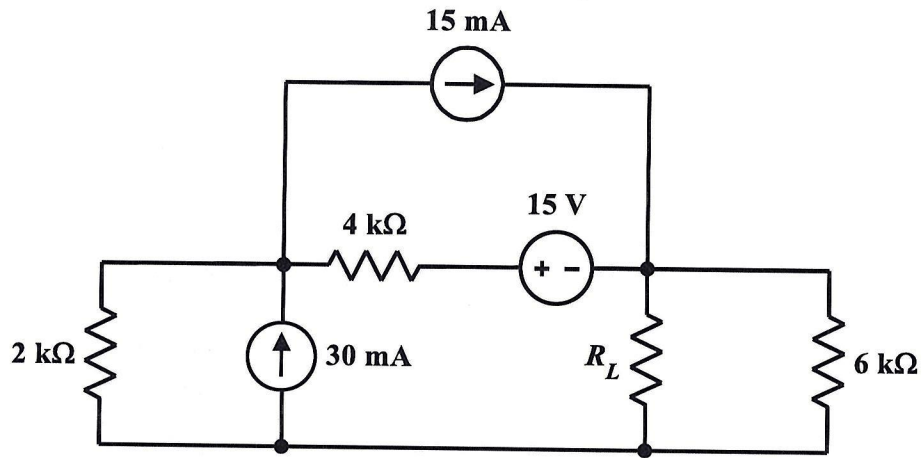
3. Determine the value of R_L that will absorb maximum power from the remainder of the circuit.



$$R_L = R_N = R_T = 6\text{ k}\Omega \parallel (4\text{ k}\Omega + 2\text{ k}\Omega)$$

$$= 3\text{ k}\Omega$$

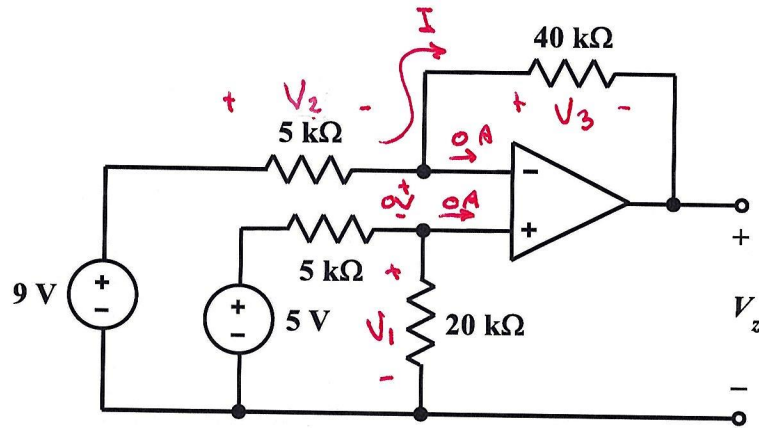4. Determine the numerical value of the voltage V_z .



$$V_1 = \frac{20k\Omega}{5k\Omega + 20k\Omega} \cdot 5V = 4V$$

$$V_2 = 9V - V_1 = 5V$$

$$I = \frac{5V}{5k\Omega} = 1mA$$

$$V_3 = (40k\Omega) I = 40V$$

$$V_z = -40 + 0 + 4 = -36V$$