

EE 2240
Final Exam
Fall 2021

Please read these comments and instructions before starting the exam:

This is a **take-home** exam. You may use any resources you wish, with the exception of human consultants.

There are 6 problems, each worth a maximum of 25 points. Very little partial credit will be given, so please take your time and check your work.

Clearly and completely define any variables you add to a problem for use in your solution. (Show them, along with your assumed reference direction or polarity if appropriate, on the circuit diagram.). Also, make a special effort to present your solutions in a neat and orderly manner. If a solution is difficult to follow, it's not worth as many points as one that is easy to follow.

Your solutions are due on Tuesday, December 14, by 9:30AM.

No extensions will be granted.


The solutions you submit must be done by hand. LTspice, MATLAB, and other tools may be used to check your work if you wish, but they may not be used to generate the solutions you submit for grading.

***PLEASE* submit your solutions as a single PDF file.**

Name _____

By writing or printing my name in the space above, I hereby affirm that I have neither given nor received assistance in preparing my solution for this problem.

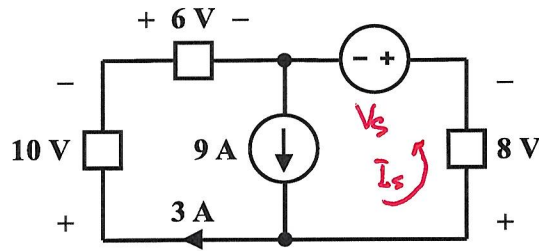1. Is the independent voltage source *absorbing* or *delivering* power? How much? Show work to justify your answers.



$$V_s = -8 + 10 + 6 = 8 \text{ V}$$

$$I_s = 9 - 3 = 6 \text{ A}$$

V_s and I_s do satisfy the Passive Sign Convention.


Therefore, the independent voltage source absorbs

$$(8 \text{ V})(6 \text{ A}) = 48 \text{ W}$$


Name _____

By writing or printing my name in the space above, I hereby affirm that I have neither given nor received assistance in preparing my solution for this problem.

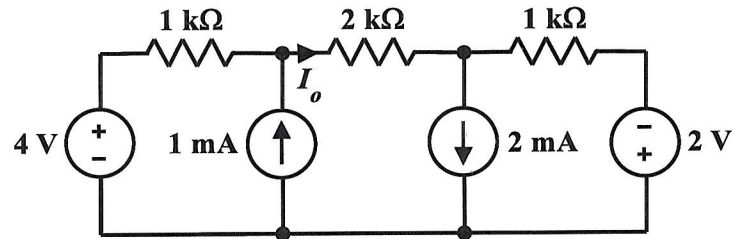
2. Find the numerical value, including sign, of I_o .




↓ source transformation ↓

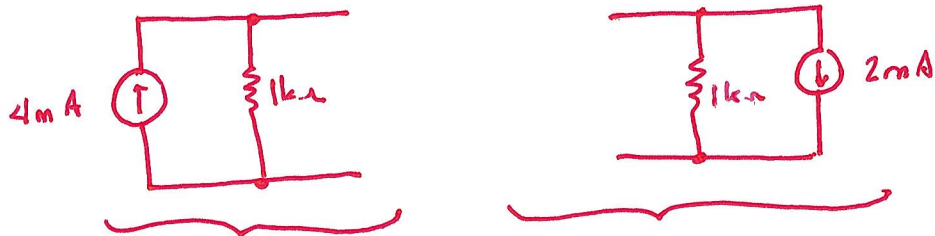

↓ combine current sources ↓

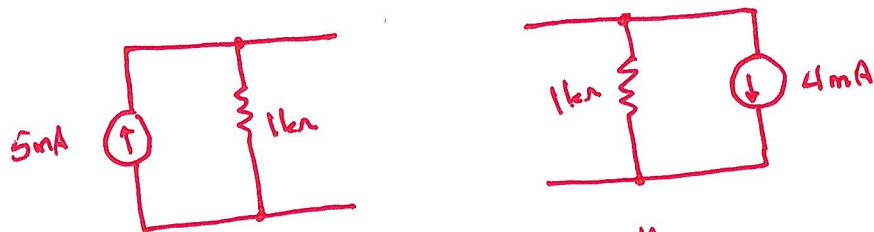

↓ source transformation ↓

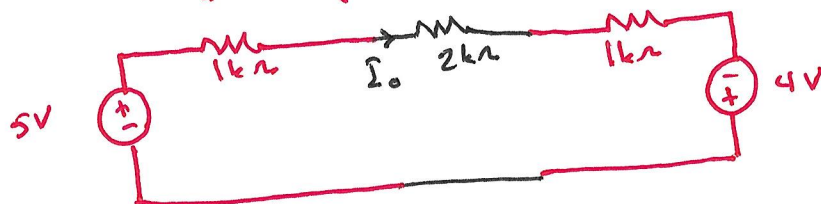

KVL: $(1\text{ k}\Omega + 2\text{ k}\Omega + 1\text{ k}\Omega) I_o = 5\text{ V} + 4\text{ V}$


$$I_o = \frac{9\text{ V}}{4\text{ k}\Omega} = 2.25\text{ mA}$$

or $\frac{9}{4}\text{ mA}$

Name _____

By writing or printing my name in the space above, I hereby affirm that I have neither given nor received assistance in preparing my solution for this problem.

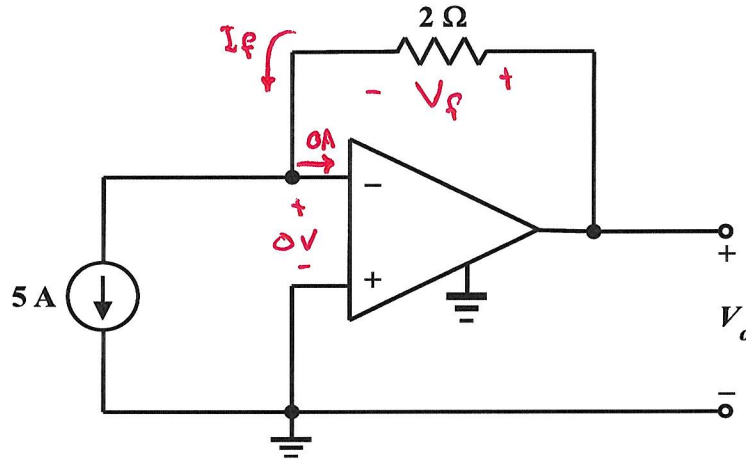3. The operational amplifier is ideal. Determine the numerical value, including sign, of V_o .



$$I_f = 5\text{ A} + 0\text{ A} = 5\text{ A}$$


$$V_f = (2\ \Omega) I_f = 10\text{ V}$$

$$V_o = V_f + 0 = 10\text{ V}$$

Name _____

By writing or printing my name in the space above, I hereby affirm that I have neither given nor received assistance in preparing my solution for this problem.

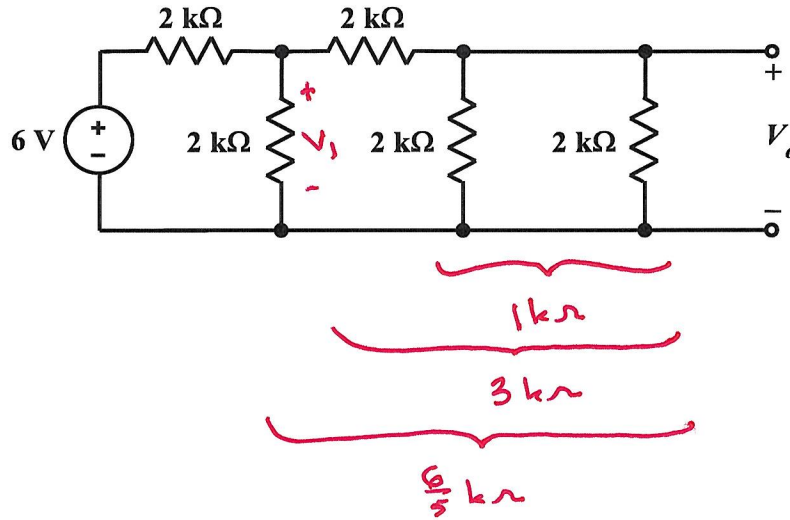4. Find the numerical value, including sign, of V_o .




$$V_1 = \frac{6/5}{2 + 6/5} \cdot 6V = \frac{3}{8} \cdot 6V = \frac{9}{4} V$$

$$V_o = \frac{1}{2+1} \cdot V_1 = \frac{3}{4} V$$

Name _____

By writing or printing my name in the space above, I hereby affirm that I have neither given nor received assistance in preparing my solution for this problem.

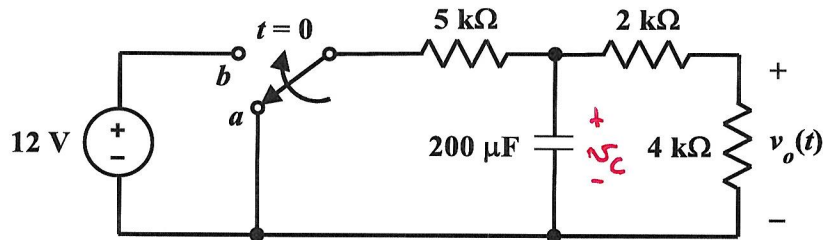5. The switch has been in position a for a long time, and is suddenly thrown to position b at $t = 0$. Find $v_o(t)$ for $t \geq 0$.



$$v_c(0) = 0 \text{ V}$$

$$v_c(\infty) = \frac{2+4}{5+2+4} \cdot 12 \text{ V} = \frac{72}{11} \text{ V}$$

$$\begin{aligned} \tau &= [5 \text{ k}\Omega \parallel (2 \text{ k}\Omega + 4 \text{ k}\Omega)] (200 \mu\text{F}) \\ &= \left(\frac{30}{11} \text{ k}\Omega\right) (200 \mu\text{F}) = \frac{6}{11} \text{ ms} \end{aligned}$$

$$\begin{aligned} v_c(t) &= [v_c(0) - v_c(\infty)] e^{-t/\tau} + v_c(\infty) \\ &= -\frac{72}{11} e^{-\frac{5500}{3}t} + \frac{72}{11} \\ &= \frac{72}{11} \left(1 - e^{-\frac{5500}{3}t}\right) \text{ V}, \quad t \geq 0 \end{aligned}$$


$$v_o(t) = \frac{4}{6} v_c(t)$$

$$= \frac{48}{11} \left(1 - e^{-\frac{5500}{3}t}\right) \text{ V}, \quad t \geq 0$$

Name _____

By writing or printing my name in the space above, I hereby affirm that I have neither given nor received assistance in preparing my solution for this problem.

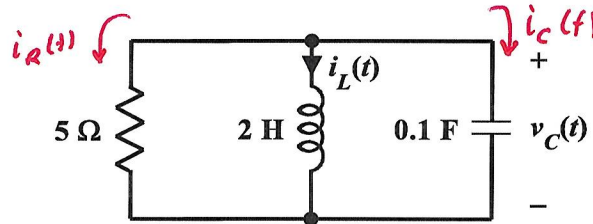6. The circuit shown below is an underdamped system, and the current through the inductor has the form $i_L(t) = e^{\alpha t} (K_1 \sin \omega t + K_2 \cos \omega t)$ A for $t \geq 0$.



- a. Determine the numerical values, including signs, of α and ω .

$$v_C(t) = (2 \text{ H}) \frac{di_L}{dt}$$

$$i_C(t) = (0.1 \text{ F}) \frac{dv_C}{dt} = 0.2 \frac{d^2 i_L}{dt^2}$$

$$i_R(t) = \frac{v_C(t)}{5 \Omega} = 0.2 v_C(t) = 0.4 \frac{di_L}{dt}$$

$$\text{KCL: } i_C(t) + i_R(t) + i_L(t) = 0.2 \frac{d^2 i_L}{dt^2} + 0.4 \frac{di_L}{dt} + i_L = 0$$

$$\text{or } \frac{d^2 i_L}{dt^2} + 2 \frac{di_L}{dt} + 5 i_L = 0 \Rightarrow r^2 + 2r + 5 = 0$$

$$\text{or } (r+1)^2 + 2^2 = 0$$

- b. If the initial conditions are $i_L(0) = 1 \text{ A}$ and $v_C(0) = 12 \text{ V}$, determine the numerical values, including signs, of K_1 and K_2 . $\therefore \alpha = -1$

$$\therefore i_L(t) = e^{-t} (K_1 \sin 2t + K_2 \cos 2t)$$

$$\therefore v_C(t) = 2 \left\{ -e^{-t} (K_1 \sin 2t + K_2 \cos 2t) + e^{-t} (2K_1 \cos 2t - 2K_2 \sin 2t) \right\}$$

$$\Rightarrow i_L(0) = K_2 = 1 \Rightarrow K_2 = 1$$

$$v_C(0) = 2 \{ -K_2 + 2K_1 \} = 2 \{ -1 + 2K_1 \} = 12$$

$$\Rightarrow K_1 = \frac{7}{2}$$

- c. Using the numbers determined above, write out the complete expression for $i_L(t)$.

$$i_L(t) = e^{-t} \left(\frac{7}{2} \sin 2t + \cos 2t \right) \text{ A}, t \geq 0$$