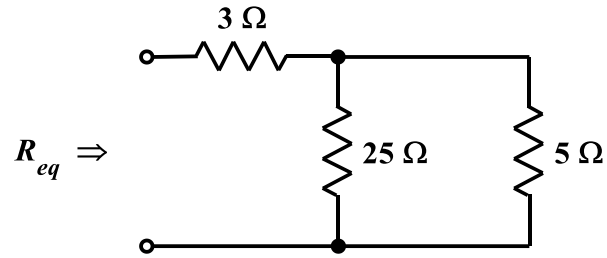


EE 2240  
**Homework Problem #005**



Determine the value of  $R_{eq}$ .