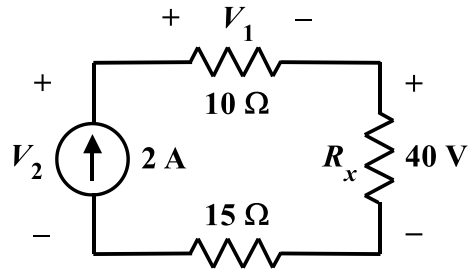


EE 2240
Homework Problem #009

For the circuit shown below:



- Determine the value of V_1 .
- Determine the value of R_x .
- Determine the value of V_2 .
- How much power does R_x absorb?
- How much power does the independent current source deliver?