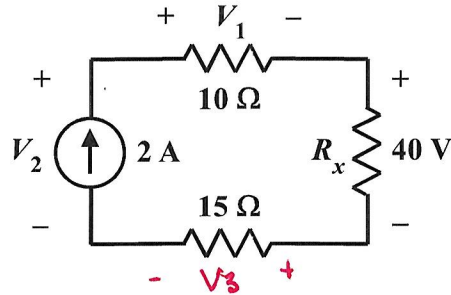


EE 2240
Homework Problem #009

For the circuit shown below:



a. Determine the value of V_1 .

$$V_1 = (10\Omega)(2A) = 20V$$

b. Determine the value of R_x .

$$40V = R_x(2A) \Rightarrow R_x = \frac{40V}{2A} = 20\Omega$$

c. Determine the value of V_2 .

$$V_3 = (15\Omega)(2A) = 30V$$

$$V_2 = V_1 + 40V + V_3 = 20V + 40V + 30V = 90V$$

d. How much power does R_x absorb?

$$P_x = (40V)(2A) = 80W$$

e. How much power does the independent current source deliver?

$$P_s = V_2(2A) = (90V)(2A) = 180W$$