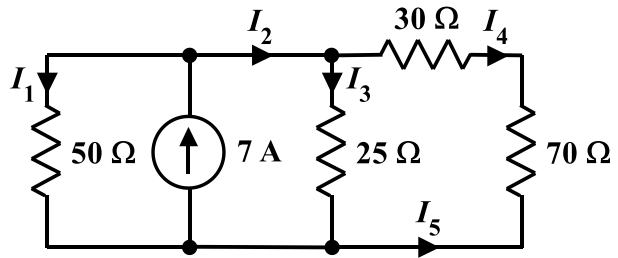


EE 2240
Homework Problem #012



Use equivalent resistance and the current divider equation to determine each of the following:

a. I_1

b. I_2

c. I_3

d. I_4

e. I_5