
EE 2240 **Homework Problem #013**

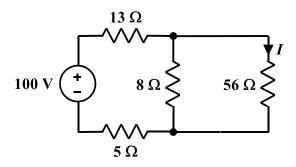

Determine the value of *I*.