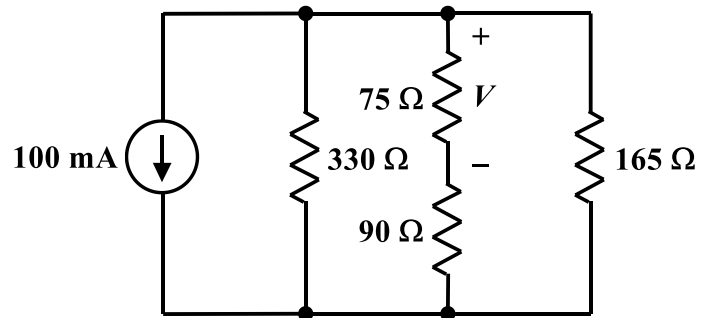


EE 2240
Homework Problem #014



Determine the value of V .