

EE 2240
Homework Problem #022

Use the nodal analysis method to determine V_y .

