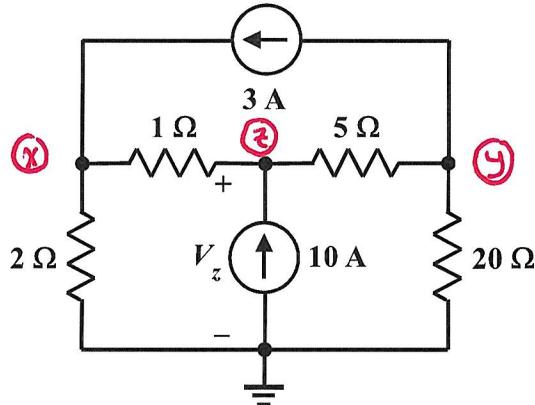


EE 2240
Homework Problem #023

Use the nodal analysis method to determine V_z .



$$-3 + \frac{V_x - V_z}{1\Omega} + \frac{V_x}{2\Omega} = 0$$

$$\frac{V_z - V_x}{1\Omega} - 10A + \frac{V_z - V_y}{5\Omega} = 0$$

$$3A + \frac{V_y - V_z}{5\Omega} + \frac{V_y}{20\Omega} = 0$$

In matrix form:

$$\left[\begin{array}{ccc|c} \frac{3}{2} & 0 & -1 & 3 \\ -1 & -\frac{1}{5} & \frac{6}{5} & 10 \\ 0 & \frac{1}{4} & -\frac{1}{5} & -3 \end{array} \right]$$

Solving,

$$V_z = \frac{\begin{vmatrix} \frac{3}{2} & 0 & 3 \\ -1 & -\frac{1}{5} & 10 \\ 0 & \frac{1}{4} & -3 \end{vmatrix}}{\begin{vmatrix} \frac{3}{2} & 0 & -1 \\ -1 & -\frac{1}{5} & \frac{6}{5} \\ 0 & \frac{1}{4} & -\frac{1}{5} \end{vmatrix}} = \frac{\frac{0.9 - 0.75 - 3.75}{0.06 + 0.25 - 0.45}}{-0.14} = \frac{-3.6}{-0.14} V = 25.7143 V$$