

EE 2240  
**Homework Problem #024**

Use the nodal analysis method to determine  $V_a$ .

