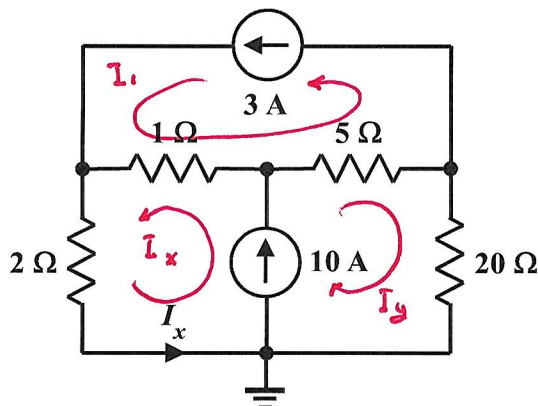


EE 2240
Homework Problem #029

- a. Assign mesh currents and express the mesh equations in the matrix form discussed in class.



$$I_1 = 3A$$

$$I_x + I_y = 10A$$

$$1(I_1 - I_x) + 5(I_y + I_1) + 20I_y - 2I_x = 0$$

In matrix form:

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 1 \\ 6 & -3 & 25 \end{bmatrix} \begin{bmatrix} I_1 \\ I_x \\ I_y \end{bmatrix} = \begin{bmatrix} 3 \\ 10 \\ 0 \end{bmatrix}$$

- b. Use MATLAB to solve the equations and determine the value of I_x . Show your work.

See the results on the next page.

$$I_x \approx 9.5714 A$$

```
>> A=[1 0 0; 0 1 1; 6 -3 25]
```

```
A =
```

```
1 0 0  
0 1 1  
6 -3 25
```

```
>> c=[3 10 0]'
```

```
c =
```

```
3  
10  
0
```

```
>> b=A\c
```

```
b =
```

```
3.0000 ← [1  
9.5714 ← [x  
0.4286 ← [y
```

```
>>
```