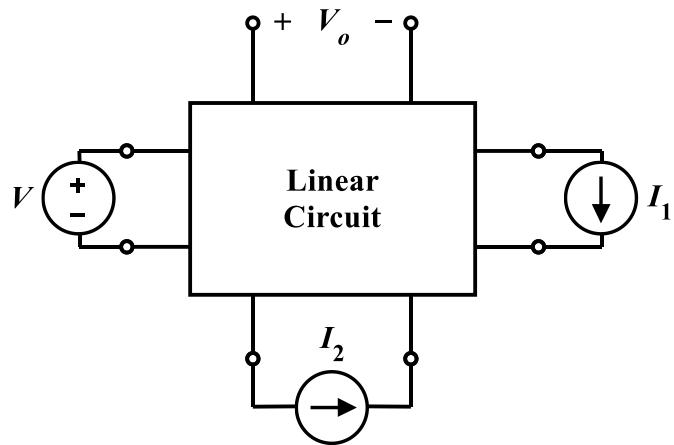


EE 2240
Homework Problem #033



$V_o = 20\text{V}$ when $V = 2\text{V}$, $I_1 = 0\text{A}$ and $I_2 = 2\text{A}$.

$V_o = 30\text{V}$ when $V = 5\text{V}$, $I_1 = 2\text{A}$ and $I_2 = 1\text{A}$.

$V_o = 50\text{V}$ when $V = 6\text{V}$, $I_1 = 3\text{A}$ and $I_2 = 5\text{A}$.

What will V_o be when $V = 5\text{V}$, $I_1 = 3\text{A}$ and $I_2 = 4\text{A}$?