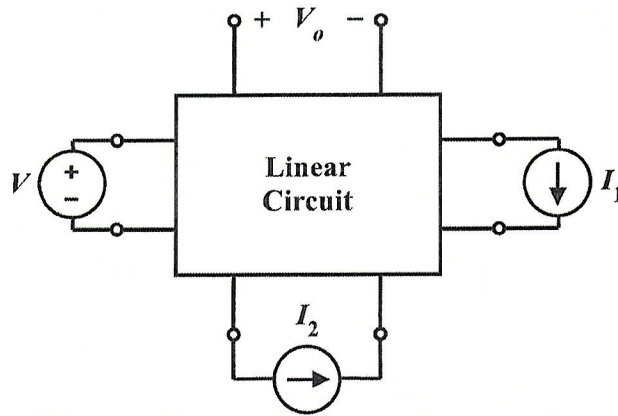


EE 2240
Homework Problem #033



$V_o = 20\text{ V}$ when $V = 2\text{ V}$, $I_1 = 0\text{ A}$ and $I_2 = 2\text{ A}$.

$V_o = 30\text{ V}$ when $V = 5\text{ V}$, $I_1 = 2\text{ A}$ and $I_2 = 1\text{ A}$.

$V_o = 50\text{ V}$ when $V = 6\text{ V}$, $I_1 = 3\text{ A}$ and $I_2 = 5\text{ A}$.

What will V_o be when $V = 5\text{ V}$, $I_1 = 3\text{ A}$ and $I_2 = 4\text{ A}$?

Assume $V_o = aV + bI_1 + cI_2$

Then

$$\begin{aligned} a(2\text{V}) + b(0\text{A}) + c(2\text{A}) &= 20\text{V} \\ a(5\text{V}) + b(2\text{A}) + c(1\text{A}) &= 30\text{V} \\ a(6\text{V}) + b(3\text{A}) + c(5\text{A}) &= 50\text{V} \end{aligned}$$

In matrix form:

$$\begin{bmatrix} 2 & 0 & 2 \\ 5 & 2 & 1 \\ 6 & 3 & 5 \end{bmatrix} \begin{bmatrix} a \\ b \\ c \end{bmatrix} = \begin{bmatrix} 20 \\ 30 \\ 50 \end{bmatrix}$$

See the next page for the MATLAB solution:

$$\text{new } V_o = 40\text{ V}$$

```
>> A=[2 0 2; 5 2 1; 6 3 5]
```

```
A =
```

```
2 0 2  
5 2 1  
6 3 5
```

```
>> c=[20 30 50]'
```

```
c =
```

```
20  
30  
50
```

```
>> abc=A\c
```

```
abc =
```

```
6.0000  
-2.0000  
4.0000
```

```
>> newVo=[5 3 4]*abc
```

```
newVo =
```

```
40
```

```
>>
```