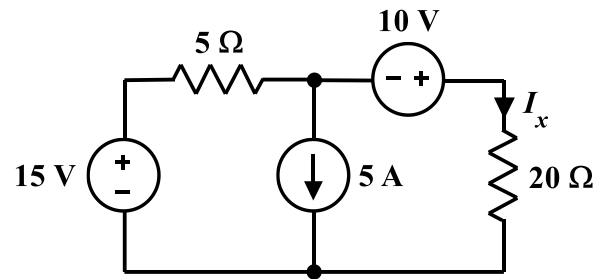


EE 2240  
**Homework Problem #034**



Use the superposition method to determine the value of  $I_x$ .