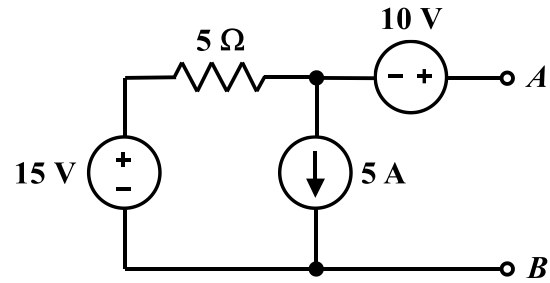


EE 2240
Homework Problem #036



Determine the Thévenin equivalent circuit with respect to terminals *A* and *B*.