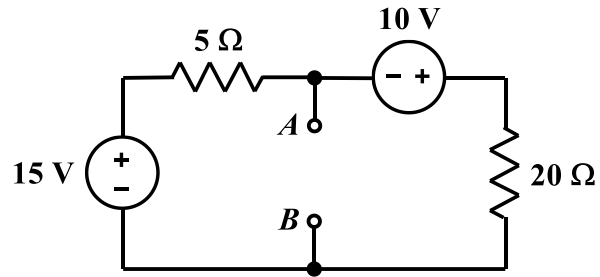


EE 2240
Homework Problem #038



Determine the Norton equivalent circuit with respect to terminals *A* and *B*.