
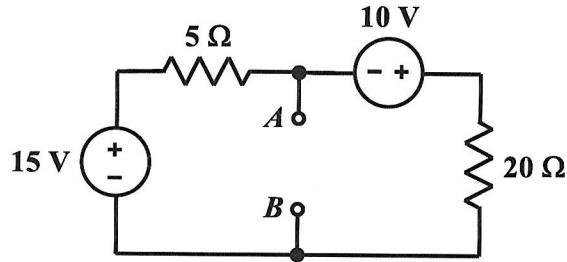


EE 2240  
Homework Problem #038

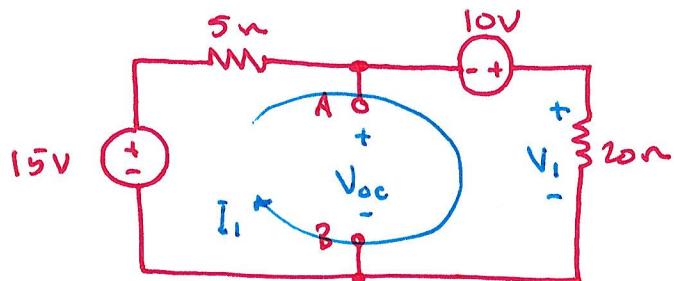

Determine the Norton equivalent circuit with respect to terminals *A* and *B*.

*Under open-circuit conditions:*




$$I_1 = \frac{15V + 10V}{5\Omega + 20\Omega} = \frac{25V}{25\Omega} = 1A$$

$$V_i = (20\Omega) I_1 = 20V$$

$$V_{oc} = -10V + V_i = 10V$$

*Under short-circuit conditions:*

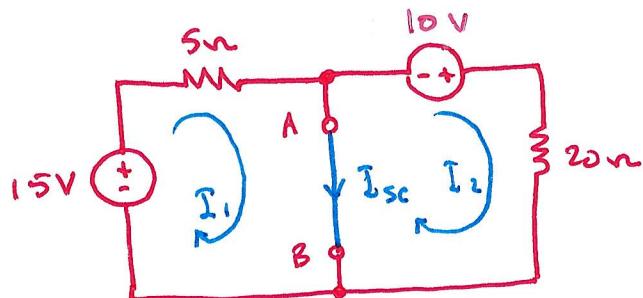

Using superposition:

$$I_1 = \frac{15V}{5\Omega} = 3A$$

$$I_2 = \frac{10V}{20\Omega} = \frac{1}{2}A$$

$$I_{sc} = I_1 - I_2 = 2.5A$$

$$I_N = I_{sc} = 2.5A$$

$$R_N = \frac{V_{oc}}{I_{sc}} = \frac{10V}{2.5A} = 4\Omega$$

So, we have the following Norton equivalent circuit:

