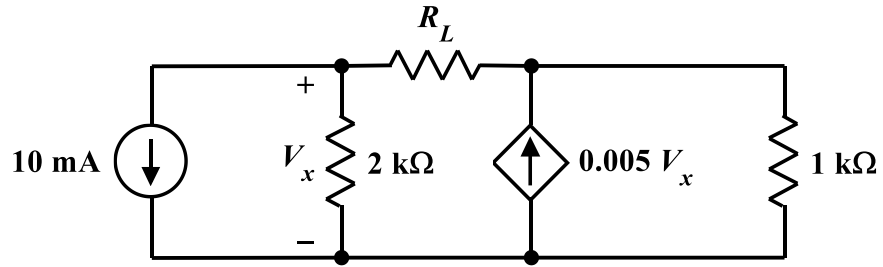


EE 2240  
**Homework Problem #045**



What value of  $R_L$  will absorb maximum power from the remainder of the circuit?