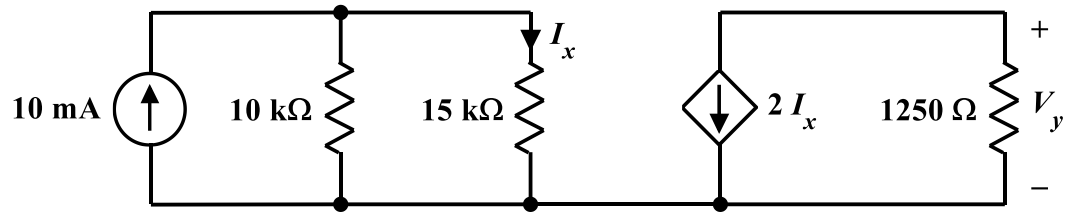


EE 2240
Homework Problem #046



Determine the value of V_y .