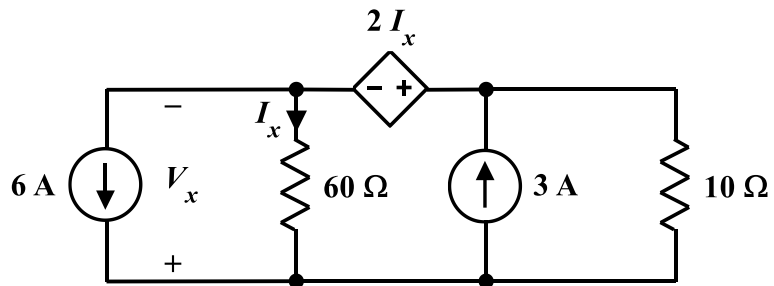


EE 2240
Homework Problem #047



Determine the value of V_x .