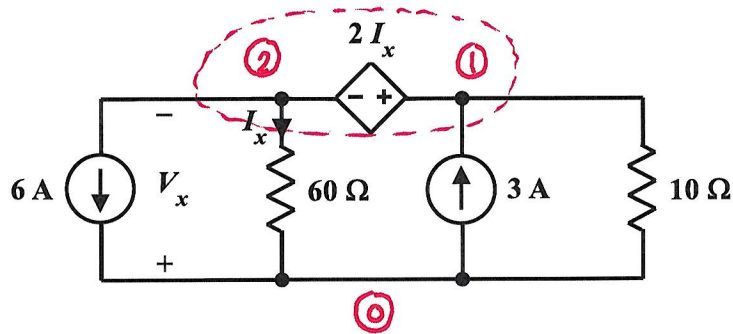


EE 2240
Homework Problem #047



Determine the value of V_x .

Use nodal analysis:

$$V_1 - V_2 = 2 I_x$$

$$6A + \frac{V_2}{60\Omega} - 3A + \frac{V_1}{10\Omega} = 0$$

$$I_x = \frac{V_2}{60\Omega}$$

$$V_x = -V_2$$

In matrix form:

$$\begin{bmatrix} 1 & -1 & -2 & 0 \\ 1/10 & 1/60 & 0 & 0 \\ 0 & -1/60 & 1 & 0 \\ 0 & 1 & 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ I_x \\ V_x \end{bmatrix} = \begin{bmatrix} 0 \\ -3 \\ 0 \\ 0 \end{bmatrix}$$

Solving yields:

$$V_x = 25V$$

(See MATLAB solution on next page.)

```
>> A=[1 -1 -2 0; 1/10 1/60 0 0; 0 -1/60 1 0; 0 1 0 1]
```

```
A =
```

```
1.0000 -1.0000 -2.0000 0
0.1000 0.0167 0 0
0 -0.0167 1.0000 0
0 1.0000 0 1.0000
```

```
>> c=[0 -3 0 0]'
```

```
c =
```

```
0
-3
0
0
```

```
>> b=A\c
```

```
b =
```

```
-25.8333
-25.0000
-0.4167
25.0000
```