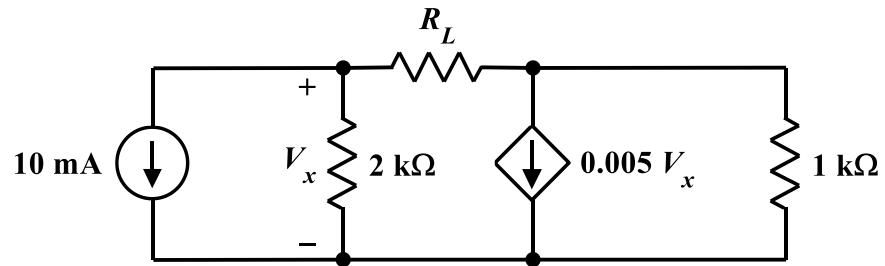


EE 2240
Homework Problem #049



What value of R_L will absorb maximum power from the remainder of the circuit?