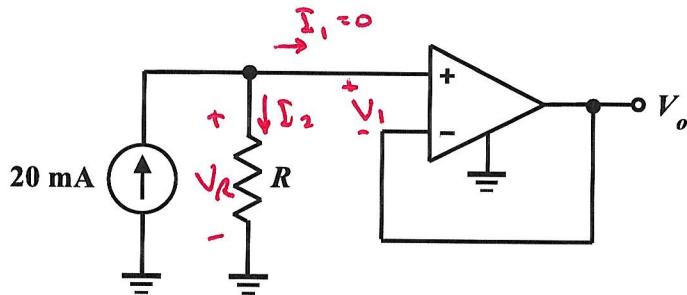


EE 2240  
Homework Problem #051



The OpAmp is ideal. Determine the value of  $R$  required to make  $V_o = 10V$ .

$$V_i = 0 \Rightarrow V_R = V_i + V_o \\ = V_o$$

$$I_1 = 0 \Rightarrow I_2 = 20 \text{ mA}$$

$$\therefore V_R = R I_2 = R(20 \text{ mA})$$

$$\text{But } V_o = 10 \text{ V}$$

$$\Rightarrow R(20 \text{ mA}) = 10 \text{ V}$$

$$\text{So } R = \frac{10 \text{ V}}{20 \text{ mA}} = 500 \text{ }\Omega$$