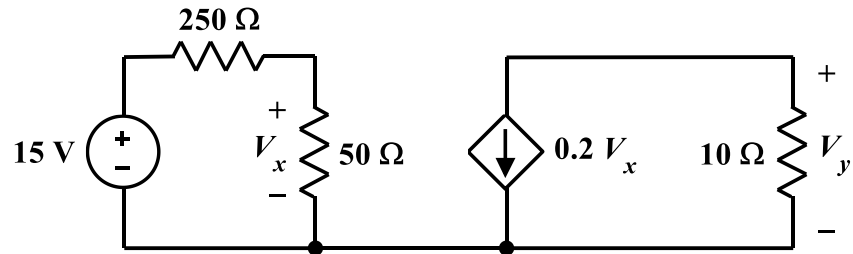


EE 2240
Homework Problem #059

Use LTspice to determine the value of V_y .



Submit a printed copy of your netlist and a printed copy of your output. Highlight the required result.