
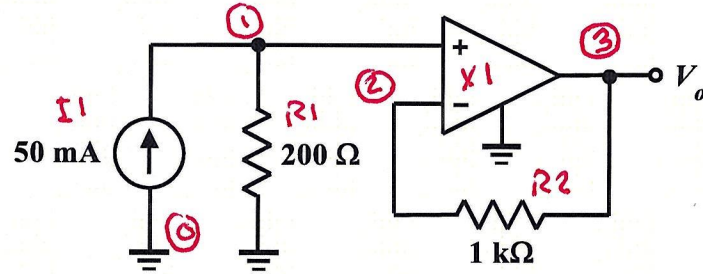


EE 2240
Homework Problem #062

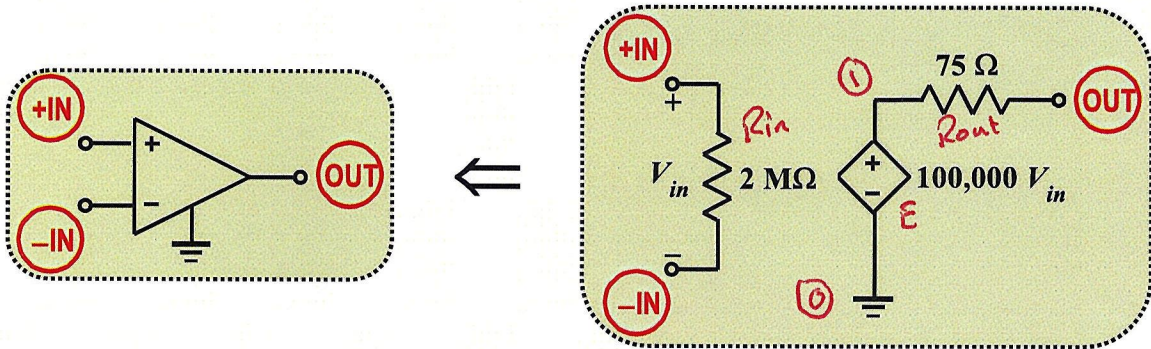Use LTspice to determine the value of V_o .



Use the model shown below for the OpAmp.



Submit a printed copy of your netlist and a printed copy of your output. Highlight the required result.

EE2240 Fall 2021 Homework Problem #062.cir

```
I1      0      1      DC      50m
R1      1      0      200
X1      1      2      3      opamp
R2      2      3      1k
.subckt opamp +IN -IN OUT
Rin     +IN     -IN     2Meg
E       1      0      +IN     -IN     100k
Rout    1      OUT     75
.ends opamp
.op
.end
```

```
--- Operating Point ---
V(1):      10          voltage
V(2):      9.9999     voltage
V(3):      9.9999     voltage ← No
I(I1):     0.05       device_current
I(R2):     4.98407e-011 device_current
I(R1):     0.05       device_current
Ix(1:+IN): 4.99995e-011 subckt_current
Ix(1:-IN): -4.99995e-011 subckt_current
Ix(1:OUT): 4.98407e-011 subckt_current
```