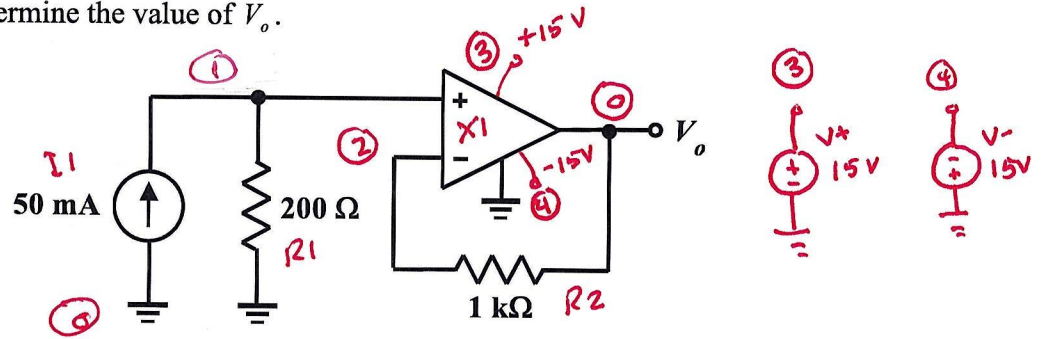


EE 2240  
Homework Problem #063

Use LTspice to determine the value of  $V_o$ .



Use the LM741/NS model for the OpAmp.

Submit a printed copy of your netlist and a printed copy of your output. Highlight the required result.

EE2240 Fall 2021 Homework Problem #063.cir

.LIB LM741.MOD

```
I1      0      1      DC      50m
R1      1      0      200
X1      1      2      3      4      o      LM741/NS
V+      3      0      DC      15
V-      0      4      DC      15
R2      2      o      1k
.op
.end
```

```
--- Operating Point ---
V(1):      9.99999      voltage
V(2):      10.0013      voltage
V(4):      -15      voltage
V(3):      15      voltage
V(o):      10.0014      voltage ← Vo
I(I1):      0.05      device_current
I(R2):      -1.02323e-007      device_current
I(R1):      0.0499999      device_current
I(V-):      -0.00170117      device_current
I(V+):      -0.00170111      device_current
Ix(1:1):      5.74126e-008      subckt_current
Ix(1:2):      1.02323e-007      subckt_current
Ix(1:99):      0.00170111      subckt_current
Ix(1:50):      -0.00170117      subckt_current
Ix(1:28):      -1.02323e-007      subckt_current
```