
## EE 2240 **Homework Problem #065**

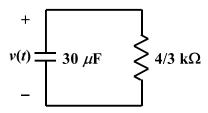

Given v(0) = 75 V, determine v(t) for  $t \ge 0$ .