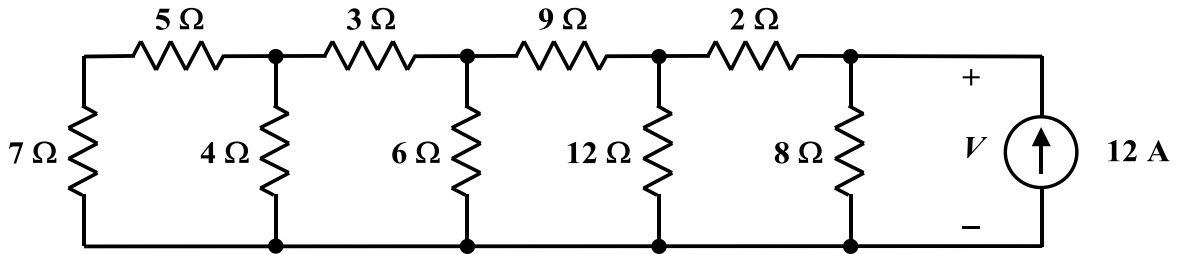


EE 2240
Problem #02



- a. Using series and parallel resistance reductions, find the equivalent resistance seen by the source.

- b. What is the voltage, V , across the source?