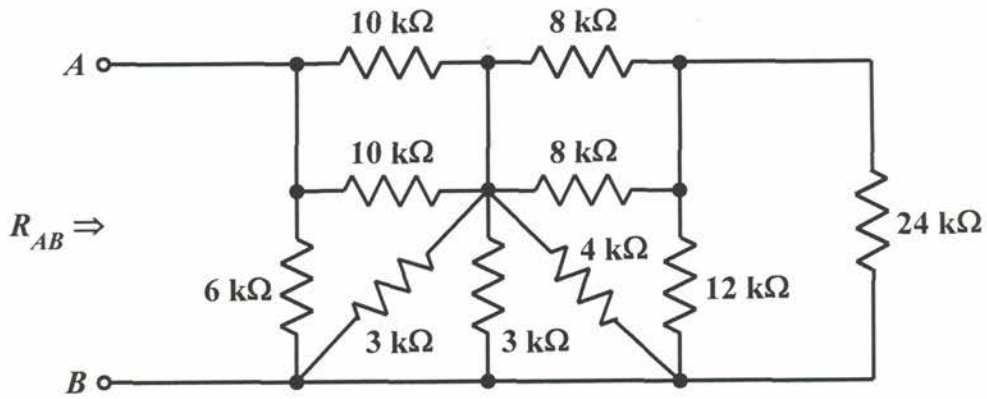


EE 2240
Problem #06

Find R_{AB} .



$$10\text{ k}\Omega \parallel 10\text{ k}\Omega = 5\text{ k}\Omega$$

$$8\text{ k}\Omega \parallel 8\text{ k}\Omega = 4\text{ k}\Omega$$

$$12\text{ k}\Omega \parallel 24\text{ k}\Omega = 8\text{ k}\Omega$$

$$4\text{ k}\Omega + 8\text{ k}\Omega = 12\text{ k}\Omega$$

$$4\text{ k}\Omega \parallel 12\text{ k}\Omega = 3\text{ k}\Omega$$

$$3\text{ k}\Omega \parallel 3\text{ k}\Omega = 1.5\text{ k}\Omega$$

$$3\text{ k}\Omega \parallel 1.5\text{ k}\Omega = 1\text{ k}\Omega$$

$$5\text{ k}\Omega + 1\text{ k}\Omega = 6\text{ k}\Omega$$

$$R_{AB} = 6\text{ k}\Omega \parallel 6\text{ k}\Omega = 3\text{ k}\Omega$$