

EE 2240
Problem #07

Given $V_2 = 10\text{ V}$, $V_3 = 10\text{ V}$, and $V_4 = 10\text{ V}$, find V_1 and V_5 .

