

EE 2240  
Problem #08

Find  $V_1$  and  $V_2$ .

