

EE 2240
Problem #01

What value should be chosen for R_L so that it will absorb maximum power from the rest of the circuit?

