EE 2240 **Problem #08**

Use mesh analysis to find I_o .

